
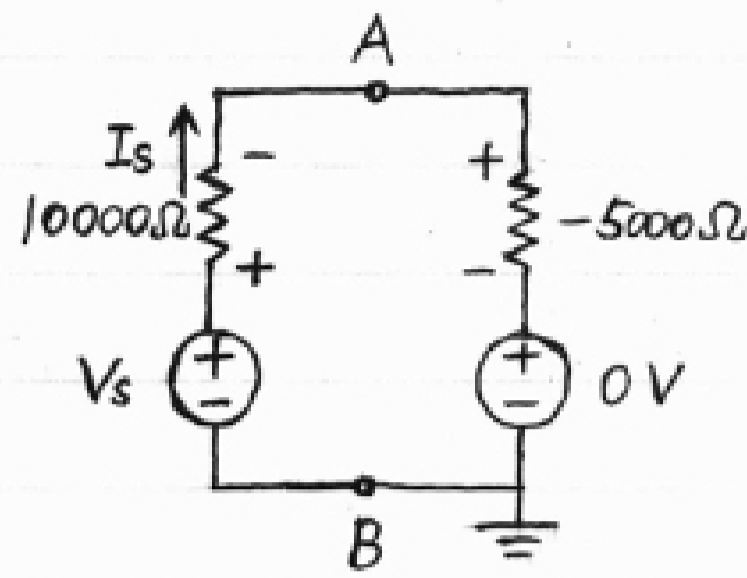


6-31

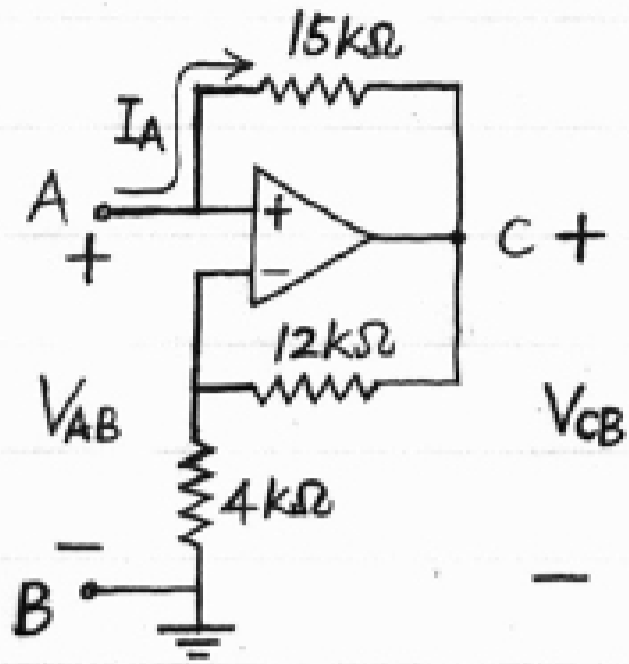

$$(a) V_{CB} = \left(1 + \frac{12k}{4k}\right) V_{AB} = 4 V_{AB} \quad (\text{non-inverting op amp circuit})$$

$$V_{AB} = (15k) I_A + V_{CB} \quad (\text{KVL}) \Rightarrow -3 V_{AB} = (15k) I_A$$

$$\therefore V_{AB} = (-5000) I_A$$


Match coefficients with (6.5):

$$R_{th} = -5000 \Omega, \quad V_{oc} = 0 \text{ V.}$$

$$(b) \text{ KVL: } V_s = (10000) I_s + (-5000) I_s + 0 = (5000) I_s$$

$$\therefore I_s = \frac{V_s}{5000}$$

Ch-6 Prob. 32

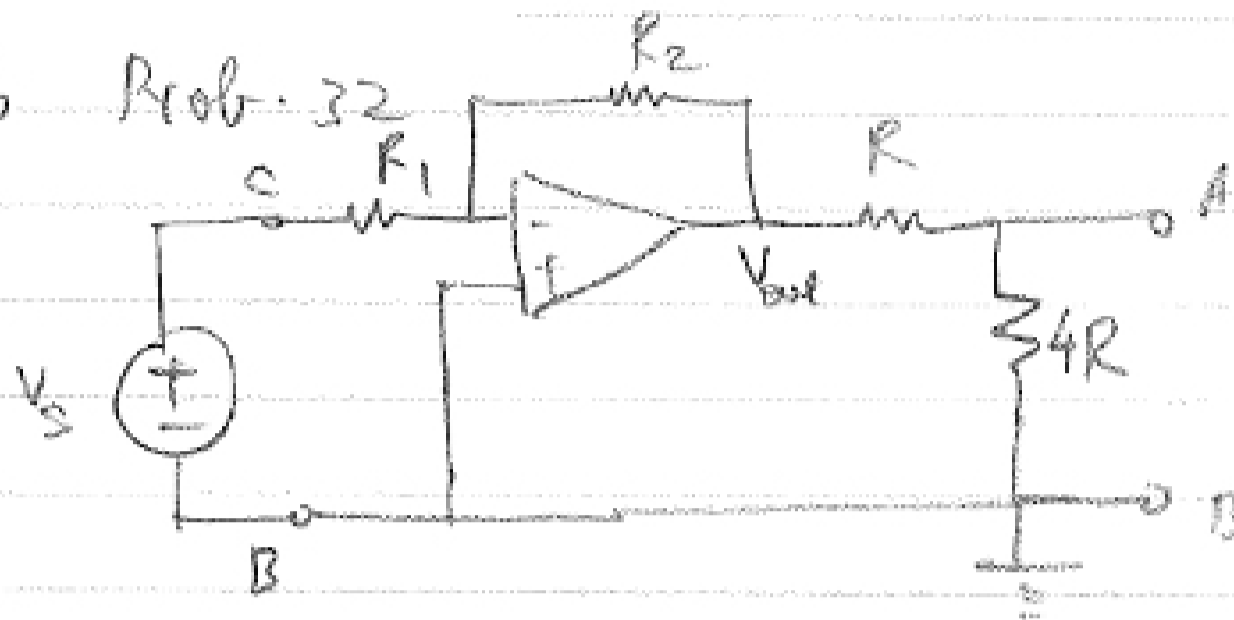

(a) Thevenin/Norton equivalent looking into AB

(i) Find  $V_{oc}$

OP-Amp is in -ve feedback & is inverting

$$\Rightarrow V_{out} = -\frac{R_2}{R_1} V_s$$


$$\Rightarrow V_{oc} = \frac{4}{5} \left( -\frac{R_2}{R_1} \right) V_s$$

(ii) Find  $I_{sc}$  (short AB)


$$I_{sc} = \frac{V_{out}}{R} = -\frac{R_2}{R_1 R} V_s$$

$$R_{th} = \frac{V_{oc}}{I_{sc}} = \frac{\frac{4}{5} \left( -\frac{R_2}{R_1} \right) V_s}{-\frac{R_2}{R_1 R} V_s} = \frac{4}{5} R$$

Thevenin equivalent :

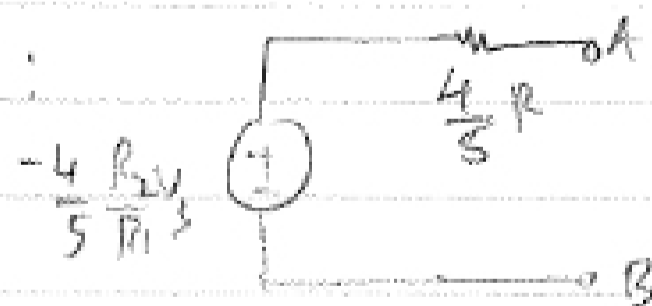

Norton equivalent

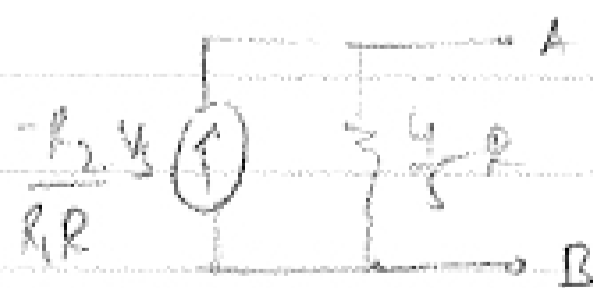

⑥ Looking in through CB

$V_{oc} = I_{sc} = 0$   $\therefore$  there are no independent sources in the circuit under consideration

To find  $R_{th}$ , add a test source  $V_t$  between C & B

$$\text{test current } I_t = \frac{V_t - V_c}{R_1} = \frac{V_t - 0}{R_1}$$

$$\frac{V_t}{I_t} = \underline{\underline{R_{th} = R_1}}$$

Thevenin / Norton equivalent: 