

4.43 Note that  $i(t)$  is in mA where  
 $1 \text{ mA} = 10^{-3} \text{ A}$

a.  $I(j\omega) = 17 \times 10^{-3} \angle^{-\pi/12} \text{ A}$   
 $V(j\omega) = 3.5 \angle 1.309 \text{ V}$

*both angles are in radians*

Basic V-I relationship in an impedance

$$V = ZI \rightarrow Z = \frac{V}{I}$$

$$Z = \frac{3.5 \angle 1.309 \text{ V}}{17 \times 10^{-3} \angle^{-\pi/12} \text{ A}} = \frac{3.5}{17 \times 10^{-3}} \angle 1.309 + \frac{\pi}{12} \Omega$$

$$= 205.9 \angle 1.5708 \text{ rad} \Omega = 205.9 \angle \frac{\pi}{2} \Omega$$

*need to recognize this to finish problem, if we solved in degrees you would see this immediately.*

The device could potentially be an inductor, capacitor, or resistor (the components we know). Looking at the phasor form of these components, we see

$$Z_L(j\omega) = \omega L \angle \frac{\pi}{2} \Omega$$

Since this matches the angle of the unknown  $Z$  we can say that the device is an inductor.


b.  $\omega L = 205.9 \Omega$

$$L = \frac{205.9}{628.3} \text{ H} = 0.327 \text{ H} = 327 \text{ mH}$$

*given*

P 4.47

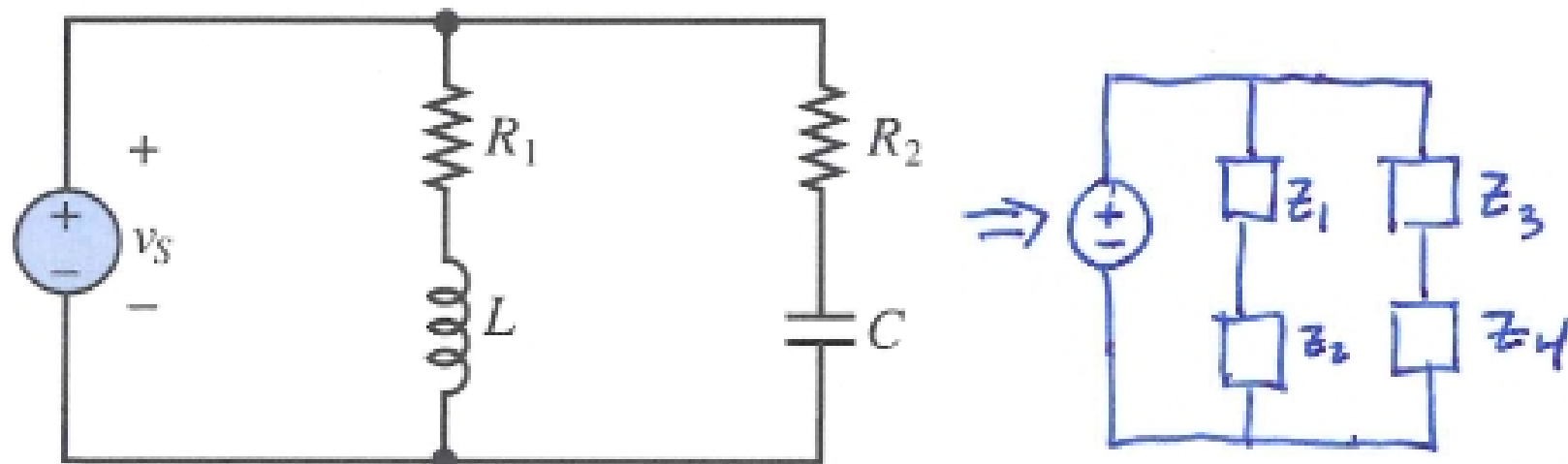Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



$$v_s(t) = 7 \cos(\underbrace{3,000t}_{\omega} + \frac{\pi}{6}) \text{ V}$$



$$Z_1 = 2.3 \times 10^3 \Omega$$

$$Z_3 = 1.1 \times 10^3 \Omega$$

$$Z_2 = j\omega L = j(3 \times 10^3)(190 \times 10^{-3}) \Omega = j570 \Omega$$

$$Z_4 = \frac{-j}{\omega C} = \frac{-j}{(3 \times 10^3)(55 \times 10^{-9})} = -j6.06 \times 10^3 \Omega$$
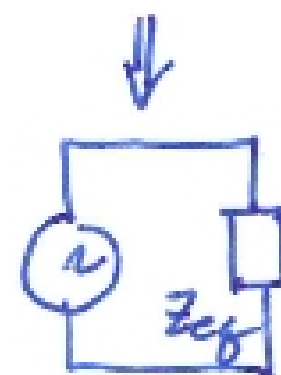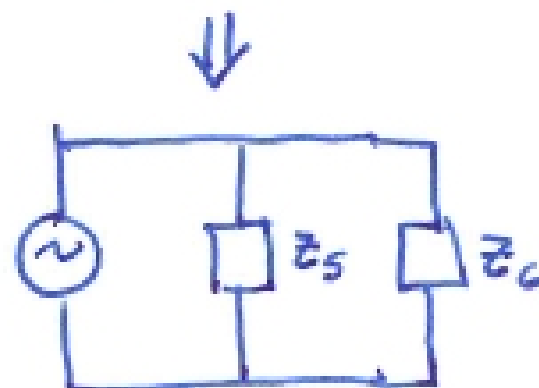
$$\uparrow 1 \text{ nF} = 10^{-9} \text{ F}$$



$$Z_5 = Z_1 + Z_2 = 2.3 \times 10^3 + j570 \Omega = 2.37 \times 10^3 \angle 13.92^\circ \Omega$$

$$Z_6 = Z_3 + Z_4 = 1.1 \times 10^3 - j6.06 \times 10^3 \Omega = 6.16 \times 10^3 \angle -79.71^\circ \Omega$$

$$Z_{eq} = \frac{Z_5 Z_6}{Z_5 + Z_6} = \frac{2.37 \times 10^3 \angle 13.92^\circ \Omega \cdot 6.16 \times 10^3 \angle -79.71^\circ \Omega}{(3.4 \times 10^3 - j5490) \Omega}$$

↑ like parallel resistors


$$= \frac{2.37 \times 6.16 \times 10^6 \angle -65.79^\circ}{6458 \angle -58.23^\circ} \Omega$$

$$= 2.261 \angle -7.56^\circ \text{ k}\Omega$$

$$\uparrow 1 \text{ k}\Omega = 10^3 \Omega$$
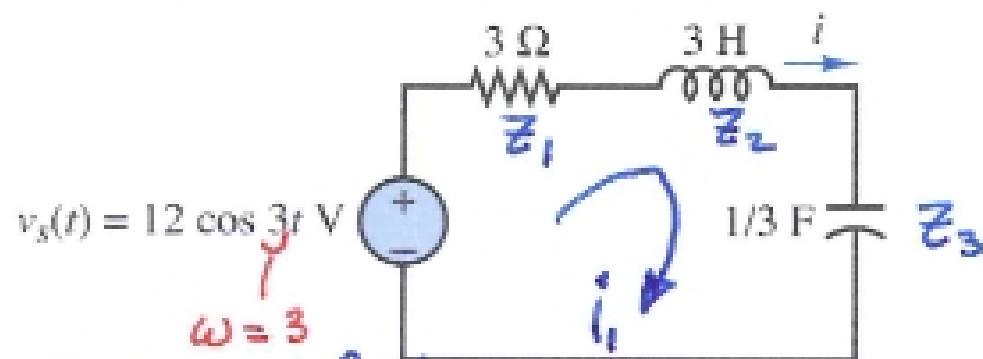
## P 4.54

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



$$v_s(t) = 12 \cos 3t \text{ V}$$

$$\omega = 3$$

$$V(\omega) = 12 \angle 0^\circ \text{ V}$$

Approach 1:

$$Z_{\text{total}} = Z_1 + Z_2 + Z_3 = 3 + j9 - j \Omega = 3 + j8 \Omega$$

$$I = \frac{V}{Z} = \frac{12 \angle 0^\circ \text{ V}}{3 + j8 \Omega} = \frac{12 \angle 0^\circ \text{ V}}{8.54 \angle 69.4^\circ \Omega} = 1.4 \angle -69.4^\circ \text{ A}$$

$$i(t) = 1.4 \cos(3t - 69.4^\circ) \text{ A}$$

Approach 2: Mesh Current

$$\sum_{\text{mesh } 1} V_{\text{drops}} = -12 \angle 0^\circ + Z_1 I_1 + Z_2 I_1 + Z_3 I_1 = 0$$

$$I_1 = \frac{12 \angle 0^\circ}{Z_1 + Z_2 + Z_3} = \frac{12 \angle 0^\circ}{Z_{\text{total}}}$$

Same answer as above

$$Z_1 = 3 \Omega$$

$$Z_2 = j\omega L = j3 \cdot 3 \Omega = j9 \Omega$$

$$Z_3 = \frac{-j}{\omega C} = \frac{-j}{3 \cdot \frac{1}{3}} \Omega = -j$$