
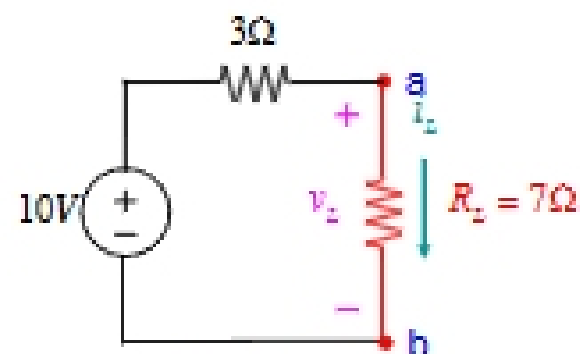
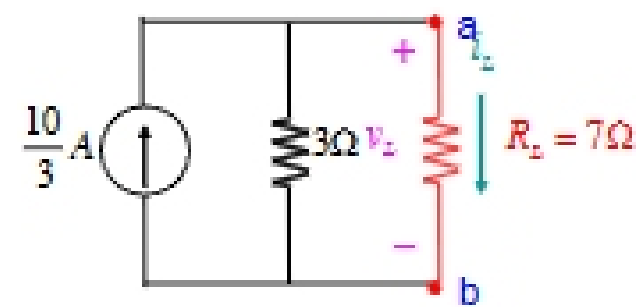


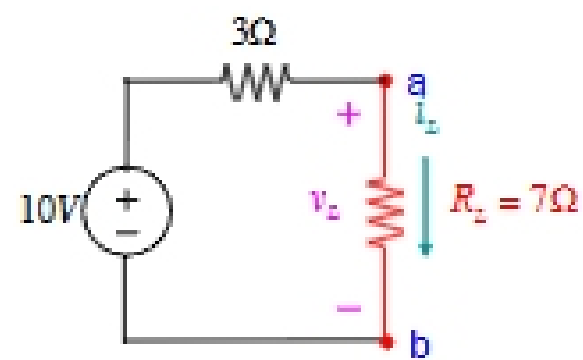Exercise :

Connect a resistive load between (a) and (b) in the two circuits

For: $R_2 = 7\Omega$ Find: $V_2 = ?$ $i_2 = ?$




$$V_2 = (10) \left(\frac{R_2}{R_{tot}} \right)$$

$$V_2 = (10) \frac{7}{3+7} \quad \boxed{V_2 = 7V}$$

$$i_2 = \frac{10}{3+7} \quad \boxed{i_2 = 1A}$$

$$i = \frac{V}{R}$$

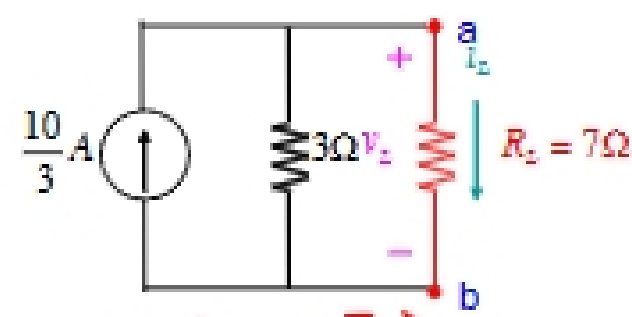

$$i = (i_s) \left(\frac{R}{R_{tot}} \right)$$

$$i_2 = \left(\frac{10}{3} \right) \frac{3}{3+7} \quad \boxed{i_2 = 1A}$$

$$V_2 = (i_2) 7 \quad \boxed{V_2 = 7V}$$

$$V = iR$$


Conclusion:

For the resistive load, the two circuits are equivalent!


Source Transformation

Between node (a) and (b):

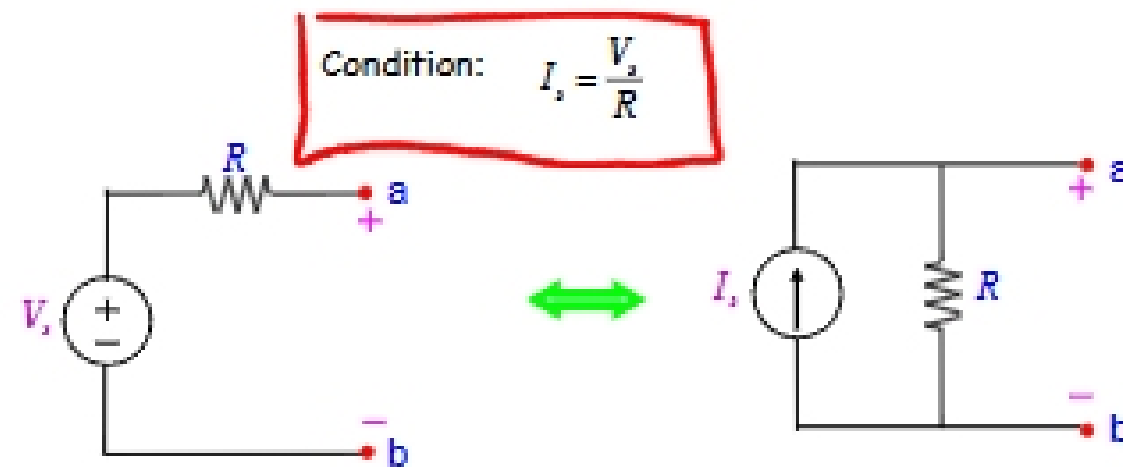Voltage source V_s in series with resistor R can be replaced by a current source I_s in parallel with R and vice versa.




Proof: Concept of equivalent circuits

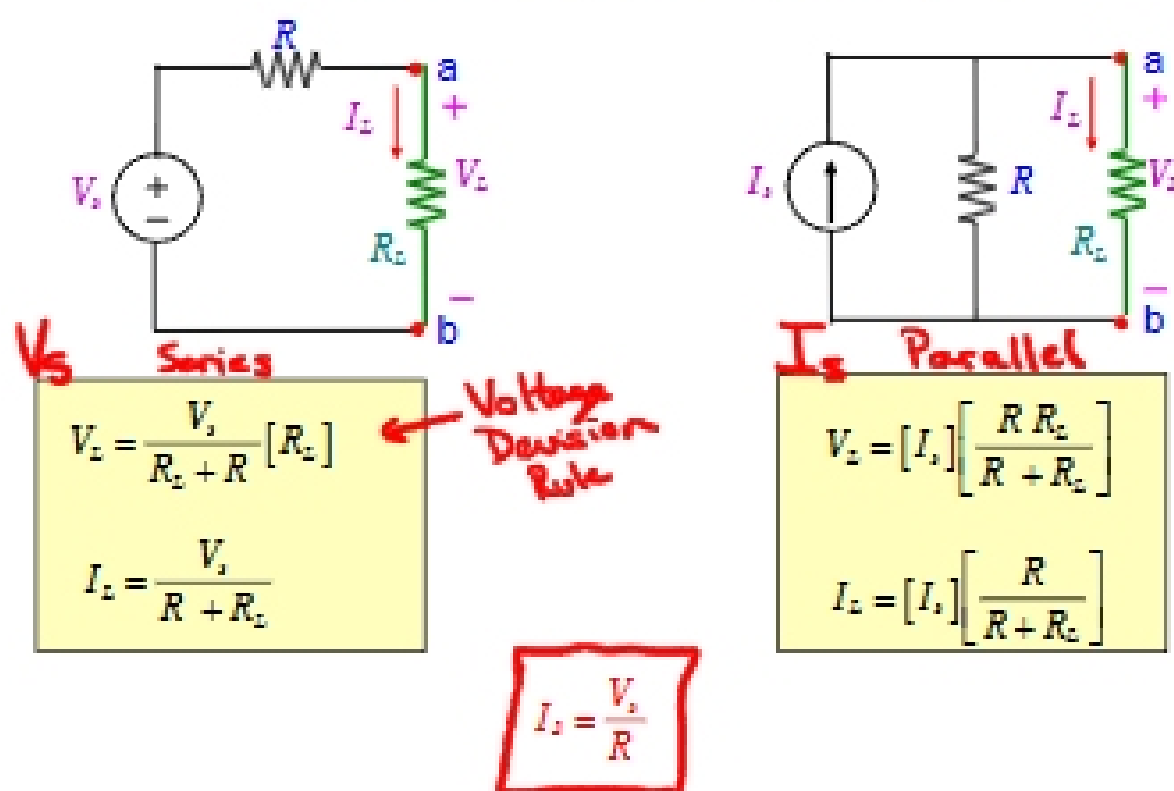


The (i-v) characteristic between (a) and (b) are identical

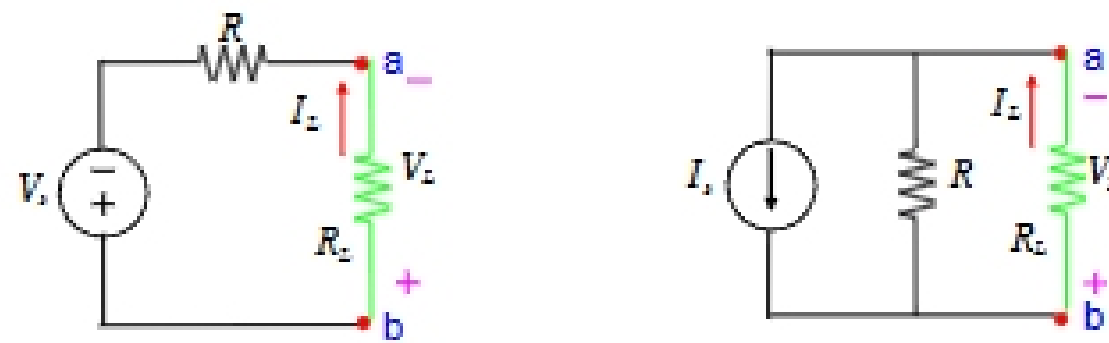Note: If the polarity of the voltage source is reversed, the direction of the current source must also be reversed as shown.



for $I_s = \frac{V_s}{R}$

Example (1)

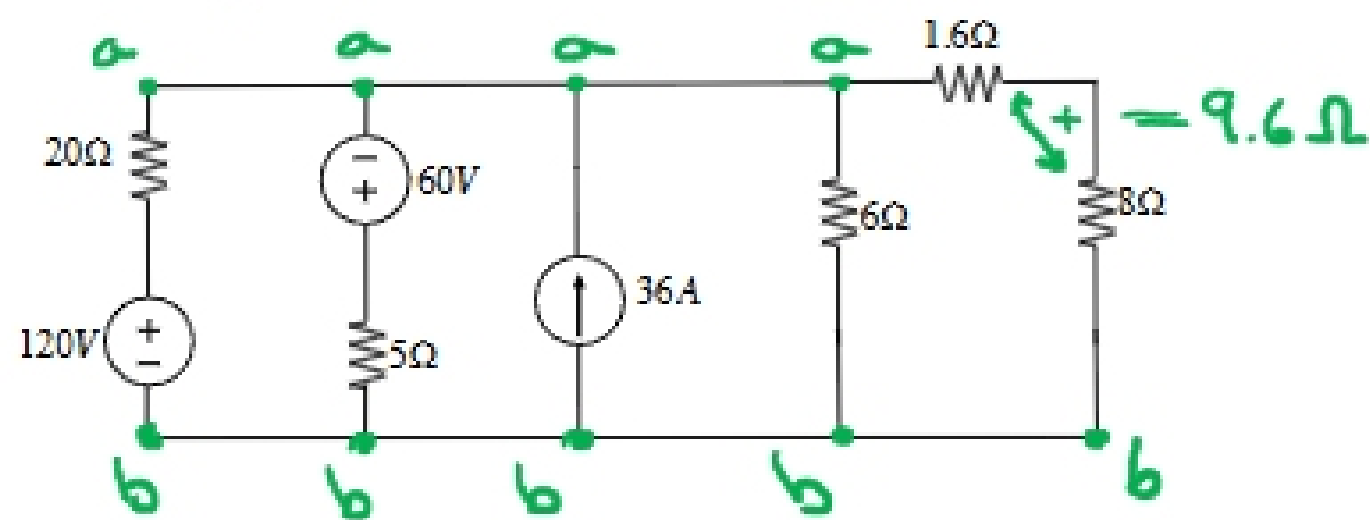

Questions

Use source transformation to find :

- The voltage across the 8 Ohms resistor.
- The power related to the current source
- The power related to the 120V source