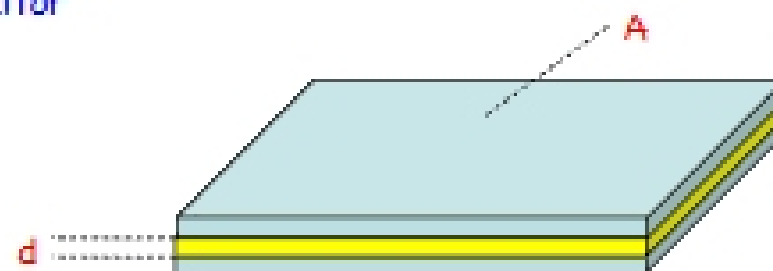


Capacitor

Physical structure :

Two conducting plates separated by dielectric material forms a Capacitor




Capacitance :

A: surface area

d: distance between conducting sheets

ϵ : permittivity of dielectric material


$$C = \frac{\epsilon A}{d}$$

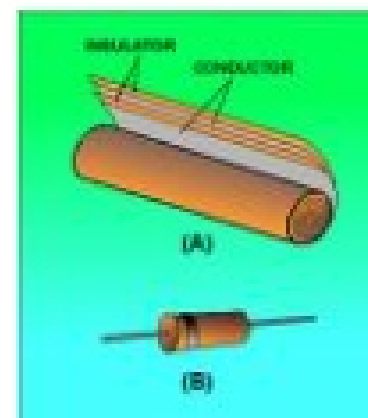

Connecting Capacitor to voltage source:


a) V is constant

$$C = \frac{q}{V}$$

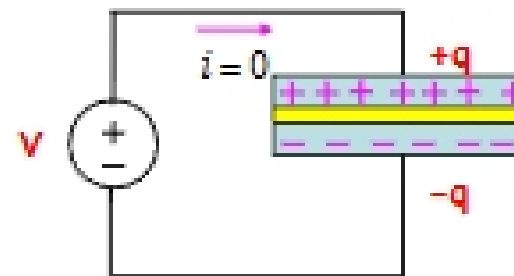

Note : C is constant !

b) $V(t)$ is variable

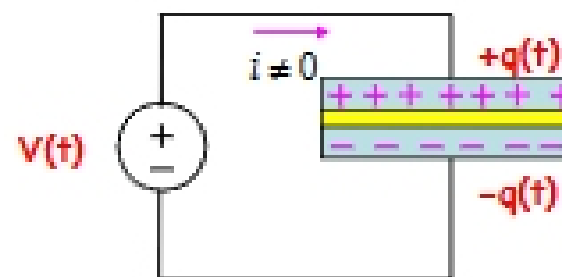

Capacitor symbol:


The (i-v) characteristic:

$$C = \frac{q}{V}$$

$$q = C V$$

$$\frac{dq}{dt} = C \frac{dv}{dt}$$

$$i = C \frac{dv}{dt}$$

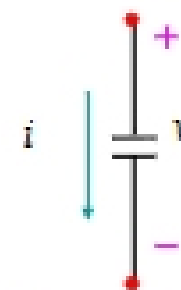


Note: Passive sign convention!

From the above relation the current through the capacitor is proportional to the time rate of change of the voltage across the capacitor

Capacitor (i-v) characteristic:

$$i = C \frac{dv}{dt}$$

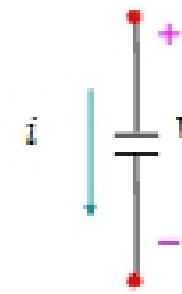

Conclusion (1):

Under steady state, (no variation with time), capacitors are replaced by an open circuit.


$$\text{Steady state} \implies \frac{dv}{dt} = 0 \implies i = 0 \implies \text{Open circuit}$$

Conclusion (2):

Capacitor voltage can not change instantaneously.

$$\text{for } dt \rightarrow 0 \implies i \rightarrow \infty \text{ (impossible)}$$

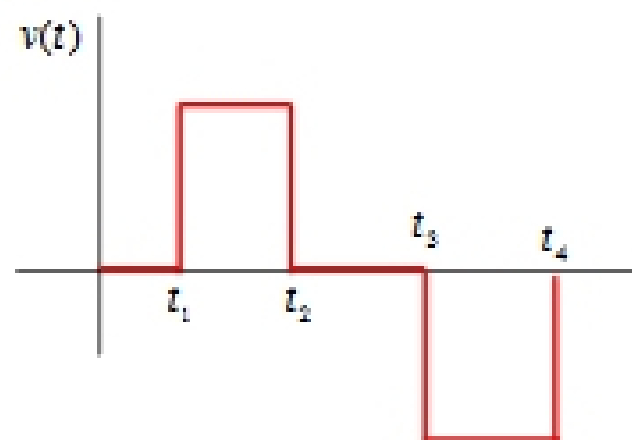Voltage across capacitor changes gradually not abruptly!



Capacitor voltage can not change abruptly as shown !!