
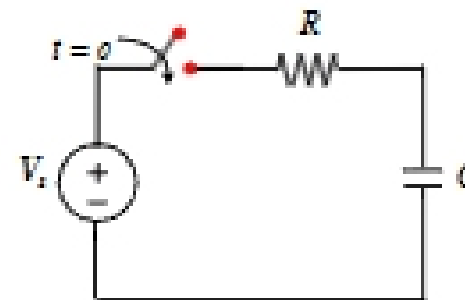


Step Response of first order circuits

Sudden application or variation of a DC sources.

Initial energy stored within capacitor is defined in terms of initial voltage v_c (at $t=0$)

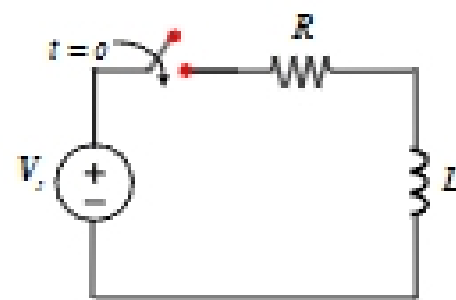Initial energy stored within inductor is defined in terms of initial current i_L (at $t=0$)



RL circuit

$t = 0^-$ just before action


$t = 0^+$ just after action

Note!



Inductor current can not change instantaneously


$$i_L(0^-) = i_L(0^+)$$

Switch is closed at $t=0$

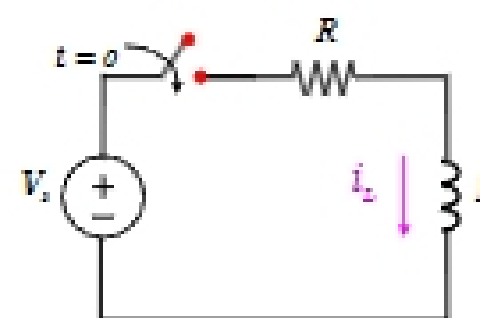

$$i_L(0^-) = i_L(0^+)$$

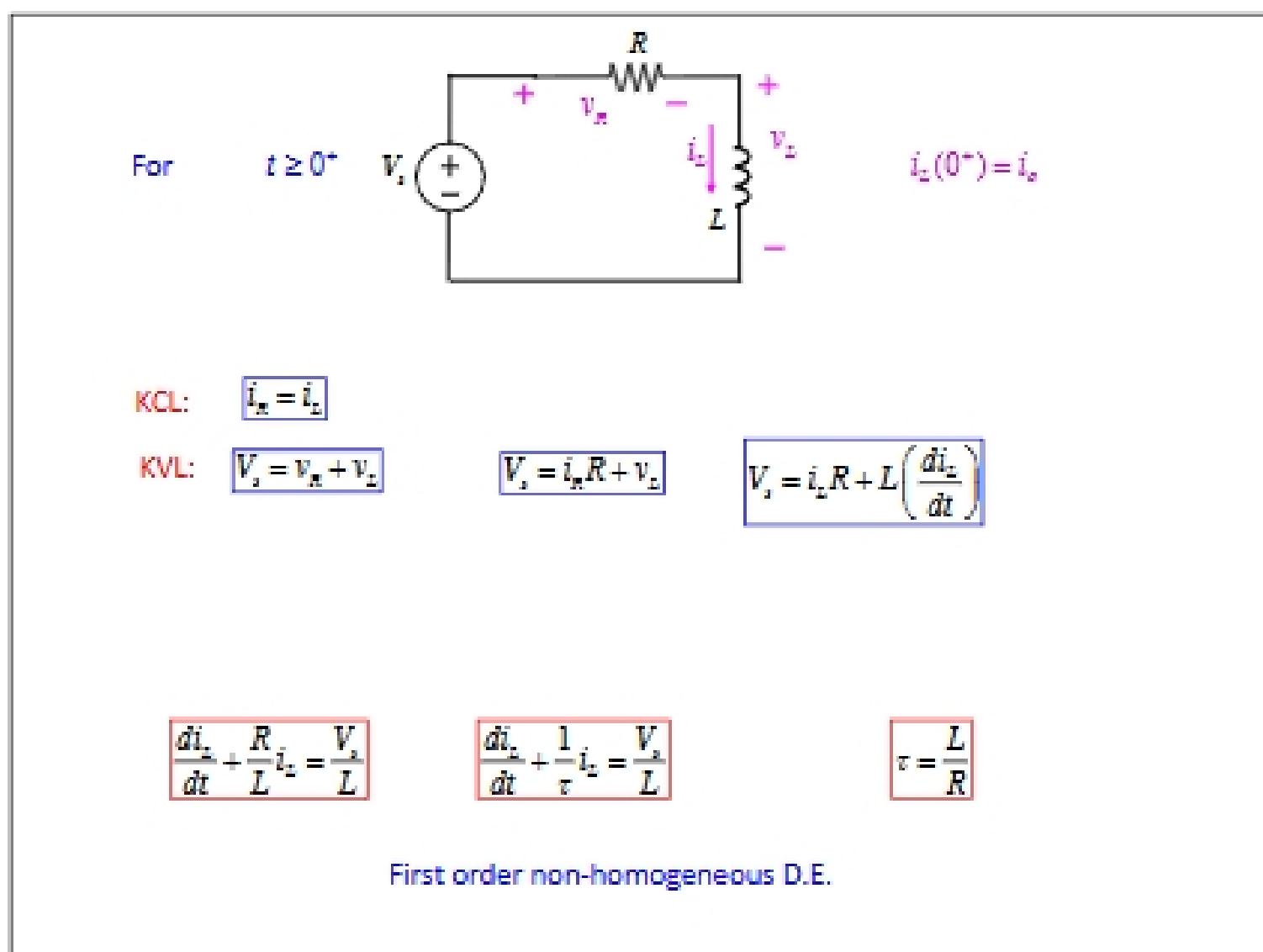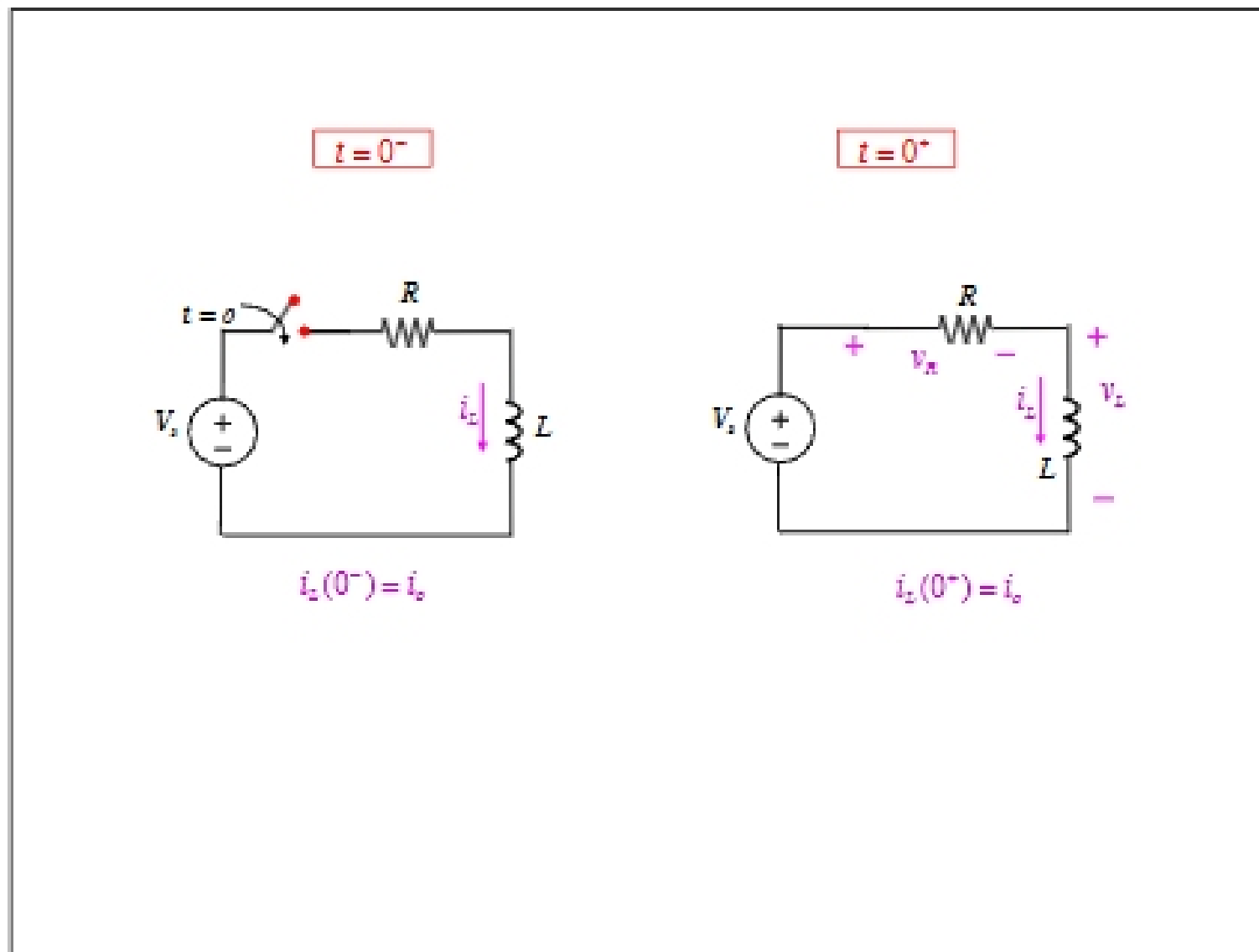

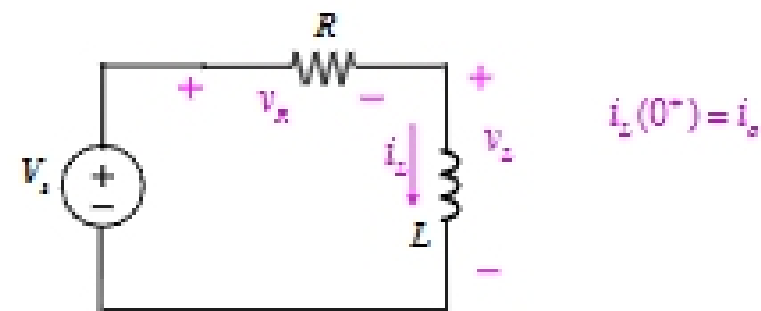


D.E. $\frac{di_L}{dt} + \frac{1}{\tau}i_L = \frac{V_s}{L}$ where $\tau = \frac{L}{R}$

Solution: $i_L(t) = \frac{V_s}{R} + \left(i_0 - \frac{V_s}{R}\right)e^{-\frac{t}{\tau}}$ $t \geq 0^+$

Check:

$t = 0^+$ $i_L(0^+) = \frac{V_s}{R} + \left(i_0 - \frac{V_s}{R}\right) = i_0$ (initial value)

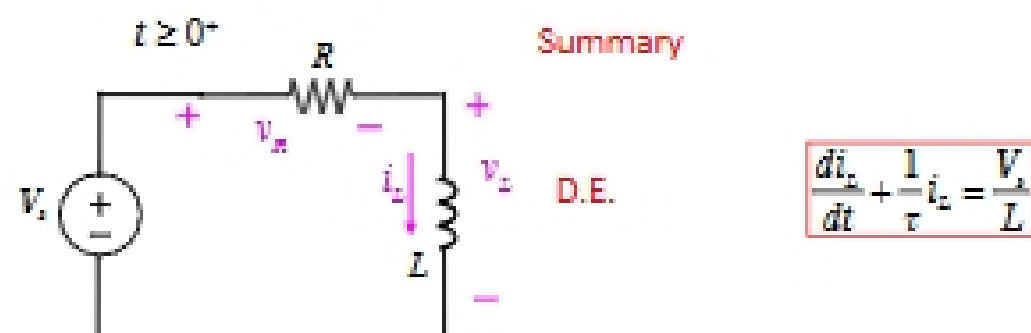$t = \infty$ $i_L(\infty) = \frac{V_s}{R} + \left(i_0 - \frac{V_s}{R}\right)(0) = \frac{V_s}{R}$ (final value)



Summary

D.E.

$$\frac{di_L}{dt} + \frac{1}{\tau}i_L = \frac{V_s}{L}$$

From the circuit connection at $t = 0^+$ $i_L(0^+) = i_0$

From the circuit connection at $t = \infty$ $i_L(\infty) = \frac{V_s}{R}$

From the circuit connection at $t \geq 0^+$ $\tau = \frac{L}{R}$

Solution: $i_L(t) = \frac{V_s}{R} + \left(i_0 - \frac{V_s}{R}\right)e^{-\frac{t}{\tau}}$ $t \geq 0^+$

$$i_L(t) = (\text{final}) + (\text{initial} - \text{final})e^{-\frac{t}{\tau}} \quad t \geq 0^+$$