

EECS150 - Digital Design  
Lecture 12 - Combinational Logic &  
Arithmetic Circuits Part 2

October 3, 2002  
John Wawrzynek

# Carry Look-ahead Adders

- In general, for n-bit addition best we can achieve is delay  $\propto \log(n)$
- How do we arrange this? (think trees)
- First, reformulate basic adder stage:


a	b	$c_i$	$c_{i+1}$	s	
0	0	0	0	0	carry "kill"
0	0	1	0	1	$k_i = a_i' b_i'$
0	1	0	0	1	
0	1	1	1	0	carry "propagate"
1	0	0	0	1	$p_i = a_i \oplus b_i$
1	0	1	1	0	
1	1	0	1	0	carry "generate"
1	1	1	1	1	$g_i = a_i b_i$

$$c_{i+1} = g_i + p_i c_i$$

$$s_i = p_i \oplus c_i$$
 
# Carry Look-ahead Adders

- “Group” propagate and generate signals:



- $P$  true if the group as a whole propagates a carry to  $c_{out}$
- $G$  true if the group as a whole generates a carry
- Group  $P$  and  $G$  can be generated hierarchically.

$$C_{out} = G + PC_{in}$$