

EECS 150 - Components and Design Techniques for Digital Systems

Lec 02 – CMOS Technology 9-2-04

David Culler

Electrical Engineering and Computer Sciences
University of California, Berkeley

<http://www.eecs.berkeley.edu/~culler>
<http://www-inst.eecs.berkeley.edu/~cs160>

1

Outline

- Summary of last time
- Overview of Physical Implementations
- CMOS devices
- Announcements/Break
- CMOS transistor circuits
 - basic logic gates
 - tri-state buffers
 - flip-flops
 - » flip-flop timing basics
 - » example use
 - » circuits

2

We will learn in CS 150 ...

- Language of logic design
 - Logic optimization, state, timing, CAD tools
- Concept of state in digital systems
 - Analogous to variables and program counters in software systems
- Hardware system building
 - Datapath + control = digital systems
- Hardware system design methodology
 - Hardware description languages: Verilog
 - Tools to simulate design behavior: scopes + function (inputs)
 - Logic compilers synthesize hardware blocks of our designs
 - Mapping onto programmable hardware (code generation)
- Contrast with software design
 - Both map specifications to physical devices
 - Both must be flawless...the price we pay for using discrete math

3


What is logic design?

- What is design?
 - Given problem spec, solve it with available components
 - While meeting criteria for size, cost, power, beauty, elegance, etc.
- What is logic design?
 - Choose digital logic components to perform specified control, data manipulation, or communication function and their interconnection
 - Which logic components to choose?
Many implementation technologies (fixed-function components, programmable devices, individual transistors on a chip, etc.)
 - Design optimized/transformed to meet design constraints

4

What is digital hardware?

- Devices that sense/control wires carrying digital values (physical quantity interpreted as "0" or "1")
 - Digital logic: voltage < 0.8v is "0", > 2.0v is "1"
 - Pair of wires where "0"/"1" distinguished by which has higher voltage (differential)
 - Magnetic orientation signifies "0" or "1"
- Primitive digital hardware devices
 - Logic computation devices (sense and drive)
 - » two wires both "1" - make another be "1" (AND)
 - » at least one of two wires "1" - make another be "1" (OR)
 - » a wire "1" - then make another be "0" (NOT)
 - Memory devices (store)
 - » store a value
 - » recall a value previously stored

 

5


Overview of Physical Implementations

The stuff out of which we make systems.

- Integrated Circuits (ICs)
 - Combinational logic circuits, memory elements, analog interfaces.
- Printed Circuits (PC) boards
 - substrate for ICs and interconnection, distribution of CLK, Vdd, and GND signals, heat dissipation.
- Power Supplies
 - Converts line AC voltage to regulated DC low voltage levels.
- Chassis (rack, card cage, ...)
- holds boards, power supply, provides physical interface to user or other systems.
- Connectors and Cables.


6

Integrated Circuits



- Primarily Crystalline Silicon
- 1cm - 25mm on a side
- 100 - 200M transistors
- (25 - 50M "logic gates")
- 3 - 10 conductive layers
- 2002 - feature size = 0.13um = 0.13 x 10⁻⁶ m
- "CMOS" most common - complementary metal oxide semiconductor

Chip in Package



- Package provides:
 - spreading of chip-level signal paths to board-level
 - heat dissipation.
- Ceramic or plastic with gold wires.

Printed Circuit Boards




- fiberglass or ceramic
- 1-20 conductive layers
- 1-20in on a side
- IC packages are soldered down.

Multichip Modules (MCMs)


- Multiple chips directly connected to a substrate. (silicon, ceramic, plastic, fiberglass) without chip packages.

What Complementary about CMOS?

- Complementary devices work in pairs

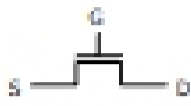


n-channel
 open when voltage at G is low
 closes when:
 voltage(G) > voltage(S) + α




p-channel
 closed when voltage at G is low
 opens when:
 voltage(G) < voltage(S) - α

Transistor-level Logic Circuits (inv)

- Inverter (NOT gate):

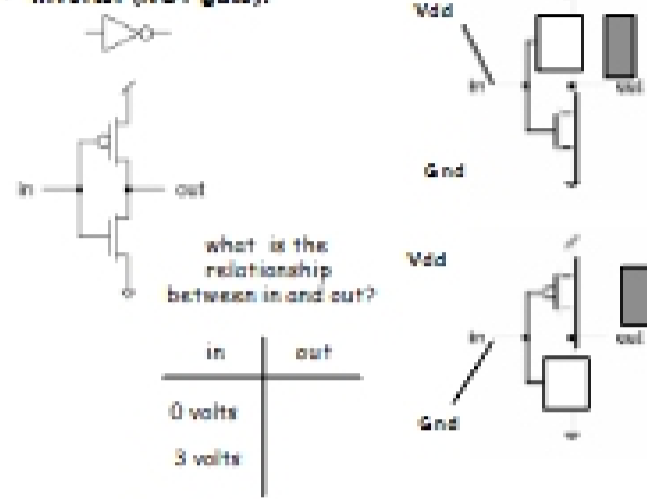

Logical Values

 

- Threshold**
 - Logical 1 (true) : $V > V_{dd} - V_{th}$
 - Logical 0 (false) : $V < V_{th}$


in	out	not(out, in)
F	T	
T	F	

- Noise margin?

Big idea: Self-restoring logic

- CMOS logic gates are self-restoring
 - Even if the inputs are imperfect, switching time is fast and outputs go rail to rail
 - Doesn't matter how many you cascade
 - Although propagation delay increases
- Manage fan-out to ensure sharp and complete transition

Element of Time

 

- Logical change is not instantaneous
- Broader digital design methodology has to make it appear as such
 - Clocking, delay estimation, glitch avoidance

Announcements

If you are on the wait list and would like to get into the class you must:

- Turn in an appeal for on third floor Soda
- Attend lectures and do the homework, the first two weeks.
- In the second week of classes, go to the lab section in which you wish to enroll. Give the TA your name and student ID.
- Later, we will process the waitlist based on these requests, and lab section openings.