

f) Energy Relationship

$$w(t) = \int_{-\infty}^t v(\tau) i(\tau) d\tau$$

$$= \int_{-\infty}^t v(\tau) C \frac{dv}{d\tau} d\tau \rightarrow = C \int_{-\infty}^t v(\tau) dv \rightarrow = C \left( \frac{v^2}{2} \right) \Big|_{-\infty}^t$$

$$w(t) = \frac{1}{2} C v^2(t)$$

Passive element!

Terminal Conditions

$$i(t) = C \frac{dv}{dt}$$


$$v(t) = \frac{1}{C} \int_{t_0}^t i(\tau) d\tau + v(t_0)$$

$$w_c(t) = \frac{1}{2} C v^2(t)$$

$$Q = CV$$

Equivalent Capacitance

series:

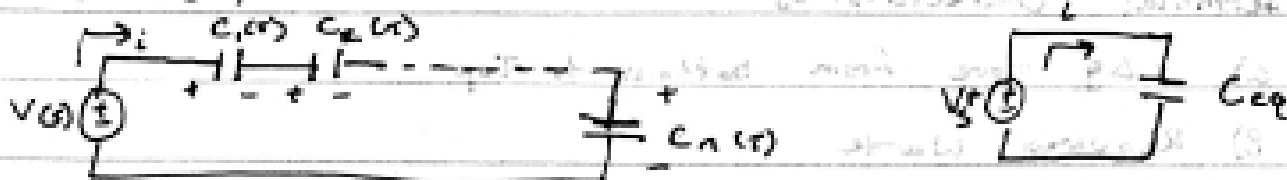

$$v(t) = v_1(t) + v_2(t) + \dots + v_n(t)$$

$$v(t) = \frac{1}{C} \int_{t_0}^t i(\tau) d\tau + v(t_0) + \int_{t_0}^t \frac{1}{C_n} i(\tau) d\tau + v_n(t_0)$$

$$v(t) = \int_{t_0}^t i(\tau) d\tau \left[ \frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_n} \right] + (v_1 + v_2 + \dots + v_n)$$

$$v(t) = \frac{1}{C_{eq}} \int_{t_0}^t i(\tau) d\tau + v(t_0)$$

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_n}$$


$$C_{eq} = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_n}}$$



Capacitance in Parallel


$$C_{eq} = C_1 + C_2 + C_3 + \dots + C_n$$
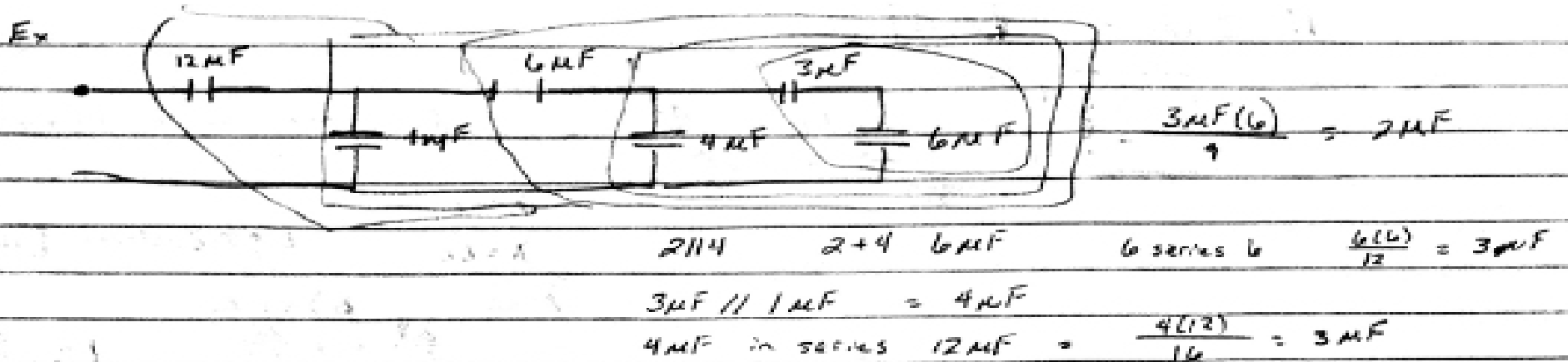
$$1F = \frac{1 \text{ coulomb}}{1 \text{ volt}}$$



A  $10 \mu F$  capacitor has  $v(0) = 10V$  the current through the capacitor is given by:

$$i(t) \text{ mA}$$

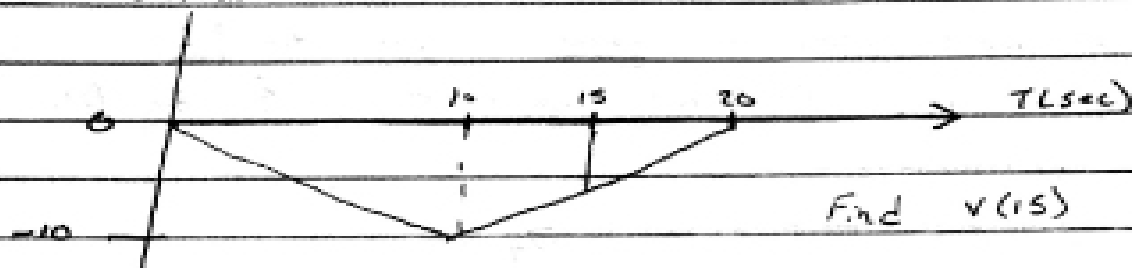

$$v(t) = \frac{1}{C} \int_{t_0}^t i(\tau) d\tau + v(t_0)$$

$$-7 \text{ } 0 \leq t \leq 10 \text{ msec}$$

$$i = -20 \times 10^{-3} \quad 10 \text{ msec} \leq t \leq 20 \text{ msec}$$

$$v(t) = \frac{1}{10 \times 10^{-6}} \left[ \int_0^{10 \times 10^{-3}} -7 d\tau + \int_{10 \times 10^{-3}}^{15 \times 10^{-3}} (t - 20 \times 10^{-3}) d\tau + v(0) \right]$$

$$= \frac{1}{10 \times 10^{-6}} \left( -\frac{\tau^2}{2} \Big|_0^{10 \times 10^{-3}} + \left( \frac{\tau^2}{2} - 20 \times 10^{-3} \tau \right) \Big|_{10 \times 10^{-3}}^{15 \times 10^{-3}} \right) + 10V$$

$$= \frac{1}{10 \times 10^{-6}} \left( -50 \times 10^{-6} + \frac{125 \times 10^{-6}}{2} - 20 \times 10^{-3} (5 \times 10^{-3}) \right) + 10V$$

$$= \frac{1}{10} (-50 + 62.5 - 100) + 10$$

$$= -9.75 + 10 = \boxed{+1.25V}$$


or

$$\frac{1}{10 \times 10^{-6}} \left( \frac{1}{2} (10 \times 10^{-3}) (-10 \times 10^{-3}) + \left( \frac{-15 \times 10^{-3}}{2} \right) (5 \times 10^{-3}) \right) + 10$$

$$\frac{1}{10} (-50 - 37.5) + 10$$

$$-9.75 + 10 = \boxed{1.25V}$$

## B. Inductor [coil]

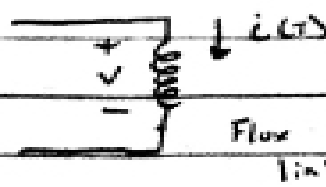

Flux,  $\Phi$   
Flux linkage  $\rightarrow \lambda = N\Phi$

$\Phi$  increase as  $i$  increase

$$\lambda \sim i$$

$$\lambda = Li$$

$L$ : Inductance [Henry] H

$$\Delta \lambda = L \Delta i$$

$$\frac{\Delta \lambda}{\Delta t} = L \frac{\Delta i}{\Delta t}$$

$$\lim_{\Delta t \rightarrow 0} \frac{\Delta \lambda}{\Delta t} = L \lim_{\Delta t \rightarrow 0} \frac{\Delta i}{\Delta t}$$


$$\frac{d\lambda}{dt} = L \frac{di}{dt} \Rightarrow v = L \frac{di}{dt}$$

Faraday's law of Electromagnetic induction:  $\frac{d\lambda}{dt} = v$

$$v = L \frac{di}{dt} \quad i = C \frac{dv}{dt}$$

An inductor acts like a short circuit to DC

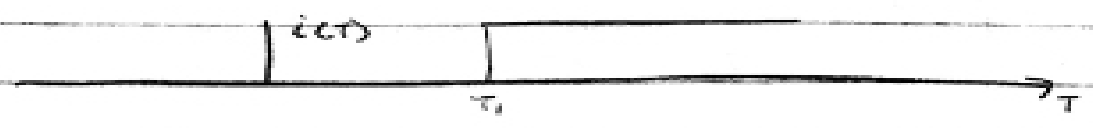A capacitor acts like an open circuit to DC



The current through an inductor cannot change instantaneously

$$\frac{di}{dt} = \frac{1}{L} v$$

$$\int_{i(t_0)}^{i(t)} di = \frac{1}{L} \int_{t_0}^t v(t) dt \rightarrow i(t) - i(t_0) = \frac{1}{L} \int_{t_0}^t v(t) dt$$


$$i(t) = \frac{1}{L} \int_{t_0}^t v(t) dt + i(t_0)$$

Energy Relationship.

$$w(t) = \int_{-\infty}^{t} v(t) i(t) dt = \int_{-\infty}^{t} L \frac{di}{dt} i(t) dt$$

$$w(t) = L \frac{i^2}{2} = \frac{1}{2} L i^2(t) \geq 0 \quad \text{Passive element.}$$

### Series Inductors

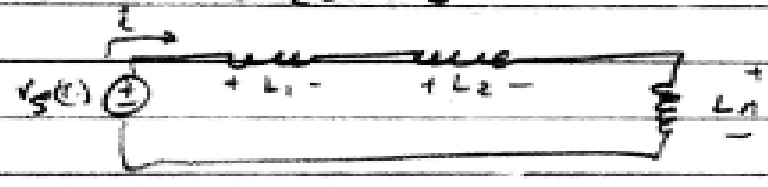

$$\text{KVL: } v_s(t) = v_1 + v_2 + \dots + v_n$$

$$= L_1 \frac{di}{dt} + L_2 \frac{di}{dt} + \dots + L_n \frac{di}{dt}$$

$$= \frac{di}{dt} [L_1 + L_2 + L_n]$$



series  $L_{eq} = L_1 + L_2 + L_n$

Parallel  $L_{eq} = \frac{1}{\frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_n}}$

Act just like Resistors