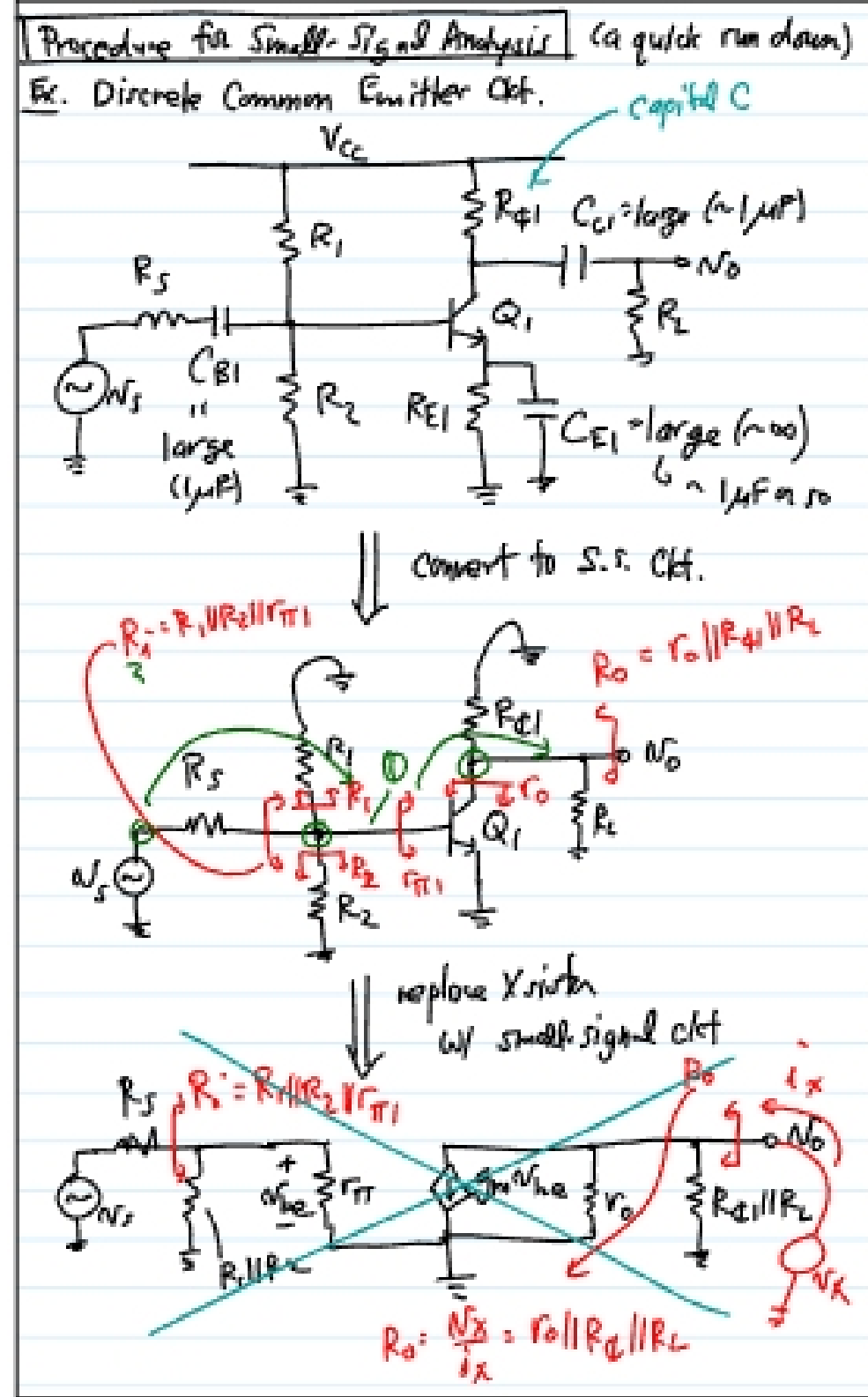


• Today:


- ↳ Inspection analysis for input resistance, output resistance, and gain
- But first: Logistics
- Passed out sign up sheet for discussion sections
- Problem with the Wednesday section: 2:30-3:30 p.m. might not work
 - ↳ Possible to switch to Thursday, 2-3?
- Some people cannot make the Monday 5-7 lab
 - ↳ Solution: whenever the lab is such that instruments in the lab need to be used, the lab will be 4-6 on Monday; otherwise, it will be 5-7



Procedure:

- ① Find the DC operating pt. → get voltages & currents at all nodes & branches, respectively
- ② Determine S.S. parameters for devices in the signal path (e.g., g_m , r_{π} , r_o , ...)
- ③ Convert the full ckt. to the S.S. ckt.
⇒ zero out DC sources
= short out large capacitor
- ④a) If needed, replace Xistor w/ its small-signal ckt.
→ this should NOT be needed often
→ when is it needed? → generally it covers where there is feedback!
- ④b) Analyze by inspection based on prior S.S. analysis experience! → this should be the case 99% of the time
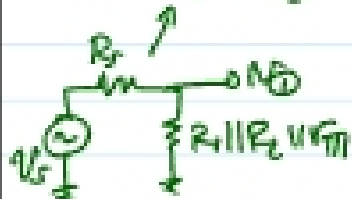
$$A_v = \frac{v_{O1}}{v_i} \cdot \frac{v_{O2}}{v_{O1}} = - \left(\frac{R_1 \parallel R_2 \parallel r_{\pi 1}}{R_1 \parallel R_2 \parallel r_{\pi 1} + R_S} \right) g_{m1} (R_{E1} \parallel R_{E2})$$




$$\frac{v_{O1}}{v_i} = \frac{R_1 \parallel R_2 \parallel r_{\pi 1}}{R_1 \parallel R_2 \parallel r_{\pi 1} + R_S}$$

$$\frac{v_{O2}}{v_{O1}} = -g_{m1} R_{O1} = -g_{m1} (R_{O1} \parallel R_{E1} \parallel R_{E2}) \approx -g_{m1} (R_{O1} \parallel R_{E1})$$

\uparrow g_{m1} \uparrow $R_{O1} = R_{E1} \parallel R_{E2} \parallel r_o$

Ex. Common-Emitter:

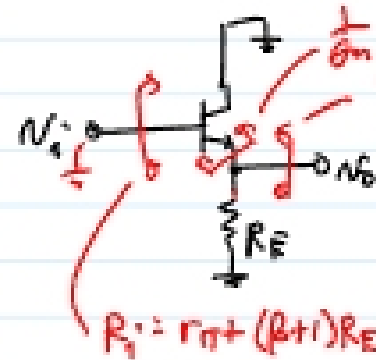


$$R_i = r_{\pi} + (\beta + 1)R_E$$

$$R_o = \frac{1}{g_m} \parallel R_E$$

$$\frac{v_{O2}}{v_{O1}} = \frac{R_E}{r_o + R_E} = \frac{(\beta + 1)R_E}{r_{\pi} + (\beta + 1)R_E}$$

$$\frac{1}{g_m} = \frac{V_T}{I_C} = r_e$$

Ex. Common-Base:

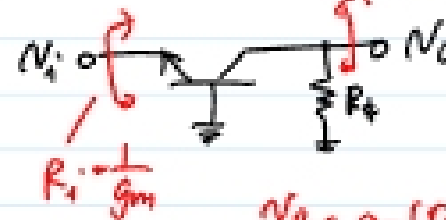


$$R_o = r_o \parallel R_L$$

$$R_i = \frac{1}{g_m}$$

$$\frac{v_{O2}}{v_{O1}} = g_m (r_o \parallel R_L) \approx g_m R_L$$

⇒ so far, we've been talking about "midband" analysis

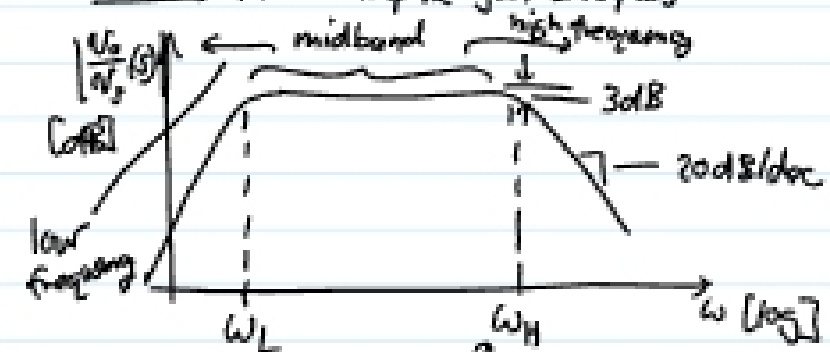
→ Bode Plot: (for the amp we just analyzed)



we want this!
→ use OCTC (open ckt time constant) analysis

Useful Inspection Formulas

The General Case (Midband)

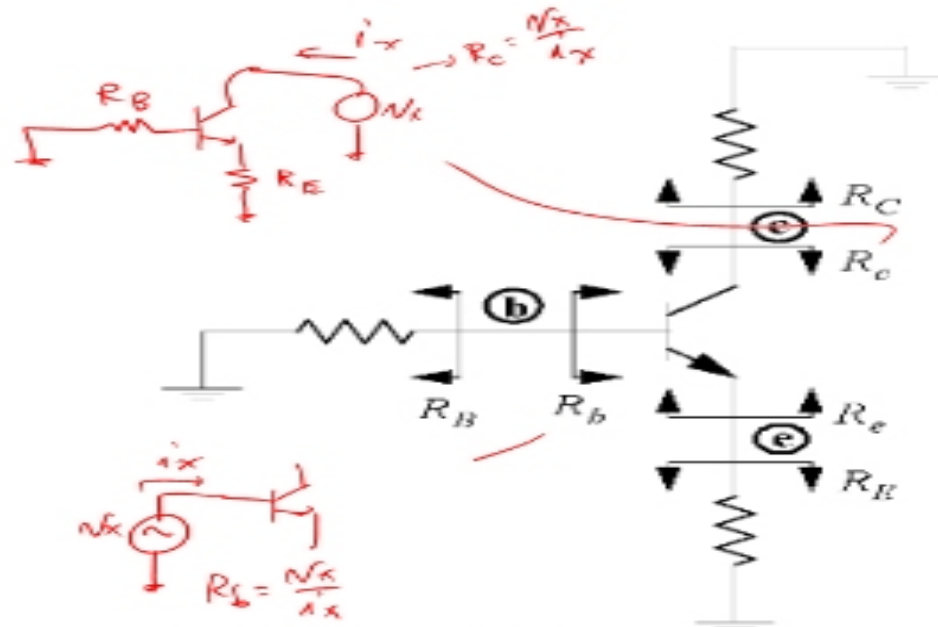

Node Resistances:

$$R_{\text{C}} = R_C \parallel R_c$$

$$R_{\text{E}} = R_E \parallel R_e$$

$$R_{\text{B}} = R_B \parallel R_b$$

$$R_b = (r_e + R_E)(\beta + 1) = r_{\pi} + (\beta + 1)R_E$$

$$R_e = \frac{r_{\pi} + R_B}{\beta + 1} \cong \frac{1}{g_m} + \frac{R_B}{\beta + 1}$$

$$R_c = r_o \left[1 + \frac{g_m R_E}{1 + (R_B/r_{\pi})} \right]$$

Base-to-Collector Gain:

$$\frac{v_c}{v_b} = -G_m R_{\text{C}} \quad G_m = \frac{g_m}{1 + g_m R_E}$$


Emitter-to-Collector Gain:

$$\frac{v_c}{v_e} = -G_m R_{\text{C}} \quad G_m = -\left(\frac{r_{\pi}}{r_{\pi} + R_B} \right) g_m$$

Base-to-Emitter Gain:

$$\frac{v_e}{v_b} = \frac{R_E \parallel r_o}{R_E \parallel r_o + r_e}$$

High Frequency Analysis

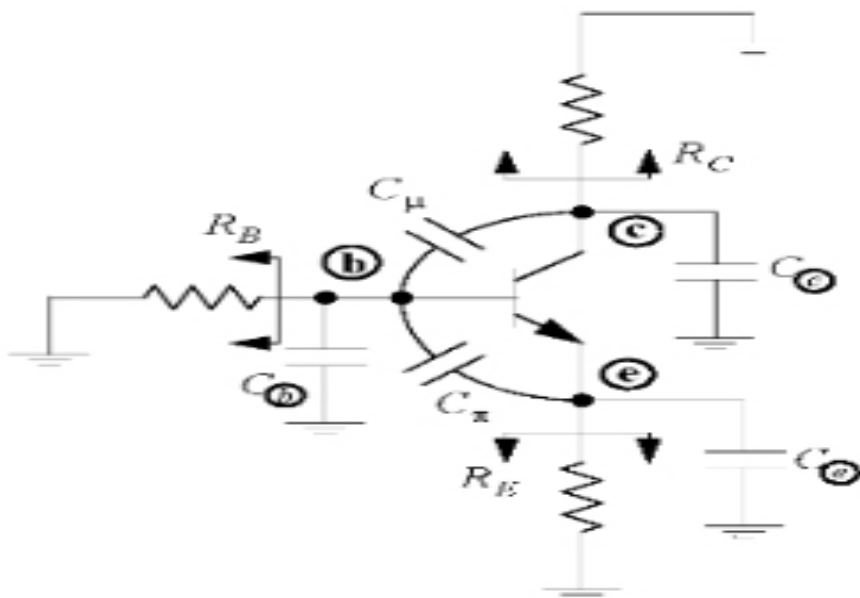

$$\omega_H = \frac{1}{\tau_b + \tau_c + \tau_e + \tau_{\mu o} + \tau_{\pi o}}$$

$$\tau_b = C_{\text{B}} R_{\text{B}} \quad \tau_{\pi o} = C_{\pi} R_{\pi o}$$

$$\tau_c = C_{\text{C}} R_{\text{C}} \quad \tau_{\mu o} = C_{\mu} R_{\mu o}$$

$$\tau_e = C_{\text{E}} R_{\text{E}}$$

$$R_{\pi o} = r_{\pi} \parallel \frac{R_B + R_E}{1 + g_m R_E}$$

$$R_{\mu o} = R_{\text{B}} + R_{\text{C}} + G_m R_{\text{C}} R_{\text{B}}$$