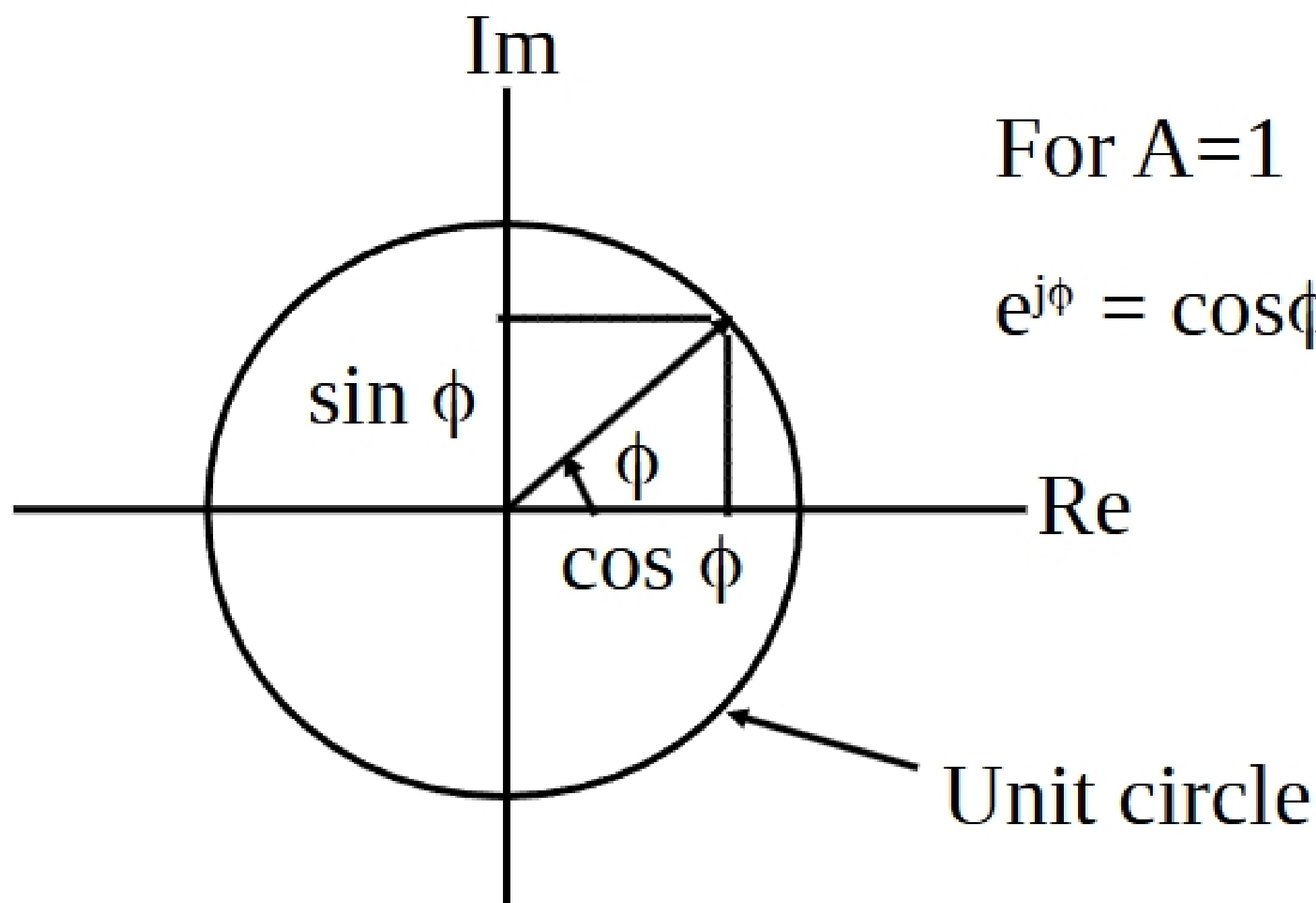


Phasors

Phasors: Complex number representations of sinusoidal signals at fixed frequency, ω .

$$\text{Complex number} = Ae^{j\omega t + \phi} = A(e^{j\omega t} e^{j\phi})$$

$$\text{But if } \omega \text{ is constant: } Ae^{j\phi} \equiv A \angle \phi$$



$$|e^{j\phi}| = e^{j\phi} e^{-j\phi} = \cos^2 \phi + \sin^2 \phi = 1$$

$A \angle \phi$ completely specifies the quantity
 $A \cos(\omega t + \phi)$ for known ω .

Phasor voltage : $\underline{V} = V_m \angle \phi$
 Phasor current: $\underline{I} = I_m \angle \phi$ } Denoted by
 bold type in
 text.

$v(t) = -15 \sin(\omega t - 60^\circ)$
 $v(t) = 15 \cos(\omega t + 30^\circ)$ } $\underline{V} = 15 \angle 30^\circ$
 $i(t) = 25 \cos(\omega t + 45^\circ)$ } $\underline{I} = 25 \angle 45^\circ$


Ohm's Law Relationships for SSS

Exists for resistors, inductors & capacitors.

General form: $\underline{V} = z(j\omega) \underline{I}$

$z(j\omega)$ - impedance (units: ohms)

Impedance concept for resistors

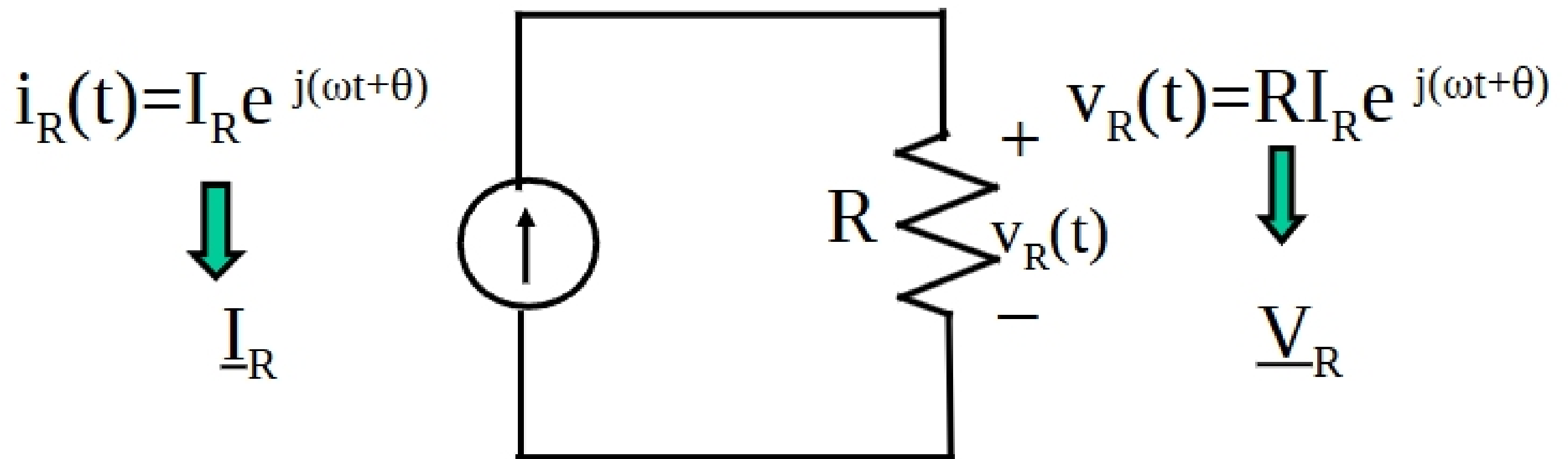

$$\underline{V}_R = z_R(j\omega) \underline{I}_R \quad \boxed{z_R(j\omega) = R}$$

$$\underline{V}_R = R \underline{I}_R$$

Resistor impedance is independent of frequency

Impedance concept for inductors

