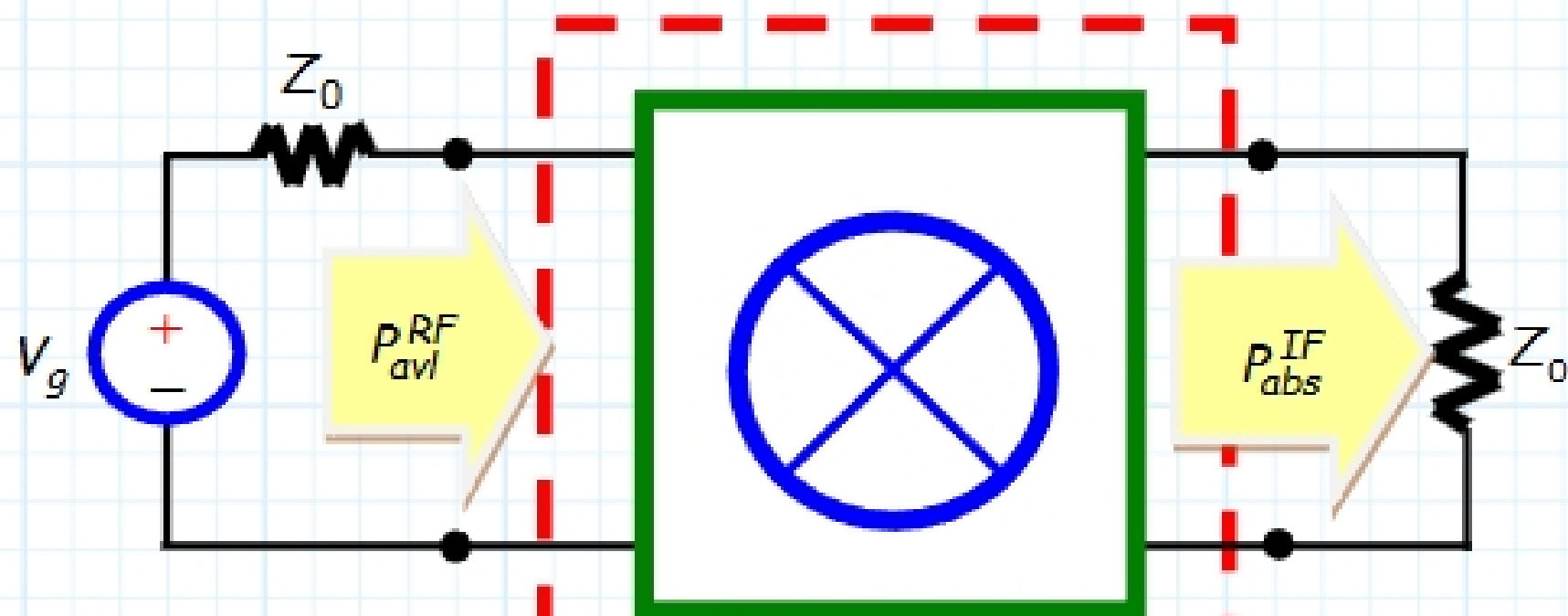


# Mixer Conversion Loss



Again, a mixer/LO pair can be considered a **two-port device**.

Now, let's consider the "gain" of this 2-port device, i.e.:

$$\text{Mixer "Gain"} = \frac{P_{out}}{P_{in}} = \frac{P_{abs}^{IF}}{P_{avl}^{RF}}$$


## Available power

If the RF port of the mixer is **reasonably matched**, then total voltage is approximately equal the **incident voltage** on the RF port:

$$v_{RF}(t) = v_{RF}^+(t) = A_{RF} \cos[\omega_{RF} t + \varphi_{RF}]$$

And so, the **available power** of the "matched" source is:

$$P_{avl}^{RF} = \frac{|V_g|^2}{8Z_0} = \frac{A_{RF}^2}{2Z_0}$$

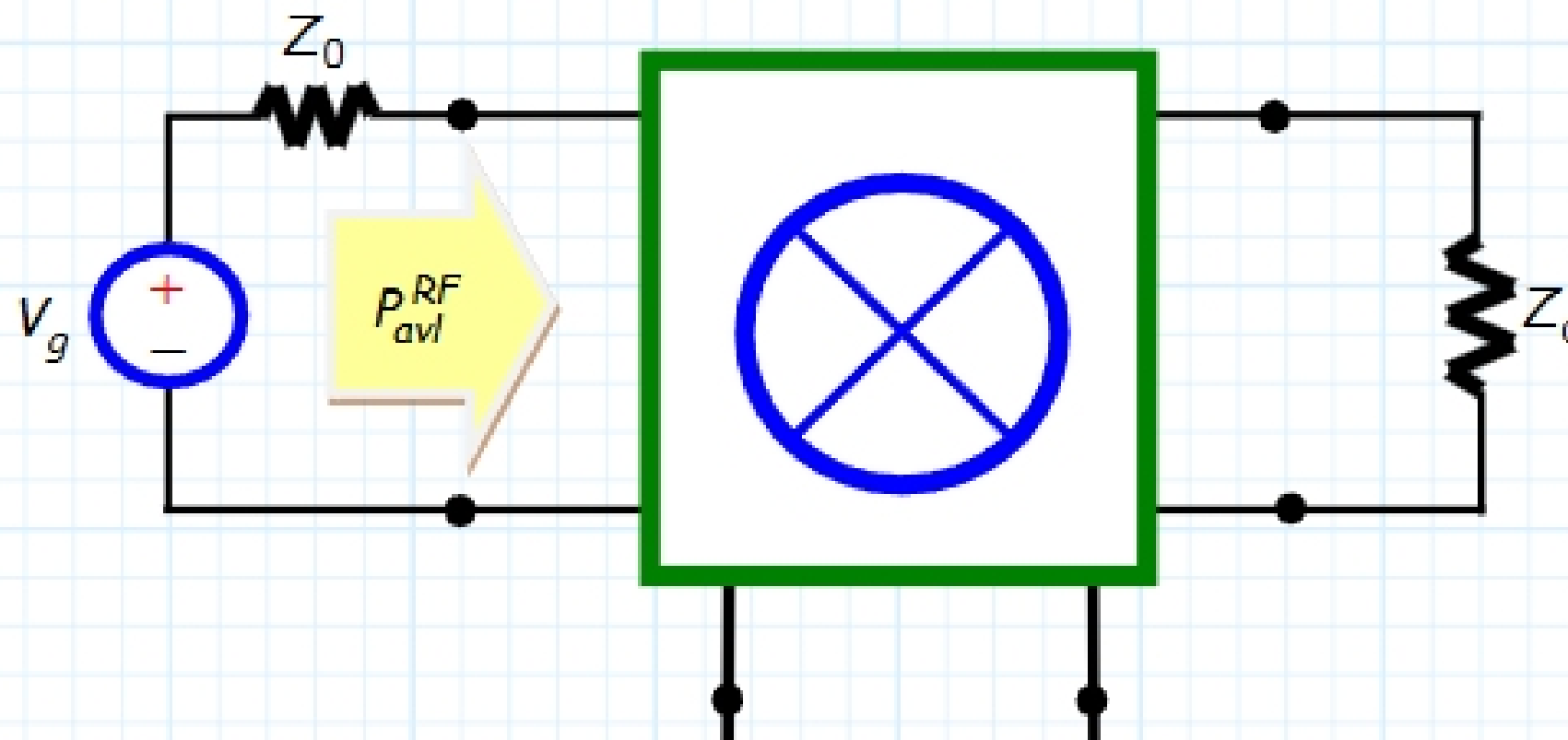

## Absorbed power

Likewise, the **total** down-converted signal voltage at the IF port is equal to the **incident voltage** on the "matched" load:

$$v_{IF}(t) = v_{IF}^+(t) = A_{RF} \frac{2}{\pi} \cos[(\omega_{RF} - \omega_{LO})t + \varphi_{RF}]$$

And so the **power absorbed** by the "matched" load is:

$$P_{abs}^{IF} = \frac{A_{RF}^2}{2Z_0} \left(\frac{2}{\pi}\right)^2 = P_{avl}^{RF} \left(\frac{2}{\pi}\right)^2$$

