

Matched, Lossless, Reciprocal Devices

As we discussed earlier, a device can be **lossless** or **reciprocal**. In addition, we can likewise classify it as being **matched**.

Let's examine **each** of these three characteristics, and how they relate to the **scattering matrix**.

Matched

A matched device is another way of saying that the **input impedance** at each port is **equal to Z_0** when **all other** ports are terminated in matched loads. As a result, the **reflection coefficient** of each port is **zero**—no signal will be come out of a port if a signal is incident on that port (but **only** that port!).

In other words, we want:

$$V_m^- = S_{mm} V_m^+ = 0 \quad \text{for all } m$$

a result that occurs when:

$$S_{mm} = 0 \quad \text{for all } m \text{ if matched}$$

We find therefore that a matched device will exhibit a scattering matrix where all **diagonal elements are zero**.

Therefore:

$$\mathcal{S} = \begin{bmatrix} 0 & 0.1 & j0.2 \\ 0.1 & 0 & 0.3 \\ j0.2 & 0.3 & 0 \end{bmatrix}$$

is an example of a scattering matrix for a **matched**, three port device.

Lossless

For a lossless device, all of the power that delivered to each device port must eventually find its way **out!**

In other words, power is not **absorbed** by the network—no power to be **converted to heat!**

Recall the **power incident** on some port m is related to the amplitude of the **incident wave** (V_{0m}^+) as:

$$P_m^+ = \frac{|V_{0m}^+|^2}{2Z_0}$$

While power of the **wave exiting** the port is:

$$P_m^- = \frac{|V_{0m}^-|^2}{2Z_0}$$

Thus, the power **delivered** to (absorbed by) that port is the **difference** of the two:

$$\Delta P_m = P_m^+ - P_m^- = \frac{|V_{0m}^+|^2}{2Z_0} - \frac{|V_{0m}^-|^2}{2Z_0}$$

Thus, the **total power incident** on an N -port device is:

$$P^+ = \sum_{m=1}^N P_m^+ = \frac{1}{2Z_0} \sum_{m=1}^N |V_{0m}^+|^2$$

Note that:

$$\sum_{m=1}^N |V_{0m}^+|^2 = (\mathbf{V}^+)^H \mathbf{V}^+$$

where operator H indicates the **conjugate transpose** (i.e., Hermetian transpose) operation, so that $(\mathbf{V}^+)^H \mathbf{V}^+$ is the **inner product** (i.e., dot product, or scalar product) of complex vector \mathbf{V}^+ with itself.

Thus, we can write the **total power incident** on the device as:

$$P^+ = \frac{1}{2Z_0} \sum_{m=1}^N |V_{0m}^+|^2 = \frac{(\mathbf{V}^+)^H \mathbf{V}^+}{2Z_0}$$

Similarly, we can express the **total power of the waves exiting** our M -port network to be:

$$P^- = \frac{1}{2Z_0} \sum_{m=1}^N |V_{0m}^-|^2 = \frac{(\mathbf{V}^-)^H \mathbf{V}^-}{2Z_0}$$