



# Lumped-Element Modeling

- ☑ Last lecture
  - ↗ Conjugate power variables
  - ↗ Equivalent circuit modeling
  - ↗ One-port elements
    - Ideal Flow Source
    - Ideal Effort Source
    - Generalized Resistor
- Today:
  - ↗ One-port elements
    - Generalized Capacitor
    - Generalized Inertance
    - Co-energy
  - ↗ Kirchhoff's Laws
  - ↗ Example
  - ↗ Laplace Transform

📖 Reading: Senturia, pp. 110-118.

## ■ Ideal Capacitor, or Compliance: “C”

↗ Stores potential energy associated with a displacement.

$$e = \Phi(q) \quad \text{or} \quad q = \Phi^{-1}(e)$$

↗ When a compliance has a non-zero effort (non-zero displacement), it is storing potential energy.

$$W(q_1) = \int_0^{q_1} e \, dq = \int_0^{q_1} \Phi(q) \, dq \equiv \text{stored POTENTIAL ENERGY}$$


**PE**

$$W^*(e_1) = \int_0^{e_1} q \, de = \int_0^{e_1} \Phi^{-1}(e) \, de \equiv \text{stored POTENTIAL CO-ENERGY}$$
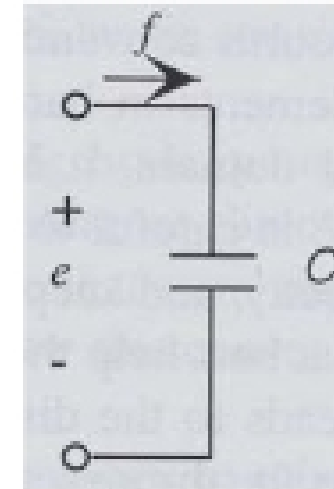
# Generalized Capacitor


- Ideal Compliance: "C"

$$e = \frac{1}{C} \int f dt \text{ or } e(j\omega) = \frac{1}{j\omega C} f(j\omega)$$



Ref. Senturia, p. 109.
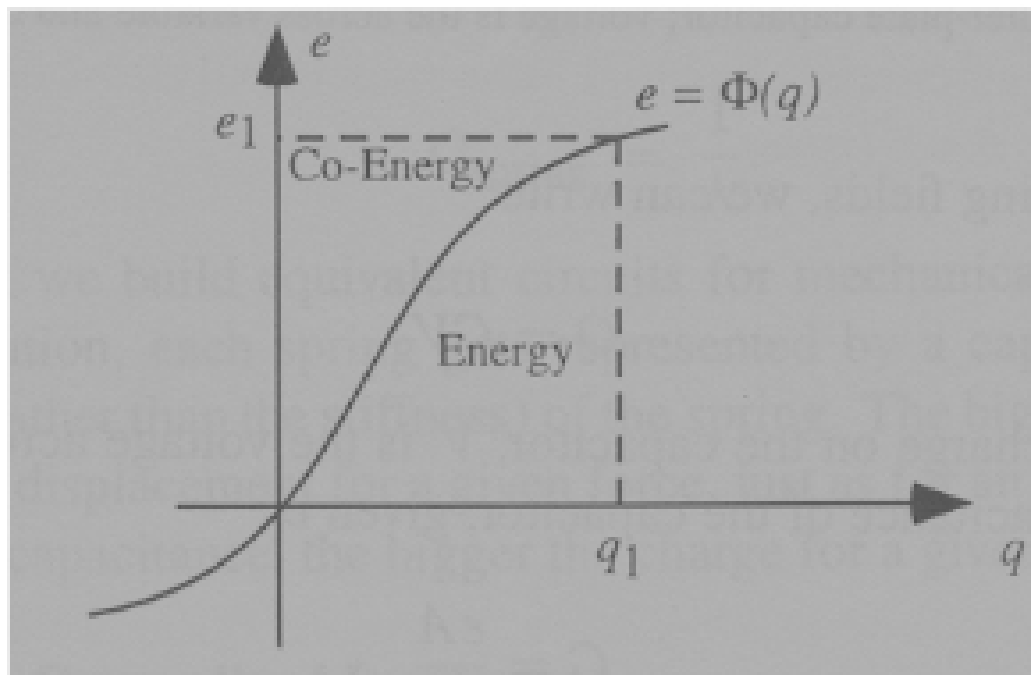
$$e(s) = Z_C(s) f(s) \quad Z_C(s) = \frac{1}{sC} \quad \text{Complex Impedance}$$



Ref. Senturia, p. 110.

$$W(q_1) = \int_0^{q_1} \Phi(q) dq$$

$$W^*(e_1) = \int_0^{e_1} \Phi^{-1}(e) de$$

If  $\Phi$  is linear,

then  $W(q_1) = W^*(e_1)$