

The Scattering Matrix

At “low” frequencies, we can completely characterize a **linear** device or network using an **impedance** matrix, which relates the currents and voltages at **each** device terminal to the currents and voltages at **all** other terminals.


But, at microwave frequencies, it is **difficult** to measure total currents and voltages!



- * Instead, we can measure the **magnitude** and **phase** of each of the two transmission line **waves** $V^+(z)$ and $V^-(z)$.
- * In other words, we can determine the relationship between the incident and reflected wave at **each** device terminal to the incident and reflected waves at **all** other terminals.

These relationships are completely represented by the **scattering matrix**. It **completely** describes the behavior of a linear, multi-port device at a **given frequency** ω , and a given line impedance Z_0 .

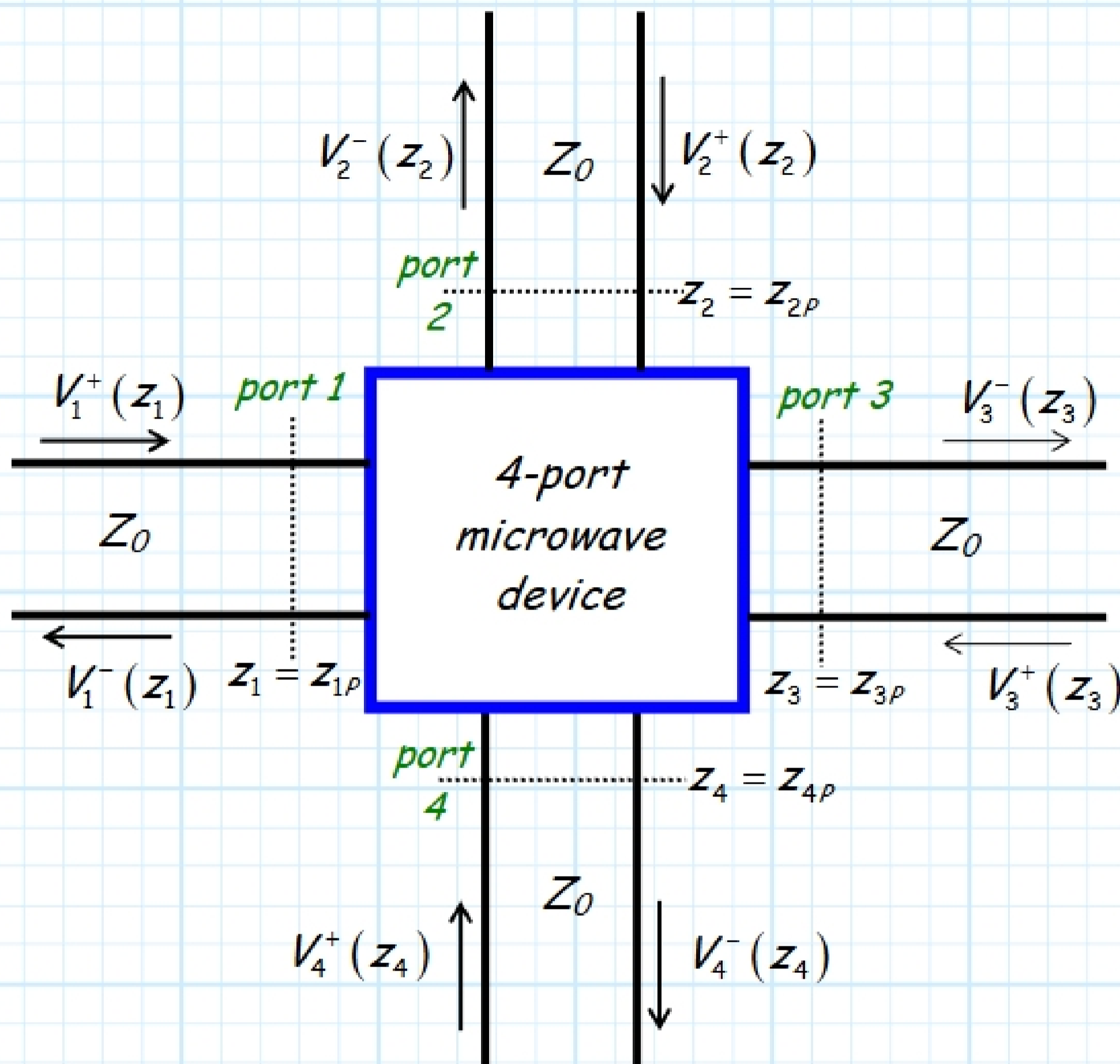
Consider now the 4-port microwave device shown below:



Note that we have now characterized transmission line activity in terms of incident and "reflected" waves. Note the negative going "reflected" waves can be viewed as the waves **exiting** the multi-port network or device.


→ Viewing transmission line activity this way, we can fully characterize a multi-port device by its **scattering parameters!**

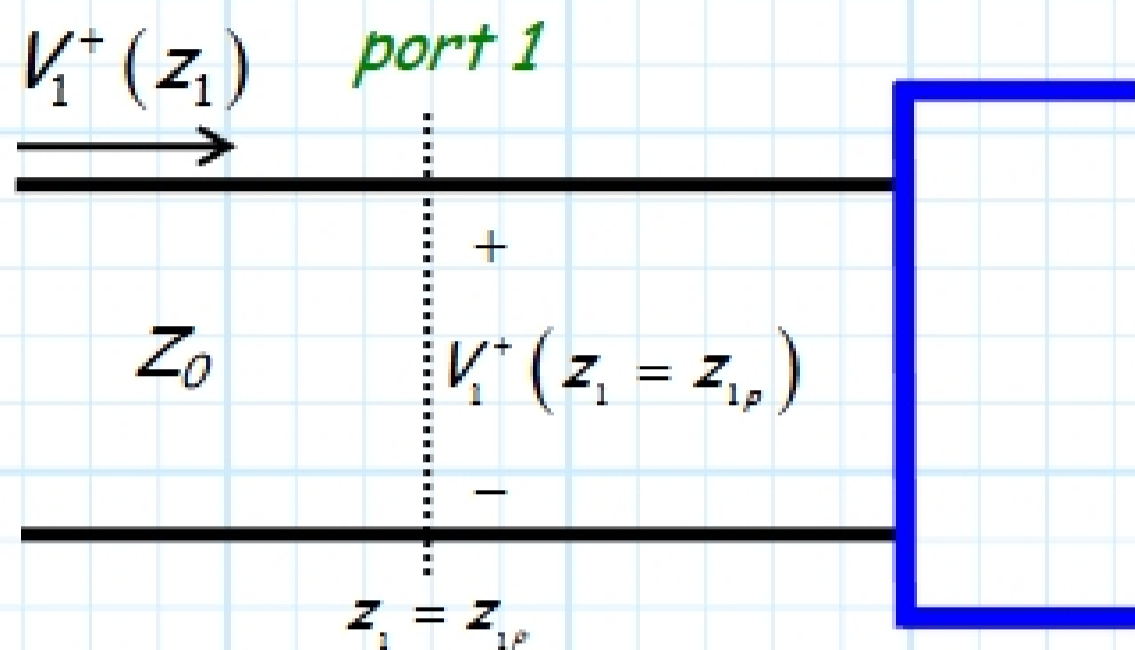Say there exists an **incident wave on port 1** (i.e., $V_1^+(z_1) \neq 0$), while the incident waves on all other ports are known to be **zero** (i.e., $V_2^+(z_2) = V_3^+(z_3) = V_4^+(z_4) = 0$).



Say we measure/determine the voltage of the wave flowing **into port 1**, at the port 1 plane (i.e., determine $V_1^+(z_1 = z_{1p})$).

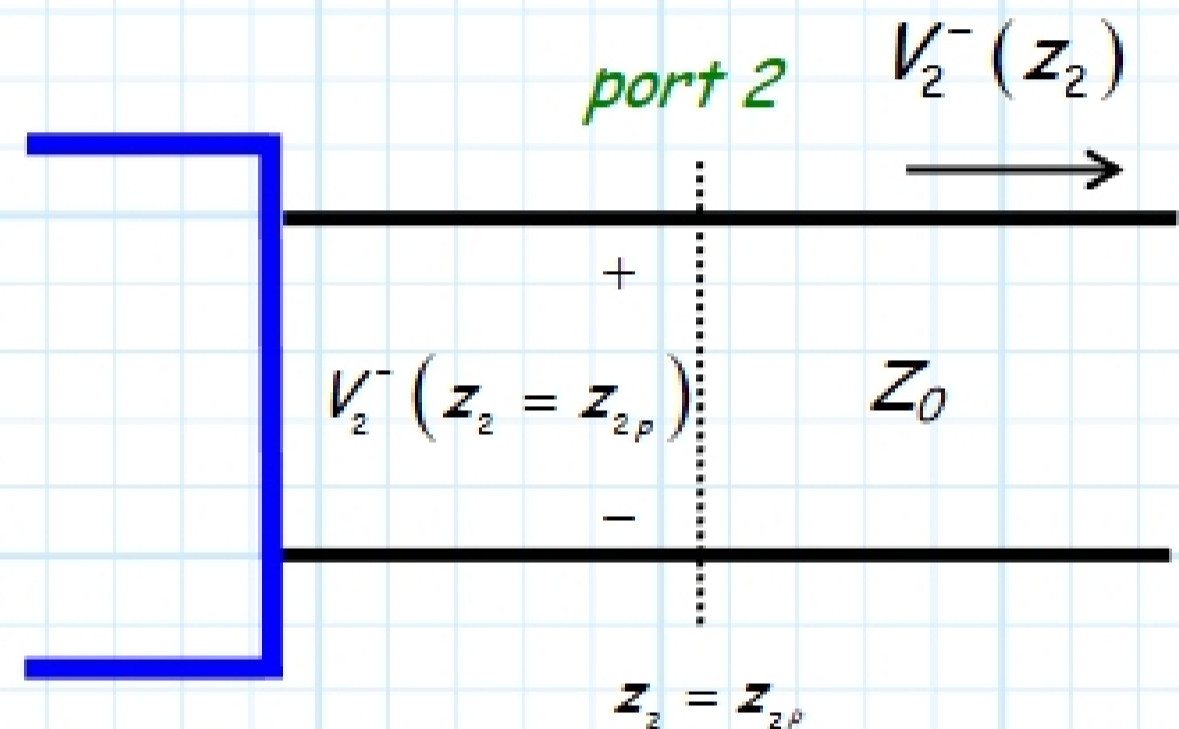Say we then measure/determine the voltage of the wave flowing **out of port 2**, at the port 2 plane (i.e., determine $V_2^-(z_2 = z_{2p})$).



The complex ratio between $V_1^+(z_1 = z_{1p})$ and $V_2^-(z_2 = z_{2p})$ is known as the **scattering parameter S_{21}** :

$$S_{21} = \frac{V_2^-(z_2 = z_{2p})}{V_1^+(z_1 = z_{1p})} = \frac{V_{02}^- e^{+j\beta z_{2p}}}{V_{01}^+ e^{-j\beta z_{1p}}} = \frac{V_{02}^-}{V_{01}^+} e^{+j\beta(z_{2p} + z_{1p})}$$

Likewise, the scattering parameters S_{31} and S_{41} are:

$$S_{31} = \frac{V_3^-(z_3 = z_{3p})}{V_1^+(z_1 = z_{1p})} \quad \text{and} \quad S_{41} = \frac{V_4^-(z_4 = z_{4p})}{V_1^+(z_1 = z_{1p})}$$