

Lecture 16

The pn Junction Diode (III)

Outline

- Small-signal equivalent circuit model
- Carrier charge storage
 - Diffusion capacitance


Reading Assignment:

Howe and Sodini; Chapter 6, Sections 6.4 - 6.5


I-V Characteristics

Diode Current equation:
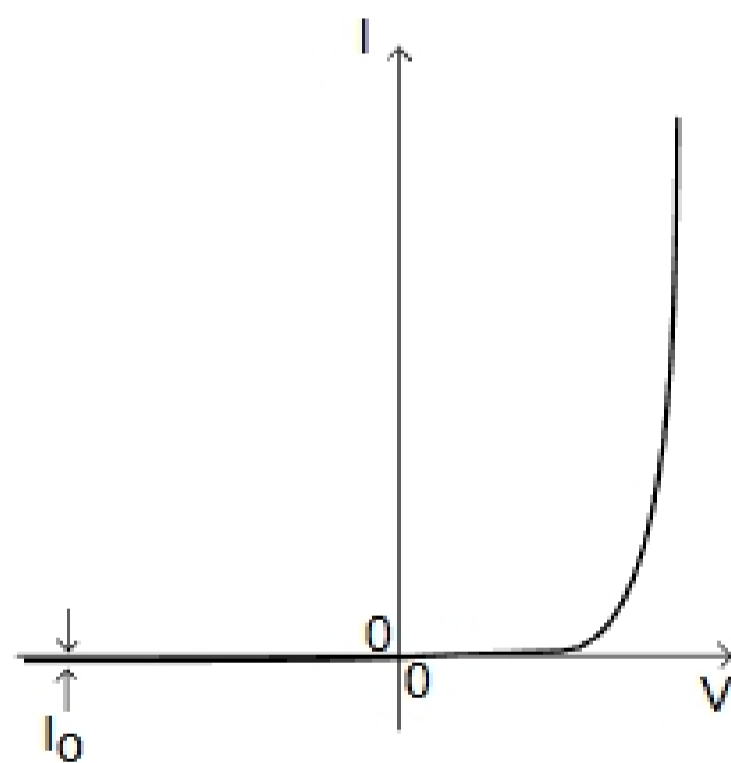
$$I = I_o \left[e^{\left(\frac{V}{V_{th}}\right)} - 1 \right]$$



linear scale

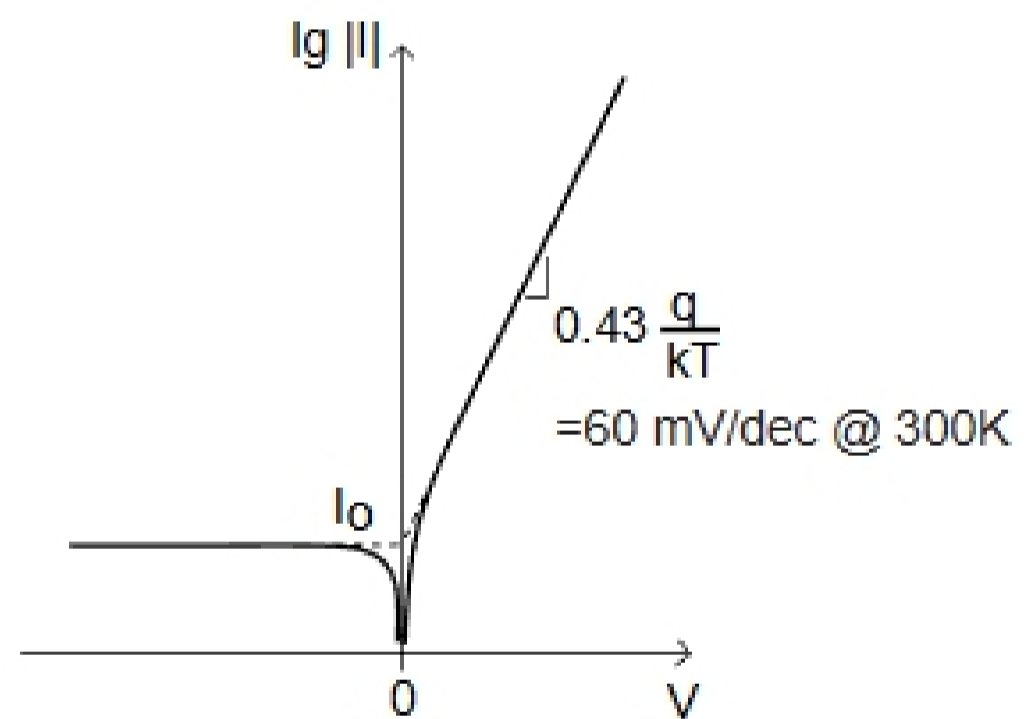

semilogarithmic scale

2. Small-signal equivalent circuit model

Examine effect of small signal adding to forward bias:

$$I + i = I_o \left[e^{\left(\frac{q(V+v)}{kT} \right)} - 1 \right] \approx I_o e^{\left(\frac{q(V+v)}{kT} \right)}$$

If v small enough, linearize exponential characteristics:

$$\begin{aligned} I + i &\approx I_o \left[e^{\left(\frac{qV}{kT} \right)} e^{\left(\frac{qv}{kT} \right)} \right] \approx I_o \left[e^{\left(\frac{qV}{kT} \right)} \left(1 + \frac{qv}{kT} \right) \right] \\ &= I_o e^{\left(\frac{qV}{kT} \right)} + I_o e^{\left(\frac{qV}{kT} \right)} \frac{qv}{kT} \end{aligned}$$

Then:

$$i = \frac{qI}{kT} \bullet v$$

From a small signal point of view. Diode behaves as **conductance** of value:

$$g_d = \frac{qI}{kT}$$