

## ***C. Microwave Sources***

**Q:** *A passive load  $Z_L$  specifies  $Z(z)$  and  $\Gamma(z)$ , but we still don't explicitly know  $V(z)$ ,  $I(z)$  or  $V^+(z)$ ,  $V^-(z)$ . How are these functions determined?*

**A:** All of these quantities are zero, unless a source (generator) is applied to trans. line. The **boundary condition** enforced by the generator will then **explicitly** determine these functions!

### **HO: A Transmission Line Connecting Source and Load**

**Q:** *OK, we can finally ask the question that we have been concerned with since the very beginning: How much **power** is delivered to the load by the source?*

**A:** **HO: Delivered Power**


**Q:** *So the power transferred depends on the **source**, the **transmission line**, and the **load**. What combination of these devices will result in **maximum** power transfer?*

**A:** **HO: Special Cases of Source and Input Impedances**

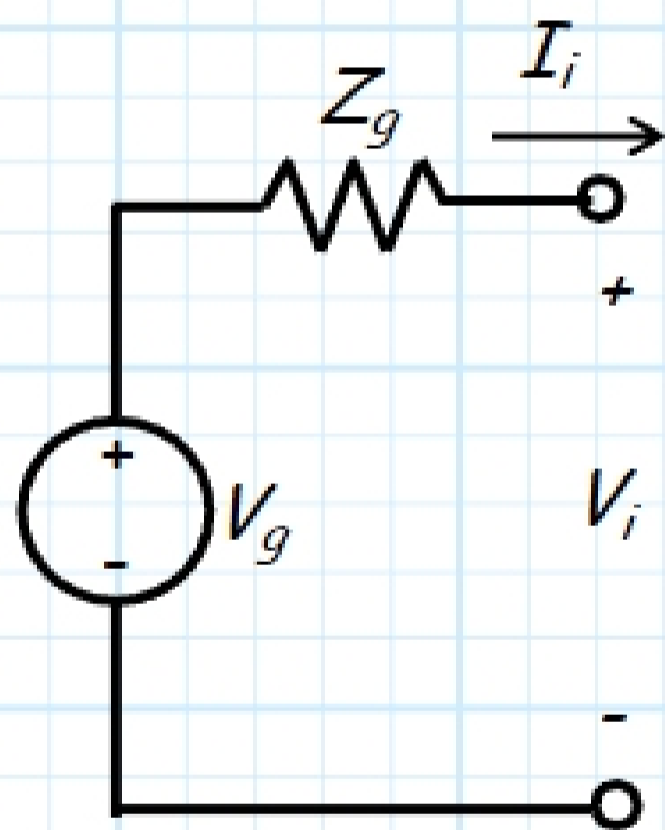
# A Transmission Line Connecting Source & Load

We can think of a transmission line as a conduit that allows **power** to flow from an **output** of one device/network to an **input** of another.

To simplify our analysis, we can model the **input** of the device **receiving** the power with its input impedance (e.g.,  $Z_L$ ), while we can model the device **output delivering** the power with its Thevenin's or Norton's equivalent circuit.




$$V_g = V_i + Z_g I_i$$

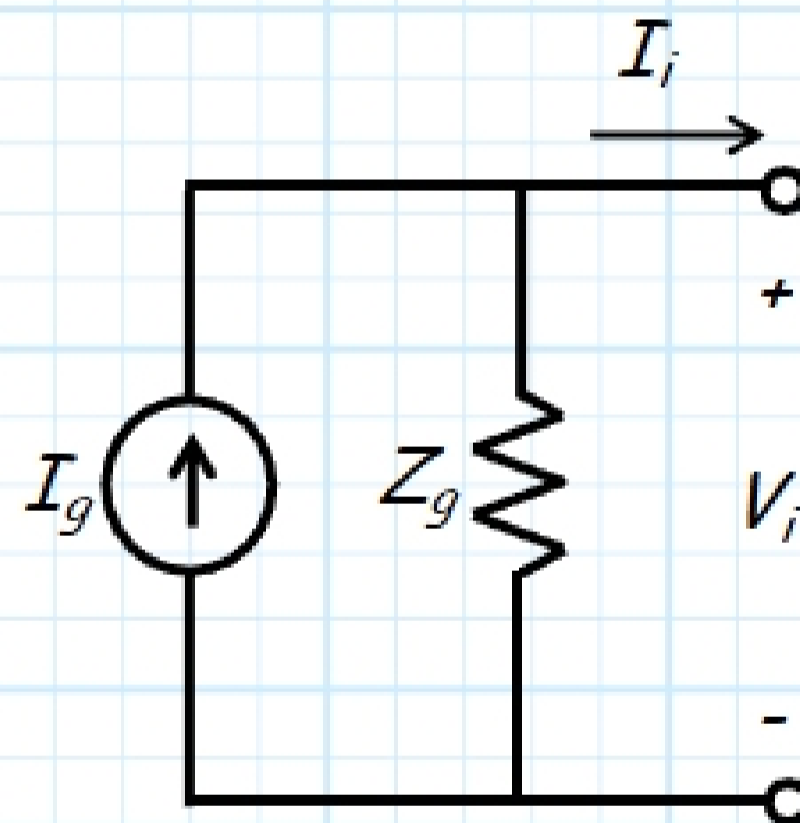

$$I_g = \frac{V_i}{Z_g} + I_i$$

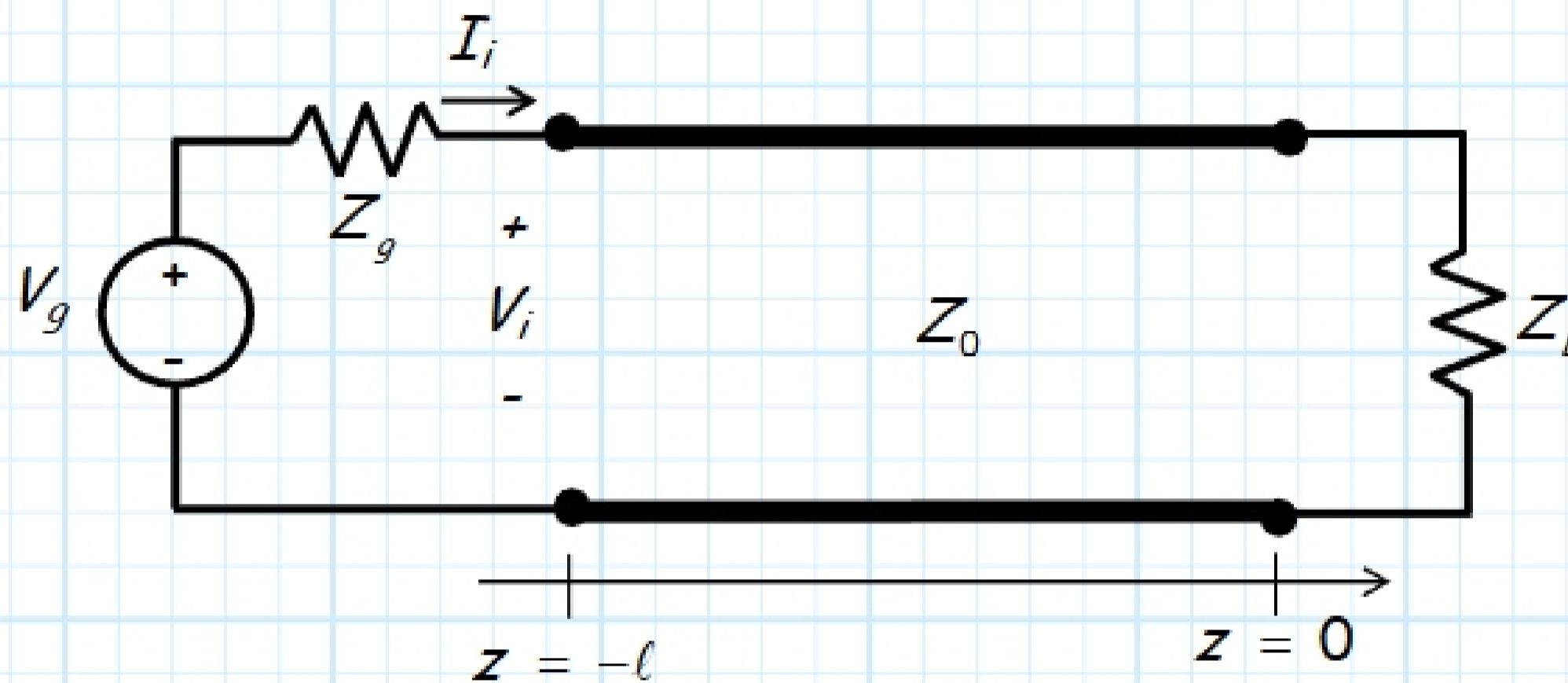Typically, the power source is modeled with its **Thevenin's** equivalent; however, we will find that the **Norton's** equivalent circuit is useful if we express the remainder of the circuit in terms of its **admittance** values (e.g.,  $Y_0, Y_L, Y(z)$ ).



**Recall** from the telegrapher's equations that the current and voltage along the transmission line are:

$$V(z) = V_0^+ e^{-j\beta z} + V_0^- e^{+j\beta z}$$

$$I(z) = \frac{V_0^+}{Z_0} e^{-j\beta z} - \frac{V_0^-}{Z_0} e^{+j\beta z}$$

At  $z = 0$ , we enforced the **boundary condition** resulting from Ohm's Law:

$$Z_L = \frac{V_L}{I_L} = \frac{V(z=0)}{I(z=0)} = \frac{(V_0^+ + V_0^-)}{\left(\frac{V_0^+}{Z_0} - \frac{V_0^-}{Z_0}\right)}$$