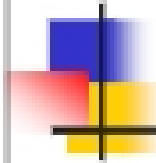


Physics 202
Chapter 32 continued
Oct 30, 2007




Induction:
LC circuit, RLC circuit

On whiteboard

- LC circuit
 - Solve Kirchhoff's equation
 - Harmonic oscillator
 - Discussion
 - analogy to mass spring system
 - Energy
- RLC circuit
 - Solution
 - Demonstration with a weakly damped RLC circuit

LC Circuits

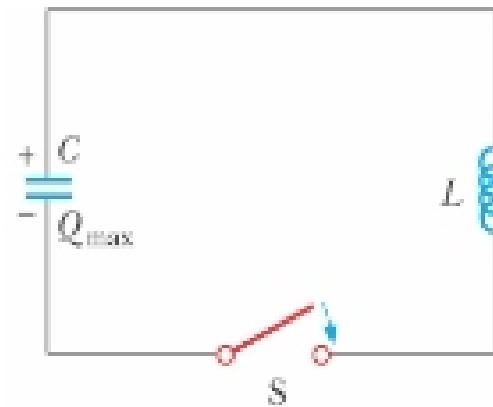- Assume the capacitor is initially charged and then the switch is closed
- Assume no resistance and no energy losses to radiation
- The current in the circuit and the charge on the capacitor oscillate between maximum positive and negative values
- With zero resistance, no energy is dissipated.




- Kirchoff's loop rule:

$$-\frac{Q}{C} - L \frac{dI}{dt} = 0$$

Discussion on whiteboard....

Derivation of LC and RLC circuit.

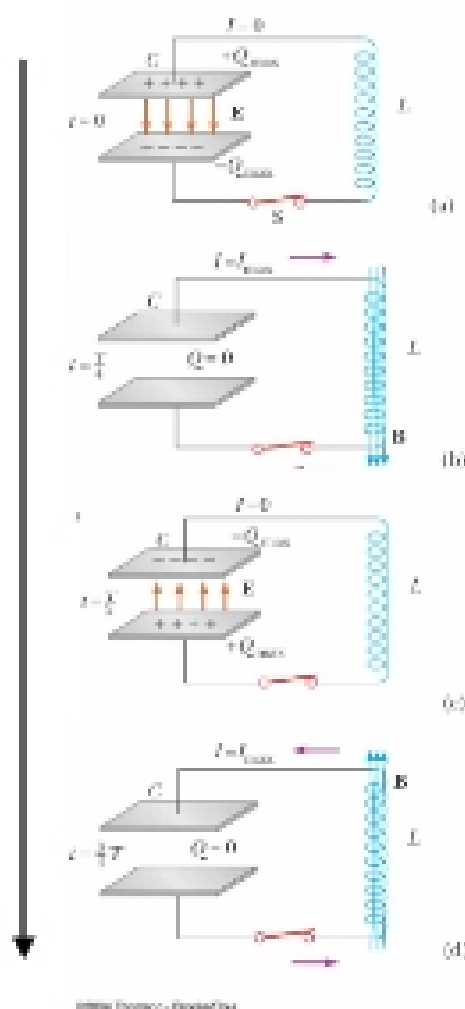

LC oscillator

- Initially energy stored in the electric field in the capacitor

$$U = \frac{Q^2}{2C}$$

- Then energy transferred to B-field

$$U = \frac{1}{2} L \cdot I^2$$

- And so forth

LC oscillator

Time [T]	Q [Q _{Max}]	I [I _{Max}]
0	1	0
1/4	0	1
1/2	-1	0
3/4	0	-1
1	1	0

Analogy to mechanical harmonic oscillator

The diagrams illustrate the analogy between the electrical LC oscillator and a mechanical harmonic oscillator. The capacitor's charge corresponds to the spring's displacement, and the inductor's current corresponds to the mass's velocity.