

Lumped Modeling in Thermal Domain


- ☑ Last lecture
 - Lumped modeling
 - Self-heating resistor

- Today:
 - Self-heating resistor
 - Other dissipation mechanisms
 - Friction, dielectric, magnetic, damping
 - Coupled flows

📖 Reading: Senturia, Chapter 11, p.278-296

- Temperature dependent resistance

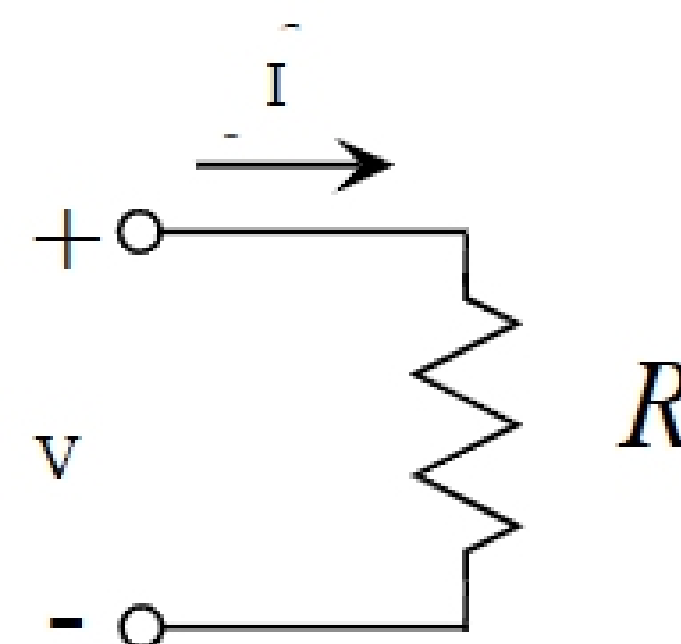
- Voltage-Current relation, $V=IR(T)$ (Ohm's Law)
 - Now we consider resistor self-heating and temperature dependence of resistance, $R(T)$
 - Joule Heating, $P_{\text{dissipation}}=VI=I^2R >0$
 - For small to moderate temperature variation, approximate $R(T)$ using first order Taylor series expansion.



$$R(T) \cong R(T_0)[1 + \alpha_R(T_R - T_0)]$$

where $\alpha_R =$ temperature coefficient of resistance [1/K]

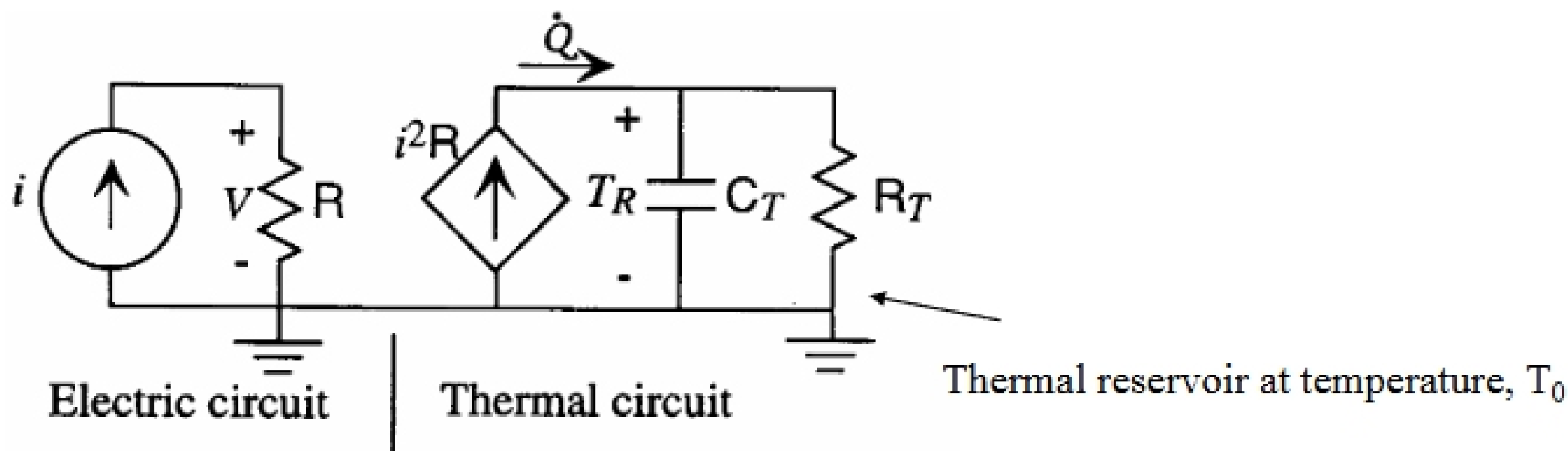- Circuit model for resistor self-heating--
Current Source



Governing equation is:

$$C_T \frac{dT_R}{dt} = -\frac{T_R}{R_T} + i^2 R_0 (1 + \alpha_R T_R)$$

$$\frac{dT_R}{dt} = -\frac{1}{R_T C_T} (1 - \alpha_R R_0 R_T i^2) T_R + \frac{i^2 R_0}{C_T}$$

Ref. Senturia, Microsystem Design, p. 231.