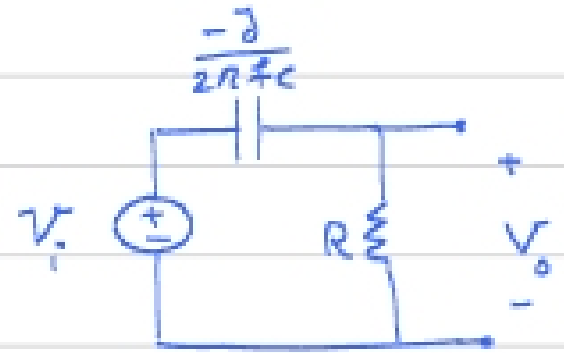




### First order RC high pass filters

$$H(f) = \frac{V_o}{V_i} = \frac{R}{R - \frac{j}{2\pi fC}}$$



$$= \frac{1}{1 - \frac{j}{2\pi fRC}} = \frac{2\pi fRC}{2\pi fRC - j1} \times \frac{j}{j} = \frac{j2\pi fRC}{j2\pi fRC + 1}$$

$$H(f) = \frac{j \frac{f}{f_B}}{1 + j \frac{f}{f_B}}$$

where,  $f_B = \frac{1}{2\pi RC}$



$$\Rightarrow |H(f)| = \frac{\frac{f}{f_B}}{\sqrt{1 + (\frac{f}{f_B})^2}}, \quad \angle H(f) = 90 - \tan^{-1} \frac{f}{f_B}$$

↘ straight line with slope of 20  $\frac{dB}{dec}$

If  $f \ll f_B \Rightarrow |H(f)|_{dB} = 20 \log \frac{f}{f_B}, \quad \angle H(f) = 90^\circ$

If  $f = f_B \Rightarrow |H(f)|_{dB} = 20 \log \frac{1}{\sqrt{2}} = -3 \text{ dB}, \quad \angle H(f) = 45^\circ$

If  $f \gg f_B \Rightarrow |H(f)|_{dB} = 20 \log 1 = 0, \quad \angle H(f) = 0$

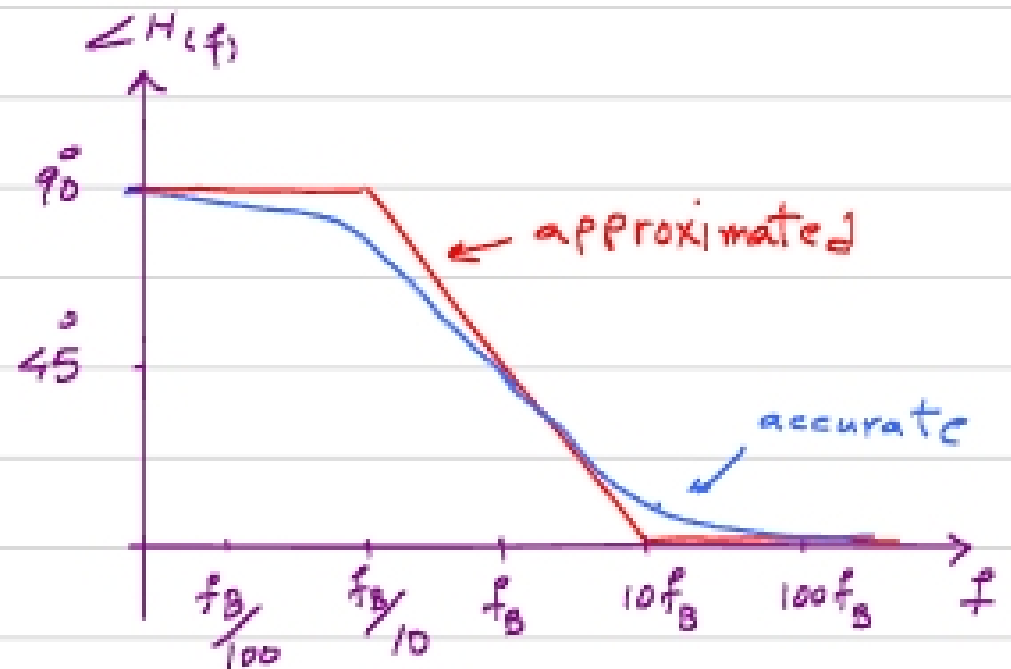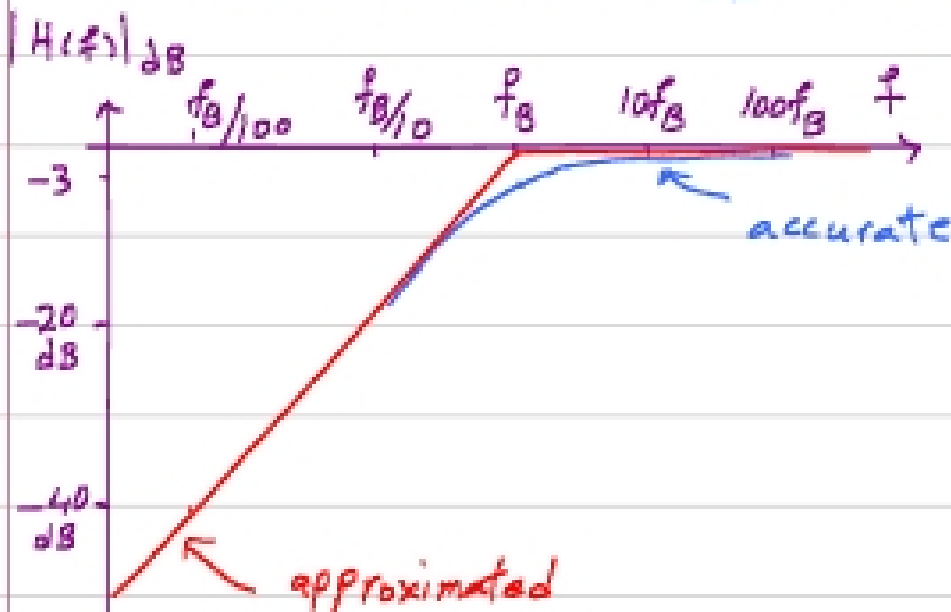


**Table 6.2. Transfer-Function Magnitudes and Their Decibel Equivalents**

$ H(f) $	$ H(f) _{dB}$
100	40
10	20
2	6
$\sqrt{2}$	3
1	0
$1/\sqrt{2}$	-3
1/2	-6
0.1	-20
0.01	-40

$$|H(f)|_{dB} = 20 \log |H(f)|$$

Ex. Find the type of filter. what is the break frequency?
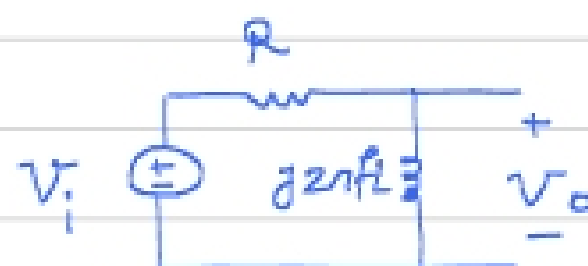
$$H(f) = \frac{V_o}{V_i} = \frac{j2\pi fL}{R + j2\pi fL} = \frac{j2\pi f \frac{L}{R}}{1 + j2\pi f \frac{L}{R}}$$



$$H(f) = \frac{j \frac{f}{f_B}}{1 + j \frac{f}{f_B}}, \quad f_B = \frac{R}{2\pi L}$$

This is the transfer function of a high pass filter with the break frequency of  $\frac{R}{2\pi L}$ .

It is also possible to find the type of filter using this reasoning:

$$Z_L = j2\pi fL \Rightarrow \text{at low frequency } (f \approx 0) \quad Z_L \approx 0 \Rightarrow$$

inductor is close to a short ckt.  $\Rightarrow V_o = 0$

$\Rightarrow$  NO low frequency components exist at the output.

at high freq.,  $Z_L$  is large (close to open ckt.)  $\Rightarrow V_o = V_i$

$\Rightarrow$  High frequency component can pass through the filter

Therefore, this is a high pass filter.


## Band pass filter

In some applications it is desired to select a certain range of frequencies and discard the other frequencies. Such filters are useful in radio receivers for example.

This filter is called band pass filter and can be made using RLC circuit. (second order circuits)

Total impedance is
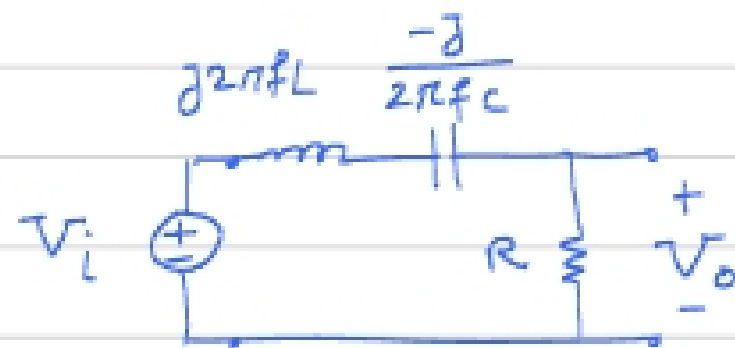
$$Z_s = R + j2\pi fL + \frac{-j}{2\pi fC}$$



Resonant frequency is defined as the frequency at which the

total impedance is purely resistive. ( $Z_L + Z_C = 0$ ). Therefore at

resonant frequency  $f_0$  :

$$j2\pi f_0 L - \frac{j}{2\pi f_0 C} = 0 \Rightarrow 4\pi^2 f_0^2 LC = 1 \Rightarrow$$

$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$

resonant  
frequency

Quality factor is defined as :

$$Q_s = \frac{|Z_L|}{R} \Big|_{f=f_0} = \frac{2\pi f_0 L}{R} \quad (1), \text{ since } |Z_L| = |Z_C| \text{ at } f=f_0, Q_s \text{ is also:}$$

$$Q_s = \frac{|Z_C|}{R} \Big|_{f=f_0} = \frac{1}{2\pi f_0 RC} \quad (2), \text{ then the total impedance can be written as:}$$

$$Z_s = R \left[ 1 + jQ_s \left( \frac{f}{f_0} - \frac{f_0}{f} \right) \right]$$

multiplied by  $Q_s$  from (1)      multiplied by  $Q_s$  from (2)

$$H(f) = \frac{V_o}{V_s} = \frac{R}{Z_s} = \frac{1}{1 + jQ_s \left( \frac{f}{f_0} - \frac{f_0}{f} \right)}$$

$$|H(f)| = \frac{1}{\sqrt{1 + Q_s^2 \left( \frac{f}{f_0} - \frac{f_0}{f} \right)^2}}$$