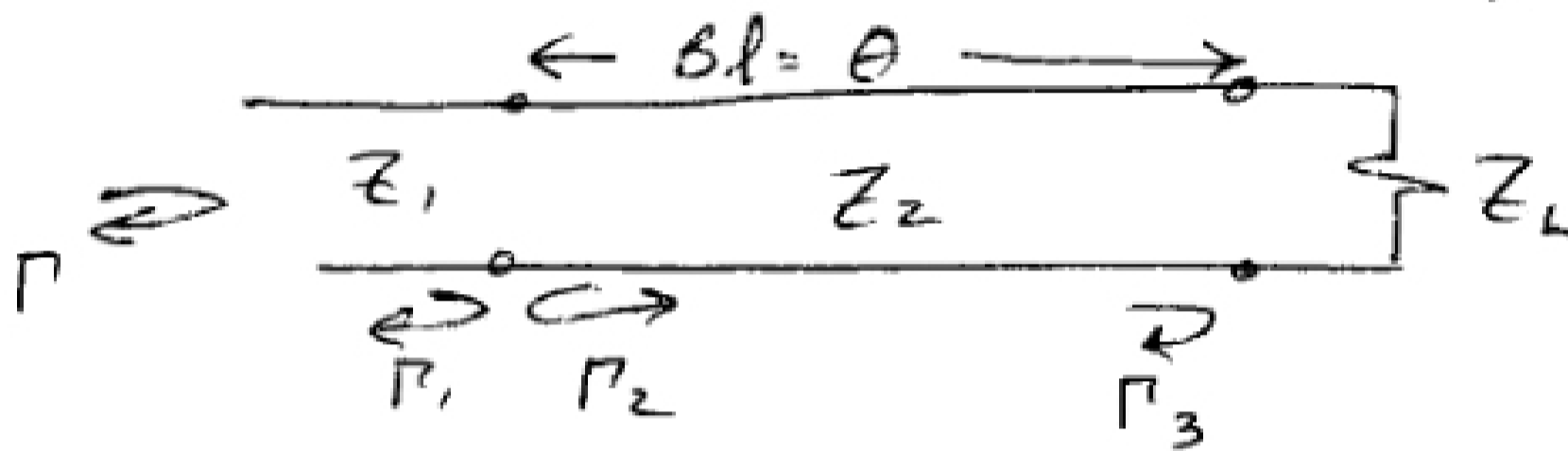


Broad Band Matching

Text Sections 5.5 + 5.6

General Theory:

Reconsider Single Section transformers:



How do you design a Broad Band match network?
 Binomial, Chebyshev
 Eq. 5.16, 20

Find Γ :

$$\Gamma_1 = \frac{Z_2 - Z_1}{Z_2 + Z_1} \quad \Gamma_2 = \frac{Z_1 - Z_2}{Z_2 + Z_1} = -\Gamma_1$$

$$\Gamma_3 = \frac{Z_L - Z_2}{Z_L + Z_2} \quad T_{12} = 1 + \Gamma_2$$

$$T_{21} = 1 + \Gamma_1$$

$$\Gamma = \Gamma_1 +$$

$$T_{12} T_{21} \Gamma_3 e^{-j2\theta}$$


$$+ T_{12} T_{21} \Gamma_3^2 \Gamma_2 e^{j4\theta}$$

+ ...

$$T_{12} (T_{21} \Gamma_3) e^{-j2\theta}$$

$$T_{12} (T_{21} \Gamma_3^2 \Gamma_2) e^{-j4\theta}$$


$$\Gamma = \Gamma_1 + T_{12} (T_{21} \Gamma_3) e^{-j2\theta} \sum_{n=0}^{\infty} \Gamma_2^n \Gamma_3^n e^{-jn\theta}$$

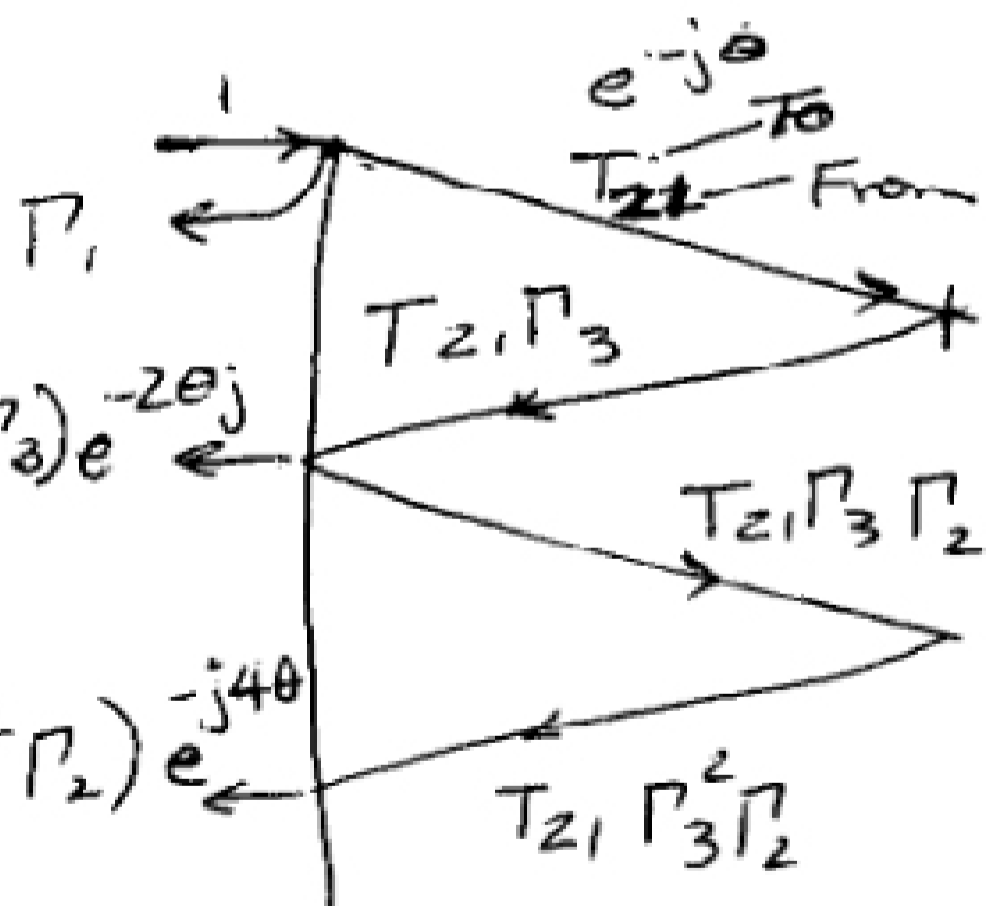

Band 3
11-12-01

Use this to design optimal broadband matching

1. Quarter wave transformer

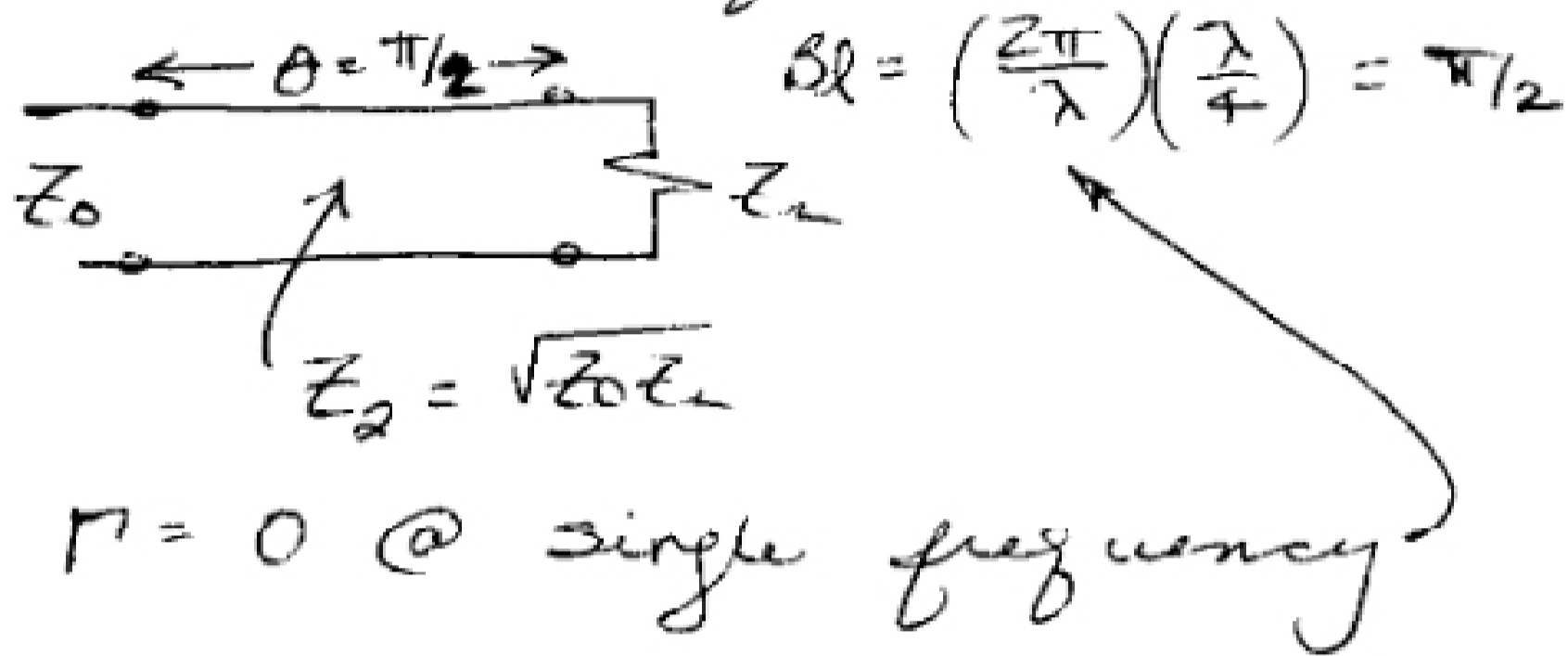

2. Binomial Matching Network

Let $\Gamma(\theta) = A(1 + e^{-jz\theta})^N$ ← # of sections = $A \sum_{n=0}^N C_n^N e^{-2jn\theta}$ ← Binomial coefficients

Produces flattest response of passband
best matching @ desired frequency some mismatch outside

Design process:

Use length of line to convert Z_L complex to Z_0 real

$N = \# \text{ sections}$


$$A = 2^{-N} \left| \frac{Z_L - Z_0}{Z_L + Z_0} \right|$$

$$BW = \frac{\Delta f}{f_0}$$

$$C_n^N = \frac{N!}{(N-n)! n!} \quad \text{for } n = 0 \text{ to } N-1$$

$$\ln \frac{Z_{n+1}}{Z_n} = 2 A C_n^N$$

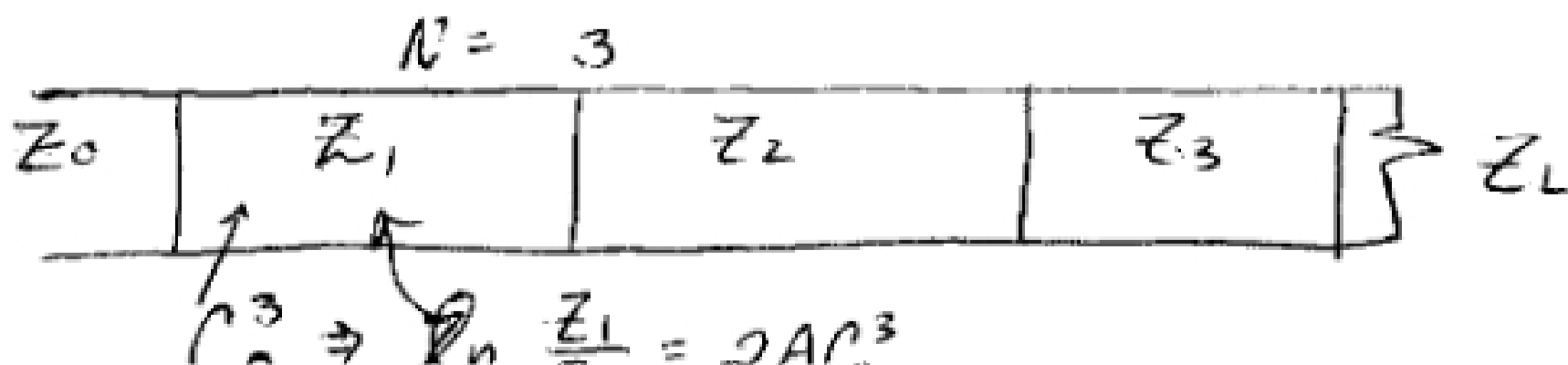Length: $\theta = 0$
 $Bl = 0, 360, \dots$
 $L = m\lambda$



3. Chebyshev.

Similar to binomial, but different calculation of Z_n

4. Tapered lines

If series (cascade) of lines provides good matching, why not a continuously-varying impedance i.e. a tapered line

Many possibilities

Research Areas:

5. Optimal matching found using optimization theory on any of the above methods

You provide a desired distribution, optimization provides a "closest fit" solⁿ

This is now commonly used for applications where optimal matching with minimal weight (# sections) is required & high power antenna systems.

Addition of sections tend to increase noise in circuit, also, so they should be minimized

6. Use of PML theory may be applied to numerical work as well.

Above theory is for normal incidence or TEM behavior. Non-TEM is more complicated and can also be optimized.