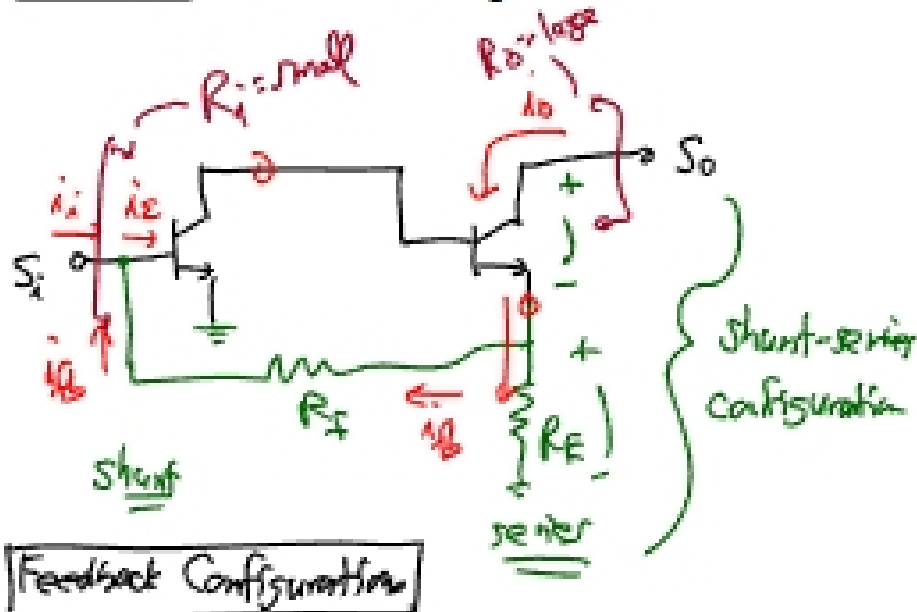


Lecture 26: Feedback Impedance

- Announcements:
  - Last HW#12 online (due during RRR week)
  - Yes, I know, but it'll help you on the Final
- Lecture Topics:
  - Effect of FB on  $Z_i$  and  $Z_o$
  - Feedback Loading
- Last Time: Feedback Configurations




Feedback Configuration

Variable	Connection	Connection	Variable
voltage	series	series	current
current	shunt	shunt	voltage

$N \rightarrow i$   
 $N \rightarrow N$     $i \rightarrow N$     $i \rightarrow i$

Effect of FB on  $Z_i$  &  $Z_o$

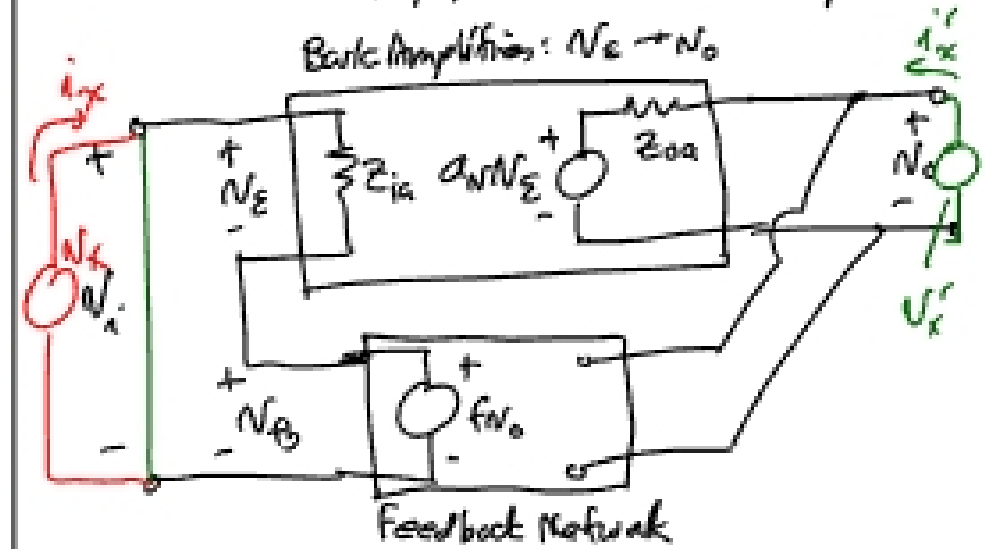Ex: series-shunt FB  
 Assumption: FB network has ideal impedances  
 i.e., it does not load the amplifier  
 Basic Amplifier:  $N_e \rightarrow N_o$



Find the T.F.:

$$\left. \begin{aligned} N_e &= N_i - N_{fb} \\ N_o &= a_v N_e \\ N_{fb} &= f N_o \end{aligned} \right\} \Rightarrow \frac{N_o}{N_i} = \frac{a_v}{1 + a_v f} \quad \checkmark$$

(as expected)

Find  $Z_i = \frac{N_x}{i_x}$ :

$N_x = N_E + N_{FB}$   
 $= N_E + fN_o = N_E + a_v f N_E = N_E(1 + a_v f)$

$i_x = \frac{N_E}{Z_{ia}}$

$Z_i = \frac{N_x}{i_x} = \frac{N_E(1 + a_v f)}{\frac{N_E}{Z_{ia}}} = Z_{ia}(1 + a_v f) = Z_i$

amplifier alone input impedance

loop gain!

When we series connect @ input: Input impedance raised by  $(1 + a_v f)!$  → makes for a better voltage amplifier!

Find  $Z_o = \frac{N_x'}{i_x'}$ : (or input shouter)

$N_E + N_{FB} = N_E + fN_x' = 0 \rightarrow N_E' = -fN_x'$

$i_x' = \frac{N_x' \cdot a_v N_E}{Z_{oa}} = \frac{N_x' + a_v f N_x'}{Z_{oa}}$

$\frac{N_x'}{i_x'} = \frac{Z_{oa}}{1 + a_v f} = Z_o$

Output impedance loaded by a factor of  $(1 + a_v f)$

Again, makes for a better voltage amplifier!

Overall, series-shunt FB improves the impedance character favorable to a  $v \rightarrow v$  amplifier:  
 $Z_i \uparrow, Z_o \downarrow$  due to series-shunt FB

Ex. Shunt-Series FB

→ Again, around FB network does not load the amplifier

Basic Amplifier:  $i_E \rightarrow i_o$

FB Network:  $i_o \rightarrow i_{FB}$

current gain of amp alone

Find T.F.:

$i_o = a_v i_E$

$i_E = i_x - i_{FB} = i_x - f i_o$

$\frac{i_o}{i_x} = \frac{a_v}{1 + a_v f}$

loop gain

Same form as for  $v \rightarrow v$  amp. This is a universal form!

Find  $Z_i = \frac{V_x}{I_x}$ :

$$\frac{V_x}{I_x} = \frac{Z_{ia}}{1 + a_i f}$$

$\Rightarrow$  again, a shunt connection reduces the impedance by  $(1 + a_i f)$ !

loop gain

Find  $Z_o = \frac{V_o}{I_o}$ :

$$Z_{oo}(1 + a_i f) = Z_o$$

series connection raises the impedance by  $(1 + a_i f)$

All together  $\rightarrow$  makes for a better  $i \rightarrow i$  amp (when using shunt-series FB)

Summary:

- ① series connection:  $Z \rightarrow Z(1+T)$
- ② shunt connection:  $Z \rightarrow \frac{Z}{(1+T)}$

$T = \text{loop gain}$

Determine the FB Loading of an Amplifier

Example: Non-Inverting Amplifier

Series-shunt:  $V \rightarrow V$

Objective: Use  $A_o = \frac{A_v}{1 + a_i f}$  to get  $A_o$ .

In order to use this equation, we must know

- (i)  $a_i \triangleq$  gain of the amplifier
- (ii)  $f \triangleq$  gain of the feedback (also, called the feedback factor)  $\leftarrow$  gain of feedback

In general:

$h$ -parameter network