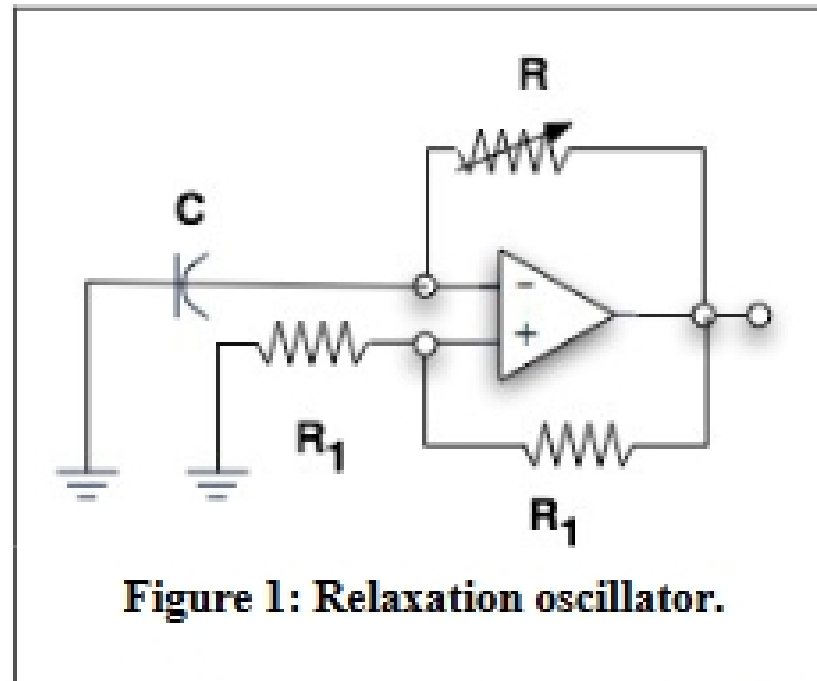



## Op Amps II

**Op-Amp Relaxation Oscillator**

Questions indicated by an asterisk (\*) should be answered before coming to lab.



Build the relaxation oscillator shown in Figure 1 above. The output should be a square wave with a frequency about  $1/(2RC)$ . Resistor  $R_1$  can be any value between  $1k\Omega$  and  $1M\Omega$ . Resistor  $R$  is one side of a potentiometer. Examine  $V_-$  and  $V_+$  (the voltages at + and - inputs) and at the output to follow the action of the switching. It is useful to display  $V_-$  and  $V_+$  simultaneously on the same scale to illustrate that the switching occurs at the crossover of  $V_-$  and  $V_+$ . How does this circuit work? Why does  $V_o$  resemble a triangular wave?

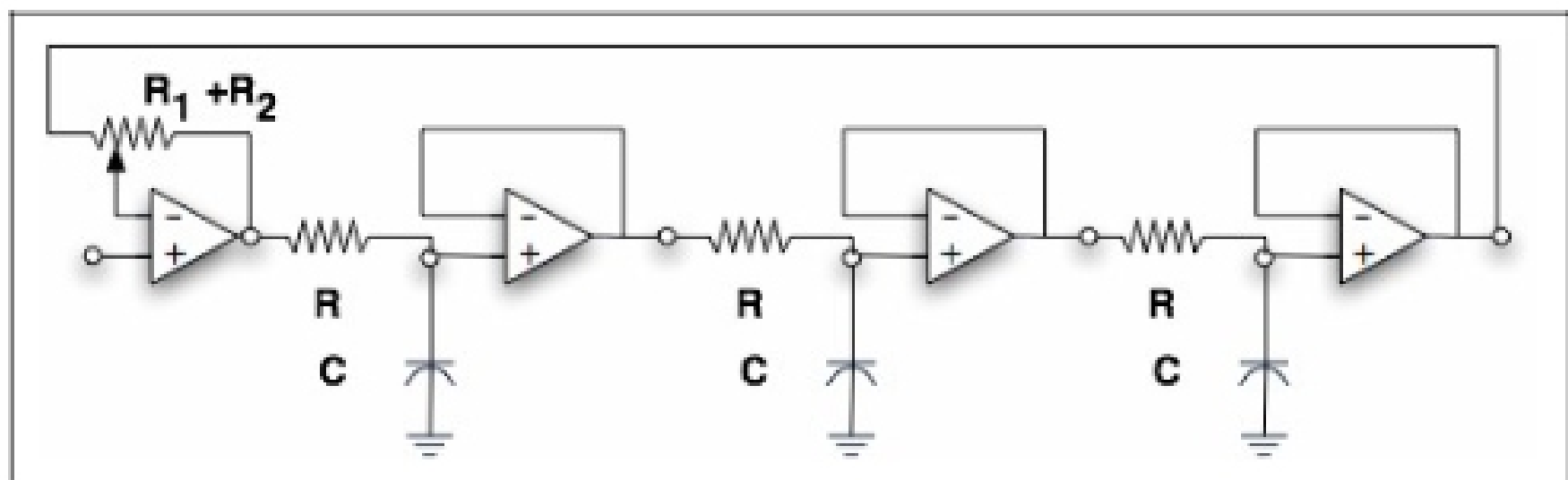**Low-Pass Resonant Filter**

**Figure 2: Low-pass resonant filter.**

\*Show that the transfer function for the low pass resonant filter, shown in Figure 2, is given by:

$$H(\omega) = \frac{1}{1 - x + x(1 + j\omega\tau)^3} \quad (1)$$

where  $\omega$  refers to the angular frequency of an oscillator connected to the non-inverting input of the first (leftmost) op amp,  $\tau = RC$  and  $x$  is the ratio of  $R_1$  to the total pot resistance  $R_1 + R_2$ . Here  $R_1$  is the part of the pot resistance between the output and the inverting input of the first op amp and  $R_2$  is the part of the pot resistance between the inverting input and output of the first op amp.

[Hint: Begin by naming the output voltages of each op amp, from left to right, as  $v_1$  through  $v_4$ . Then use the infinite gain assumption to show that:

$$\frac{(v_4 - v_{in})}{R_1} = \frac{(v_{in} - v_1)}{R_2} \quad (2)$$

Next, use what you know about RC filters to find  $v_4$  in terms of  $v_1$ .]

The resonance depends on both  $x = \frac{R_1}{R_1 + R_2}$  and  $\omega\tau = \omega RC$ . Figure 3 shows the gain versus  $\omega\tau$  for four different values of  $x$ . It can be shown (you do not have to do this) that the real part of the denominator of Equation 1 vanishes when  $3x(\omega\tau)^2 = 1$ . Furthermore, the gain is sharply peaked when  $\omega\tau = \sqrt{3}$  and  $x = \frac{1}{9}$ .

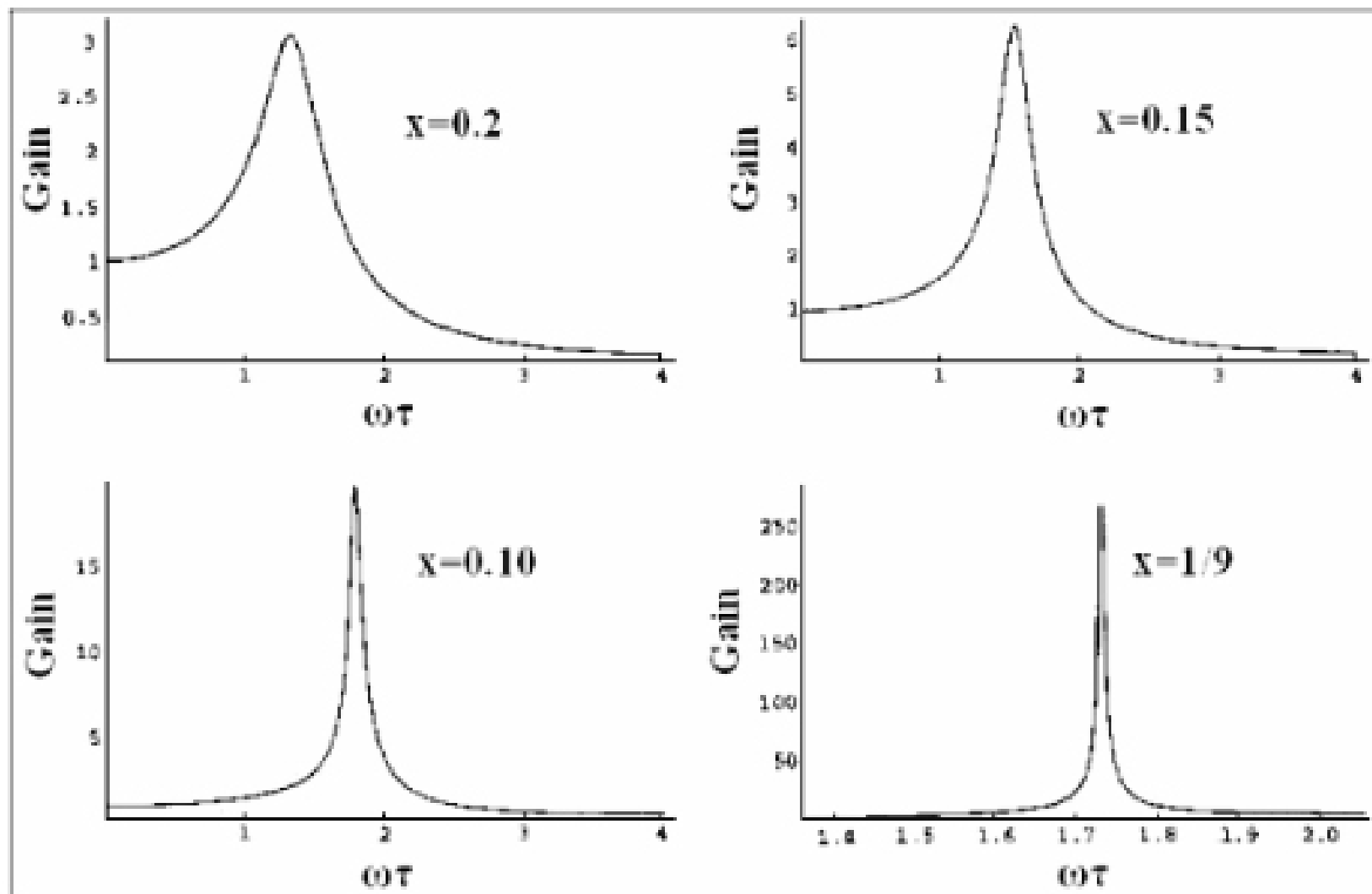


Figure 3

When you understand the equation for the transfer function, build the circuit. It is convenient to use a TL084 with four op amps in a package. Choose  $RC$  so that the resonant frequency is 2 to 5 kHz (It is best to use a resistor  $\sim 5\text{ k}\Omega$ ). Examine the resonant behavior by feeding in a sine signal from a function generator. Specifically:

- (1) Set the function generator to the  $x = \frac{1}{9}$  resonance frequency of  $f = \frac{\sqrt{3}}{2\pi RC}$ .
- (2) Adjust the pot to maximize the output amplitude (now you should be close to  $x = \frac{1}{9}$ ).
- (3) Find  $H(\omega)$  here and for 5 higher frequencies and for 5 lower frequencies.

Make a Bode plot of the transfer function. Lastly, check the high frequency roll off. It should be proportional to  $1/\omega^3$ .