


ECE/CE 3720: Embedded System Design

Chris J. Myers

Lecture 17: Output LEDs and LCDs


Slide 1

Single LED Interface

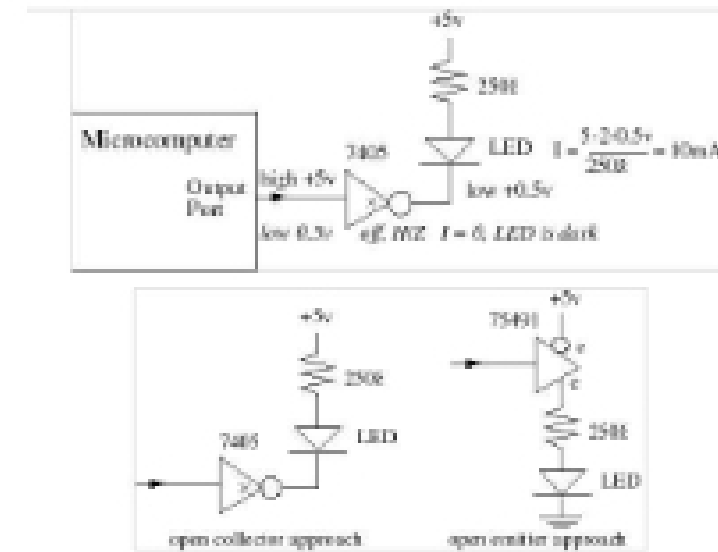

Slide 3

Interfacing Multiple LEDs

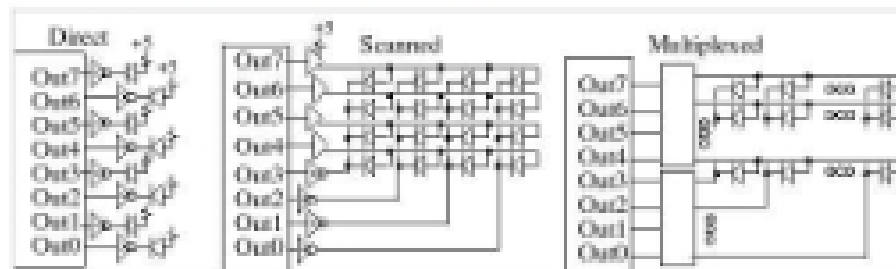

Slide 2


Output Param. for Open-Collector/Emitter Gates

(See Tables 8.4 and 8.5)

Slide 4

Slide 5

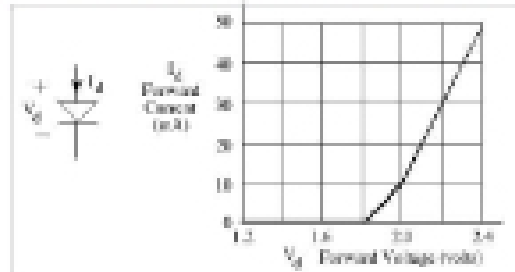
Typical Voltage/Current Response of a LED



Parameter	red	green	yellow	orange	units
Max power	55	75	60	75	mW
Peak current	160	100	80	100	mA
Max current	25	25	20	25	mA


Slide 6

Calculating the Resistor Value

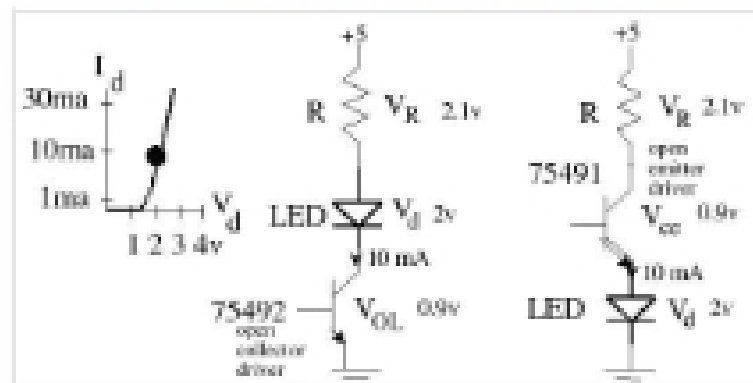


Slide 7

Seven-Segment LED Interfaces (Common-Cathode)

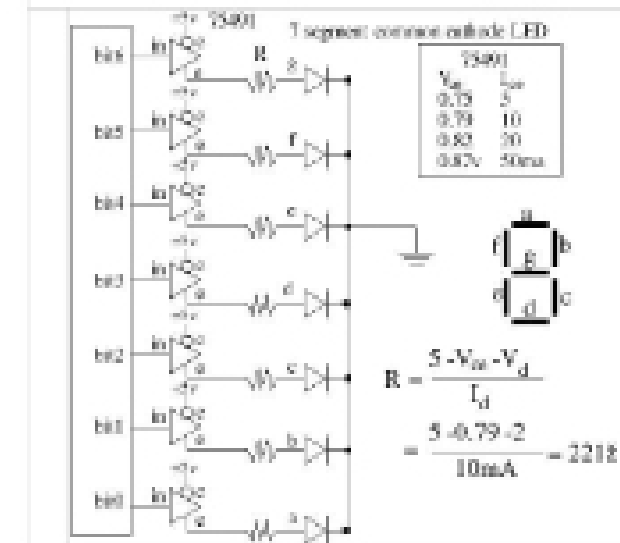


Slide 8

Seven-Segment LED Interfaces (Common-Anode)

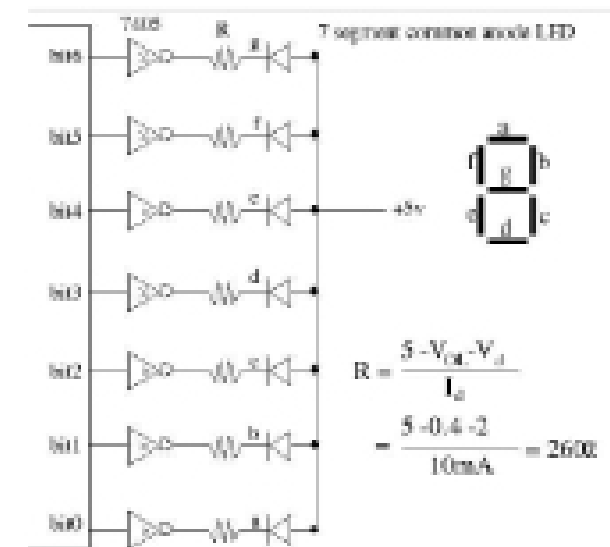

Slide 9

Scanned Seven-Segment LED Interface

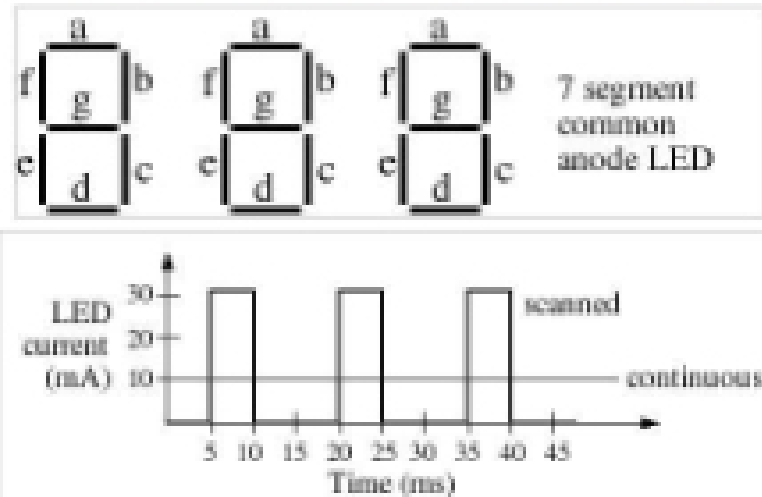


Slide 11

Software for Scanned LED Display

```
// PB7-PB0 output, 7 bit pattern
// PC2-PC0 output, selects LED digit
unsigned char code[3]; // binary codes
static unsigned char select[3]={4,2,1};
unsigned int index; // 0,1,2
#define OC5F 0x08
void ritual(void) {
asm(" sei"); // make atomic
index=0;
DDRC=0xFF; // outputs
TMSK1|=OC5F; // Arm OC5
TIFL1=OC5F; // clear OC5F
TCC5=TCNT+10000;
asm(" cli"); }
```

Slide 10

Circuit Used to Scan a LED Interface

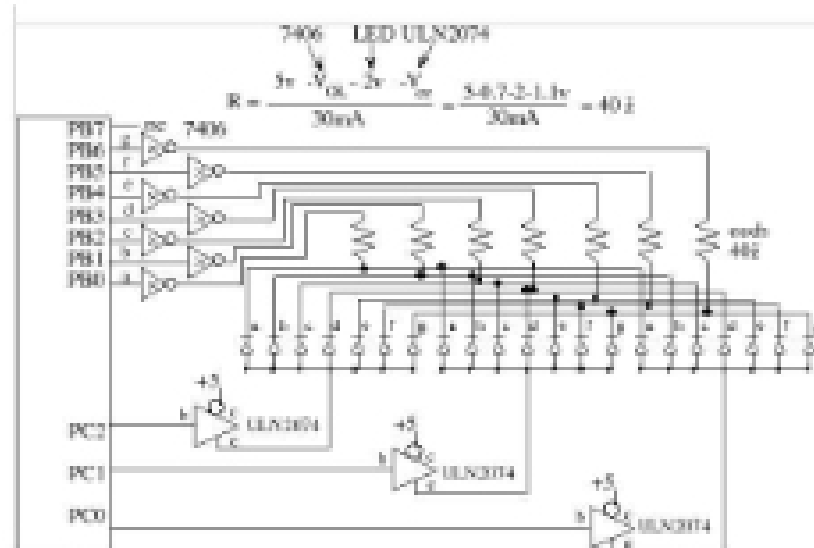

Slide 12

Software for Scanned LED Display

```
#pragma interrupt_handler TCC5handler()
void TCC5handler(void){
TIFL1=OC5F; // Acknowledge
TCC5=TCC5+10000; // every 5 ms
PORTC=select[index]; // which LED?
PORTB=code[index]; // enable
if(++index==3) index=0;}
```