

University of California
Berkeley
College of Engineering
Department of Electrical Engineering
and Computer Science

Robert W. Brodersen
EECS140

Analog Circuit Design


Lectures
on
OUTPUT STAGES

Output Stages

O-1

Large Signal Swing
Distortion
Power
Efficiency

Typical OP Amp:

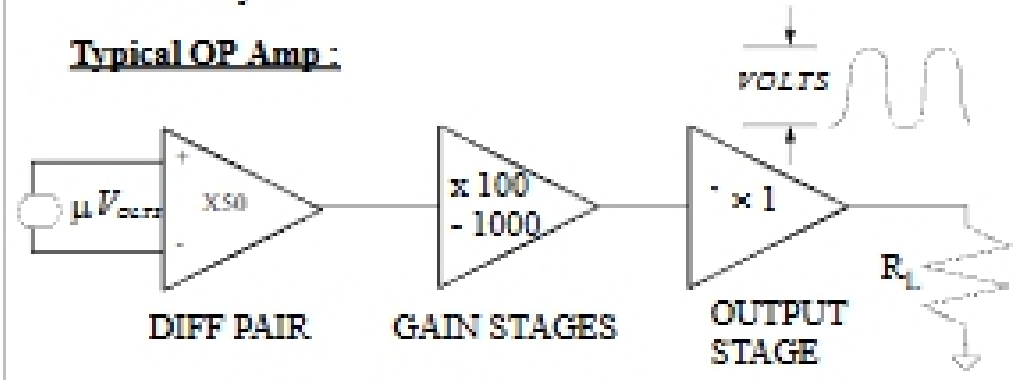


O-2

Power:

Total power from supplies = P_{TOTAL}

Power into Load = P_{LOAD}

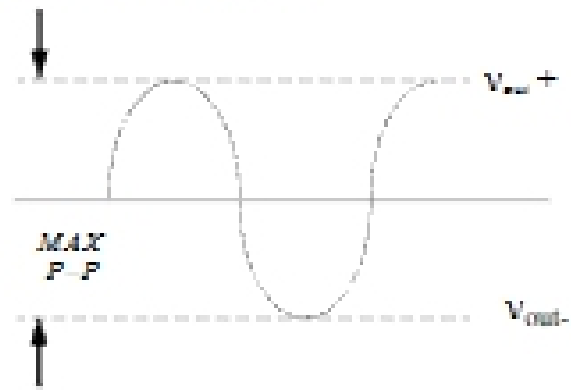
$$Efficiency = \frac{P_{LOAD}}{P_{TOTAL}} (\%)$$




V_{out+} = desired plus swing
 V_{out-} = desired neg. swing

O-3

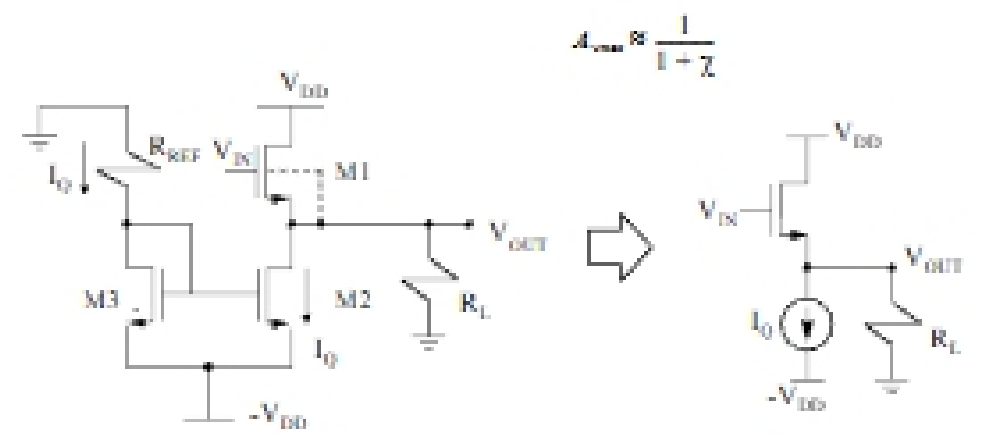Typically output load is low impedance (but not always!)
If it is, a source follower is a possible output stage.



O-4

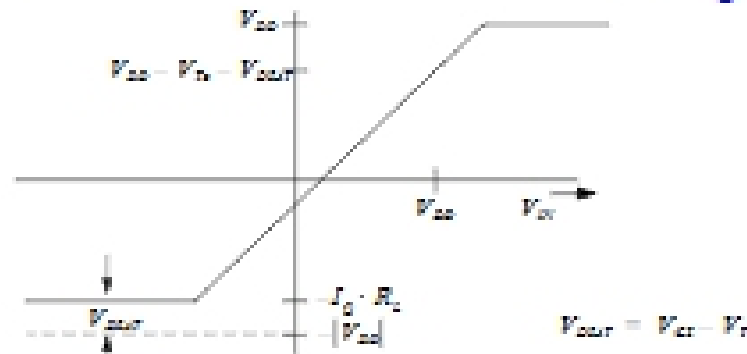

$$V_{out,max} = V_{DD} - V_T - V_{sat}$$

$$V_{out,min} = \underbrace{V_{sat} + (-|V_{sat}|)}$$

use the absolute maximum swings in the positive and negative directions

V_{out+} , V_{out-} are the desired positive and negative swings
They typically should be equal for symmetric outputs

O-5

$$① \quad I_0 = \frac{|V_{out}|}{R_c}$$

$$② \quad R_{sat} = \frac{V_{DD} - V_T - V_{sat}}{I_0} \approx \frac{V_{DD} - V_T}{I_0}$$

To set $\left(\frac{W}{L}\right)_1$ use V_{out}

$$V_{out} = (V_{DD} - |V_{sat}|)$$

$$③ \quad \left(\frac{W}{L}\right)_1 = \left(\frac{2 \cdot I_0}{k'}\right) \cdot \frac{1}{(V_{DD} - |V_{sat}|)^2}$$

Find the W/L of M1:

$$I_{D1} = I_0 + I_1 = I_0 + \frac{V_{out}}{R_c}$$

O-6

$$\frac{k'}{2} \cdot \left(\frac{W}{L}\right)_1 \cdot (V_{DD} - V_{out} - V_T)^2 = I_0 + \frac{V_{out}}{R_c}$$

$$④ \quad \left(\frac{W}{L}\right)_1 = \frac{2 \cdot \left(I_0 + \frac{V_{out}}{R_c}\right)}{k' \cdot (V_{DD} - V_{out} - V_T)^2}$$

e.g. $R_c = 300 \Omega$ $|V_{out+}| = |V_{out-}| = 3V$

$$V_{DD} = 5V \quad I_0 = 10mA \quad R_{sat} = \frac{3 - 0.7}{10mA} = 230 \Omega$$

$$\left(\frac{W}{L}\right)_1 = \frac{2 \times 10^{-2}}{90 \times 10^{-6} \cdot (5 - 3)^2} = 56$$

$$\left(\frac{W}{L}\right)_1 = \frac{2 \cdot (2 \times 10^{-2})}{90 \times 10^{-6} \cdot (5 - 3 - 0.7)^2} = 263$$

O-7

$$GAIN = \frac{g_m \cdot (R_c \parallel r_o)}{1 + g_m \cdot (R_c \parallel r_o)} \approx \frac{g_m \cdot R_c}{1 + g_m \cdot R_c}$$

$$R_{out} = \frac{1}{g_m} \parallel R_c$$

$$g_m = \left(2 \cdot k' \cdot \frac{W}{L} \cdot I_{D1}\right)^{\frac{1}{2}} = (2 \times 90 \times 10^{-6} \times 263 \times 10^{-2})^{\frac{1}{2}} = 22 \times 10^{-3}$$

$$\frac{1}{g_m} = 45 \Omega$$

$$GAIN = \frac{R_c}{\frac{1}{g_m} + R_c} = \frac{300}{45 + 300} = 0.87$$


$$R_{out} = \frac{1}{g_m} \parallel R_c = 45 \parallel 300 \approx 40 \Omega$$

O-8

$P_{Dissip} = \int V_{Dissip} \cdot (CurrentOut)$

Power @ $V_{out} = 0V$ DC Power without any signal

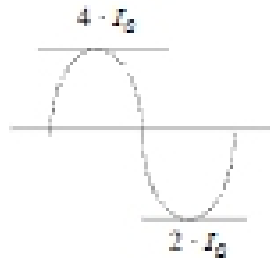$P_{Diss} = (-I_{in}) \cdot (-V_{cc}) + (-I_{in}) \cdot (-V_{ee}) + (I_{out}) \cdot V_{cc}$
 $= 3 \cdot I_Q \cdot V_{cc} = 3 \cdot (10 \times 10^{-4}) \cdot 5 = 150mW$



Average = $3 \cdot I_Q$


Efficiency = $\frac{Power\ to\ Load}{3 \cdot I_Q \cdot V_{cc}}$ (%)

O-9

$V_{Dissip} = V_{cc} |i_{c1} - i_{c2}|$

$V_{ce} = V_{ce} = V_{ce} + \underbrace{\left(\frac{2 \cdot I_{Q2}}{R_L \cdot \frac{1}{R_L}} \right)^2}_{\Delta V} = 0.7 + \left(\frac{2 \times 10 \times 10^{-4}}{90 \times 10^{-3} \times 263} \right) = 1.6V$


Efficiency (Sine Wave)

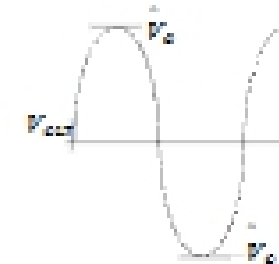

$\hat{V}_c = Peak\ Voltage$

$P_L = \frac{1}{2} \cdot \hat{V}_c \cdot I_Q = \frac{1}{2} \cdot (I_Q \cdot R_L) \cdot I_Q = \frac{1}{2} \cdot I_Q \cdot R_L$
 $= \frac{1}{2} \cdot 10^{-4} \times 300 = 15mW$

O-10

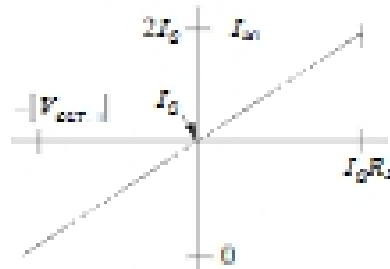

$I_{in} = I_Q + I_{in} = I_Q + \frac{V_{out}}{R_L}$
 $|V_{out}| = |V_{out}|$

$P_{Dissip} = \frac{1}{T_c} \cdot \int_0^{T_c} [(I_{out}(m)) \cdot V_{cc}] dt + 2 \cdot I_Q \cdot |V_{cc}|$
 $= 3 \cdot I_Q \cdot V_{cc} = 150mW$

Efficiency = $\frac{P_{Load}}{Total\ Power} = \frac{15mW}{150mW} = 10\%$
 $= \left(\frac{\frac{1}{2} \cdot I_Q \cdot R_L}{3 \cdot I_Q \cdot V_{cc}} \right) = \frac{1}{6} \cdot \left(\frac{I_Q \cdot R_L}{V_{cc}} \right) < 16\% \text{ MAX}$

O-11

