

This week

- Wednesday
 - **Yell** at you about the exam.
 - Capacitors II
- Friday
 - Finish Caps
 - Start Current and Resistance
- Monday
 - Quiz - Caps & Current (Through Friday's stuff)



Capacitor Circuits

Series

$$\frac{1}{C} = \sum_i \frac{1}{C_i}$$

Parallel

$$C = \sum_i C_i$$
