


Lecture 8

PCAP

Primitives, Combinations, Abstractions, Patterns
 Abstractions reduce complexity by combining multiple primitives into a single entity

Buffers with Op-Amps

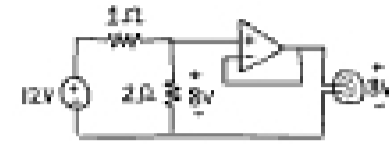Buffers can be used to increase modularity
 The voltage divided on the left acts as a module that produces 8V, regardless of loading of bulb on the right



Patterns


Changing an element changes voltages and currents systematically
 Consider the changes in V_0 and I_0 when R_0 is changed



Check yourself: Patterns

Correct answer: 3

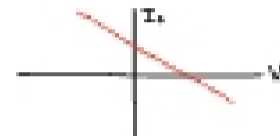The equations for the three leftmost elements are linear



Current-Voltage Relations


The current-voltage relation summarizes all possible behaviors of circuit—regardless of what the circuit is connected to
 We can think about an entire circuit as a single element: a one-port

One-Ports

If a circuit connects to the world via two terminals, then that circuit can be represented by a single generalized element called a one-port
 This is regardless of how many components are in the circuit

This is analogous to

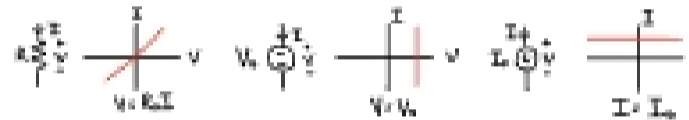- replacing delays, gains, and adders with a system function
- combining a sequence of operations in a procedure call
- combining diverse data in a list



These representations are compositional: they replace multiple elements with a single element that can be used in the same way that primitives are used

Concept Question: Graphing One-Ports

Correct answer: 3



Parallel One-Ports

If the I-V curves for two one-ports are both straight lines, then the I-V curve for the parallel combination is a straight line
 This is because the sum of two straight lines is a straight line

Series One-Ports

If the I-V curves for two one-ports are both straight lines, then the I-V curve for the series combination is a straight line
 This is because the sum of two straight lines is a straight line


Thevenin Equivalents

If the current-voltage relation is linear, the current-voltage relation is the same as that for a voltage source in series with a resistor

From the circuit, $I = \frac{V - V_0}{R}$

If $I = 0$, the $V = V_0$ (the x-intercept of the plot)

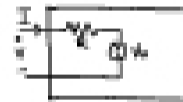The rate of growth of $I = \frac{V - V_0}{R}$ with V is the slope $1/R$.




Norton Equivalents

If the current-voltage relation is linear, the current-voltage relation is the same as that for a current source in parallel with a resistor

From the circuit, $V = I_0 R$

If $I = 0$, the $I = I_0$ (the y-intercept of the plot)

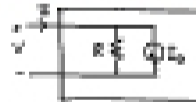The rate of growth of $I = \frac{V}{R}$ with V is the slope $1/R$.



Open-Circuit Voltage and Short-Circuit Current

If a one-port contains just resistors and current and voltage sources, then its I-V relation is determined by two points

First point: open-circuit voltage $V = V_0 = 1V$

Second point: closed-circuit current $I = I_0 = -\frac{1}{2}A$

The equivalent resistance is the slope $R = \frac{V_0}{I_0} = 2\Omega$



Conceptual Value of Equivalent Circuits

Equivalent circuits have conceptual values


Example: Will closing the switch increase or decrease I?

Replace the parts to the left and right of I by equivalent circuits

Equivalent circuit to the right of I depends on the state of the switch

Closing the switch decreases equivalent resistance to the right of I

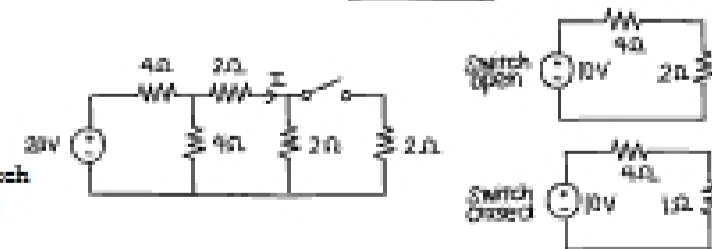Therefore, closing the switch increases I



Consequences of Linearity

If a one-port contains just linear elements (resistors, voltage sources, and current sources) then the current-voltage relation will be linear and it can be represented by a Thevenin or Norton equivalent circuit

Linear one-ports can be characterized by two points on their I-V curve

Op-Amps as Abstractions

We have treated op-amps as fundamental building blocks for circuits, but op-amps are in fact complicated circuits, but op-amps are in fact complicated circuits that contain dozens of transistors and resistors plus a few capacitors