

Example:

$$\begin{cases} \mathcal{E} = 1.5 \text{ V} \\ R = 2 \Omega \\ \Delta V_R = 1.4 \text{ V} \end{cases}$$

Given the circuit on the right, calculate the internal resistance of the battery.

Analysis: $\mathcal{E} = Ir + IR$, need to calculate current I

Solution: Current in the circuit:

$$I = \frac{\Delta V_R}{R} = \frac{1.4}{2.0} = 0.7 \text{ A}$$

$$\mathcal{E} = Ir + IR \Rightarrow Ir = \mathcal{E} - IR$$

$$\Rightarrow r = \frac{\mathcal{E} - \Delta V_R}{I} = \frac{1.5 - 1.4}{0.7} = 0.14 \Omega$$

Example

(2) What is the current passing through the 5 Ω resistor?

Solution: Current passing the 5 Ω resistor is the same as the total current:


$$I = \frac{\mathcal{E}}{R_{eq}} = \frac{75}{25} = 3 \text{ A}$$

(3) What is the voltage drop across the 5 Ω resistor?

$$\Delta V_{5\Omega} = IR = 3 \times 5 = 15 \text{ V}$$

(4) What is the current passing through the 30 Ω resistor?

- try it yourself.

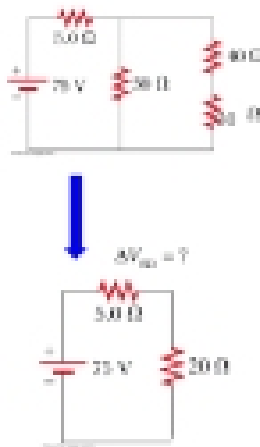

Example

What is the power delivered to resistor R_1 ? $P = I^2 R_1$

(a) Calculate the current I through the resistors:

$$I = \frac{\Delta V}{R_{eq}} = \frac{6}{18} = 0.33 \text{ A}$$

Current is the same for all resistors in series.


This current is the same for all four resistors.

(b) Power consumed by resistor R_1 :

$$\text{Power} = I^2 R_1 = (0.33)^2 \times 2 = 0.22 \text{ W}$$


What is the voltage drop ΔV_1 across resistor R_1 ?

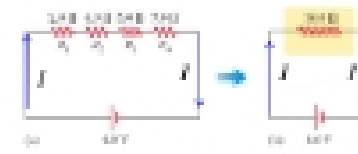From Ohm's law: $\Delta V_1 = IR_1 = 0.33 \times 2.0 = 0.67 \text{ V}$



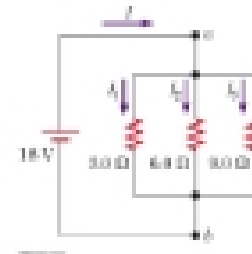Example

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \quad R_{eq} = 1.64 \Omega$$



Power delivered to each resistor

$$P_1 = \frac{(\Delta V)^2}{R_1} = \frac{18^2}{3} = 108 \text{ W}$$

$$P_2 = \frac{(\Delta V)^2}{R_2} = \frac{18^2}{6} = 54 \text{ W}$$

$$P_3 = \frac{(\Delta V)^2}{R_3} = \frac{18^2}{9} = 36 \text{ W}$$

Total power $P = P_1 + P_2 + P_3 = 198 \text{ W}$

Another way of calculating the total power $P = \frac{(\Delta V)^2}{R_{eq}} = 198 \text{ W}$

Kirchhoff's Rules

Loop Rule: The sum of the potential differences across all the elements around any closed circuit loop must be zero

Loop abcd:


$$\Delta V + \Delta V_1 + \Delta V_2 = 0$$

$$\Delta V = V_b - V_a = \mathcal{E}$$





$$\Delta V_1 = V_c - V_b = -IR_1$$

$$\Delta V_2 = V_d - V_c = -IR_2$$

- Note the sign

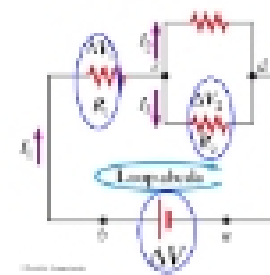

More about the Loop Rule

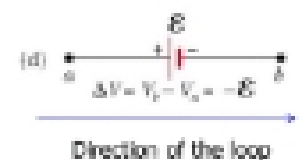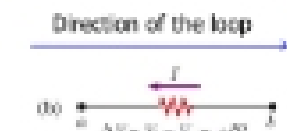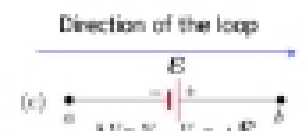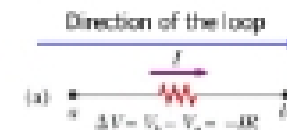

Example: Loop Rule

Loop ABCDA

$$\Delta V_{loop} = V_b - V_a = \mathcal{E} = 30 \text{ V}$$

$$\Delta V_1 = V_c - V_b = -IR_1$$


$$\Delta V_{loop} = V_d - V_c = -\mathcal{E}_2 = -10 \text{ V}$$

$$\Delta V_2 = V_a - V_d = -IR_2$$


Loop rule: $\Delta V_{loop} + \Delta V_{loop} + \Delta V_1 + \Delta V_2 = 0$

$$30 - IR_1 - 10 - IR_2 = 0 \Rightarrow 40 - IR_1 - IR_2 = 0$$
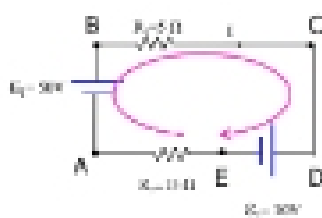
$$\Rightarrow 40 = IR_1 + IR_2 \Rightarrow I = \frac{40}{R_1 + R_2} = \frac{40}{20} = 2 \text{ A}$$



Example - Kirchhoff's Rules

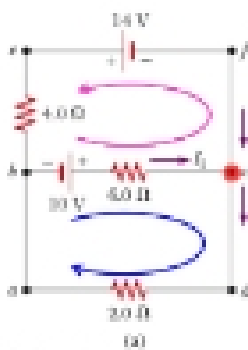

Finally, we have

$$\text{Junction rule: } I_1 + I_2 = I_3 \quad (1)$$

$$\text{Loop rule 1): } 12 - 3I_1 + 2I_2 = 0 \quad (2)$$

$$\text{Loop rule 2): } 5 - 3I_2 - I_3 = 0 \quad (3)$$

Three unknown, three equations:

$$\begin{cases} I_1 + I_2 = I_3 & (1) \\ 12 - 3I_1 + 2I_2 = 0 & (2) \\ 5 - 3I_2 - I_3 = 0 & (3) \end{cases}$$

$$\begin{cases} I_1 + I_2 = I_3 & (1) \\ 12 - 3I_1 + 2I_2 = 0 & (2) \\ 5 - 3I_2 - I_3 = 0 & (3) \end{cases}$$

Example - Kirchhoff's Rules

(a) Loop rule: (a) Loop 1 (loop bcfeb)

$$\Delta V_{loop, bcfeb} = 10 \text{ V}$$

$$\Delta V_{loop} = -I_1 \times 6$$

$$\Delta V_{loop, bcfeb} = 14 \text{ V}$$


$$\Delta V_{loop} = +I_2 \times 4$$

Loop rule: $\sum \Delta V = 0$

$$10 - 6I_1 + 14 + 4I_2 = 0$$

$$\Rightarrow 24 - 6I_1 + 4I_2 = 0 \quad (\text{divide both sides by 2})$$

$$\Rightarrow 12 - 3I_1 + 2I_2 = 0$$

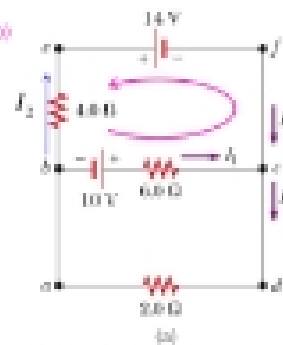

Example - Kirchhoff's Rules

$$\begin{cases} I_1 + I_2 = I_3 & (1) \\ 12 - 3I_1 + 2I_2 = 0 & (2) \\ 5 - 3I_2 - I_3 = 0 & (3) \end{cases}$$

From eq (1): $I_3 = I_1 + I_2$

Eliminate I_3 from eq (3) using eq (1)

$$5 - 3I_2 - (I_1 + I_2) = 0$$

$$5 - 4I_2 - I_1 = 0$$

$$I_1 = 5 - 4I_2$$

Substitute the above into eq (2)

$$12 - 3(5 - 4I_2) + 2I_2 = 0$$

$$22 - 11I_2 = 0$$

$$I_2 = 2 \text{ A}$$

$$\Rightarrow I_1 = 5 - 4I_2 = -3 \text{ A}$$

$$\begin{cases} I_1 = 2 \text{ A} \\ I_2 = -3 \text{ A} \\ I_3 = I_1 + I_2 = -1 \text{ A} \end{cases}$$

Example

(i) Time constant of the circuit

$$\tau = RC = (8 \times 10^3) \times (5 \times 10^{-6}) = 4.0 \text{ s}$$


(ii) Maximum charge on the capacitor after the switch is closed

$$Q = \mathcal{E}C = 12 \times (5 \times 10^{-6}) = 60 \times 10^{-6} \text{ C} = 60 \mu\text{C}$$

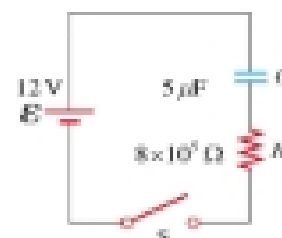(iii) Charge on the capacitor at $t = 6 \text{ sec}$ (the switch is closed when $t = 0$)

$$q(t) = Q(1 - e^{-t/\tau})$$

$$q(t = 6s) = Q(1 - e^{-6/4}) = (60 \times 10^{-6}) \times (1 - e^{-1.5}) = 4.7 \times 10^{-5} \text{ C}$$




(4) Potential difference across the resistor at $t = 6 \text{ sec}$

a. potential drop across the capacitor at $t = 6 \text{ sec}$:

$$\Delta V_C = \frac{q}{C} = \frac{4.7 \times 10^{-5}}{5 \times 10^{-6}} = 9.3 \text{ V}$$

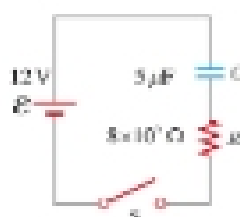b. potential drop across the resistor

$$\mathcal{E} = \Delta V_R + \Delta V_C \Rightarrow \Delta V_R = \mathcal{E} - \Delta V_C = 12 - 9.3 = 2.7 \text{ V}$$



(5) The current passing the resistor at $t = 6 \text{ sec}$: Ohm's law

$$\begin{aligned} I(t = 6s) &= \frac{\Delta V_R}{R} \\ &= \frac{2.7}{8 \times 10^3} \\ &= 3.4 \times 10^{-4} \text{ A} \end{aligned}$$

$$\begin{cases} \tau = 4 \text{ s} \\ Q = 60 \mu\text{C} \\ q(t = 6s) = 4.7 \times 10^{-5} \text{ C} \end{cases}$$