

**PROBLEM SET #2**

Issued: Tuesday, Feb.1, 2011

Due: Tuesday, Feb.8, 2011, 5:00 p.m. in the EE 140 homework box in 240 Cory

- Use inspection analysis to write expressions for the input resistance  $R_i$ , output resistance  $R_o$ , and gain  $v_o/v_s$  for each of the amplifiers in Fig PS2.1. The expressions should be in terms of the given elements and parameters of the small-signal equivalent circuits (i.e.,  $g_m$ ,  $r_p$ ,  $r_o$ ,  $\beta$ , etc.) for the transistors used. For each circuit, assume that all capacitors shown have infinite values.

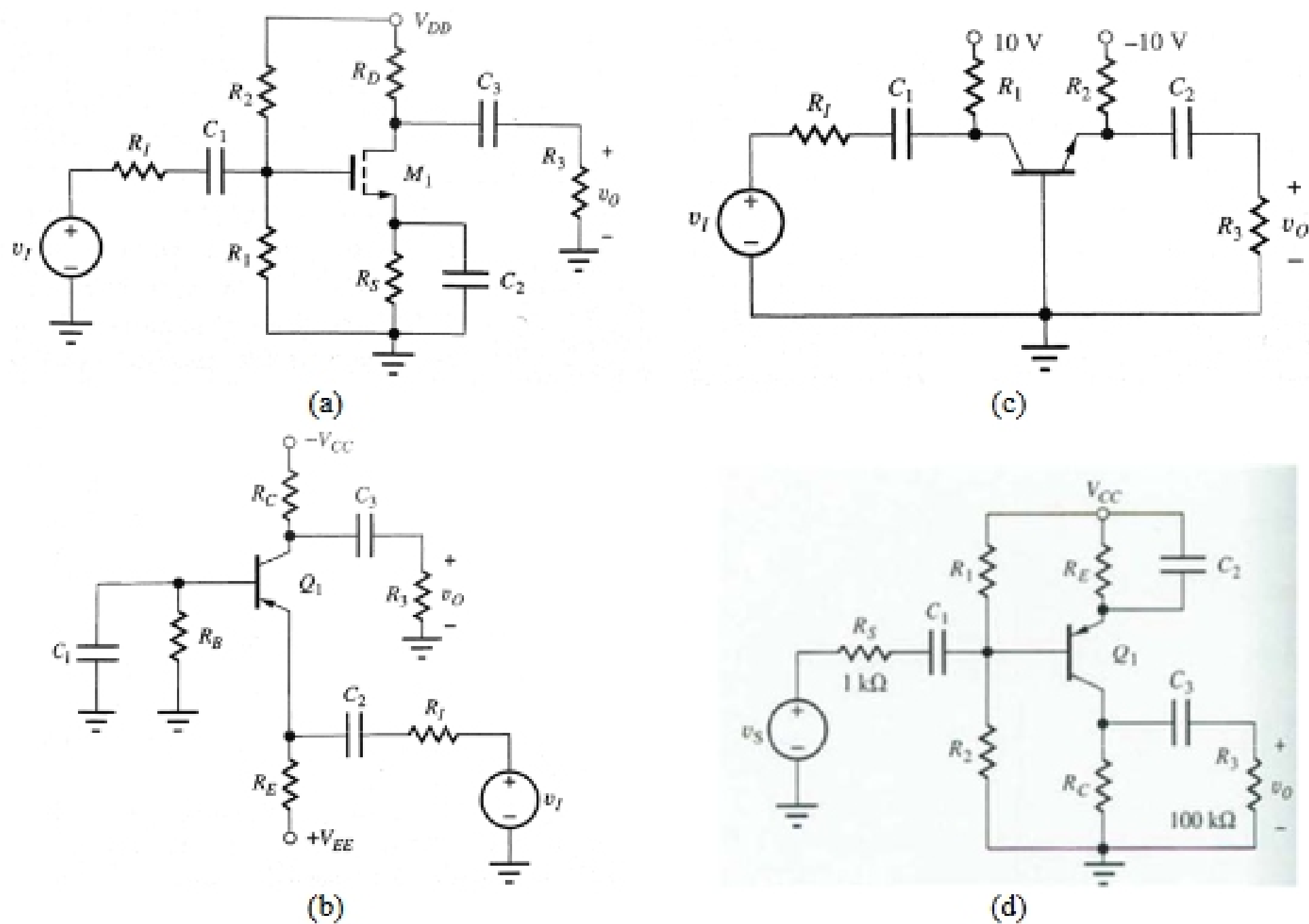


Fig. PS2.1

- Find the input resistance  $R_i$  and the voltage gain  $v_o/v_s$  of the circuit in Fig. PS2.2 using inspection analysis. Explain the purpose of the 100 k $\Omega$  resistor.

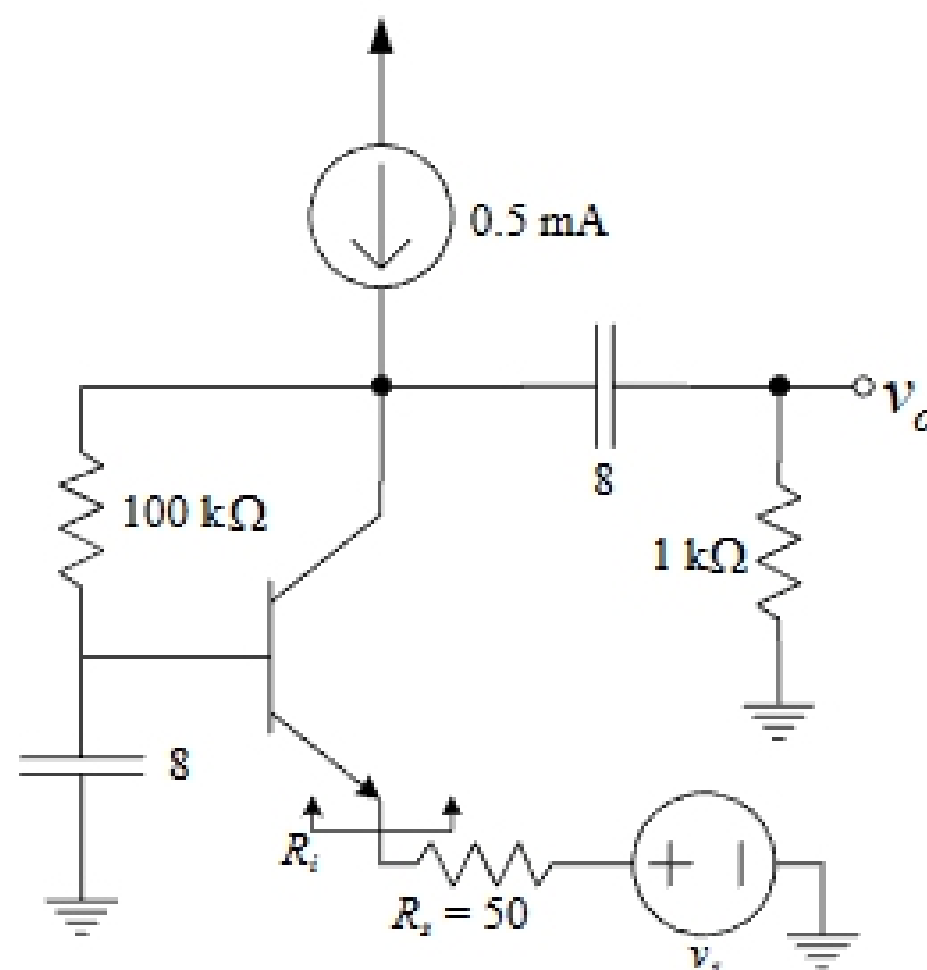


Fig. PS2.2

3. The BJT  $\beta$  values of the BJT in the emitter follower of Fig. PS2.3 may range from 20 to 200. For each extreme ( $\beta = 20$  and  $\beta = 200$ ), find:
- $I_E$ ,  $V_E$ ,  $V_B$
  - $R_i$
  - $v_o/v_s$

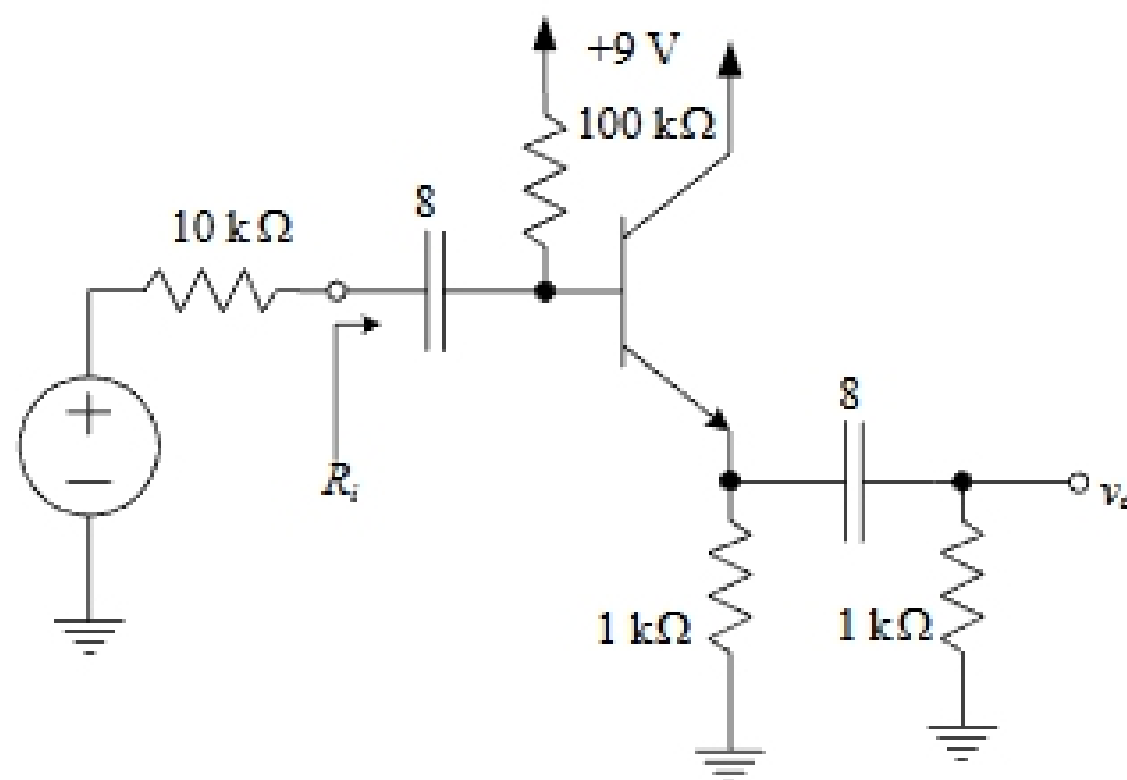


Fig. PS2.3

4. For the circuit in Fig. PS2.4, let transistor  $Q_1$  have  $\beta = 20$  and transistor  $Q_2$  have  $\beta = 200$ , and neglect the effect of  $r_o$ . Use  $V_{BE} = 0.7$  V.

- Find the DC emitter current of  $Q_1$  and  $Q_2$ . Also find the DC voltages  $V_{B1}$  and  $V_{B2}$ .
- If a load resistance  $R_L = 1\text{ k}\Omega$  is connected to the output terminal, find the voltage gain from the base to the emitter of  $Q_2$ ,  $v_o/v_{b2}$ , and find the input resistance looking into the base of  $Q_2$ ,  $R_{ib2}$ .
- Replacing  $Q_2$  with its input resistance  $R_{ib2}$  found in (b), analyze the circuit of emitter follower  $Q_1$  to determine its input resistance  $R_i$ , and the gain from its base to its emitter,  $v_{e1}/v_{b1}$ .
- If the circuit is fed with a source having a  $100\text{ k}\Omega$  resistance, find the transmission to the base of  $Q_1$ ,  $v_{b1}/v_s$ .
- Find the overall voltage gain  $v_o/v_s$  including the resistances added in parts b and d.

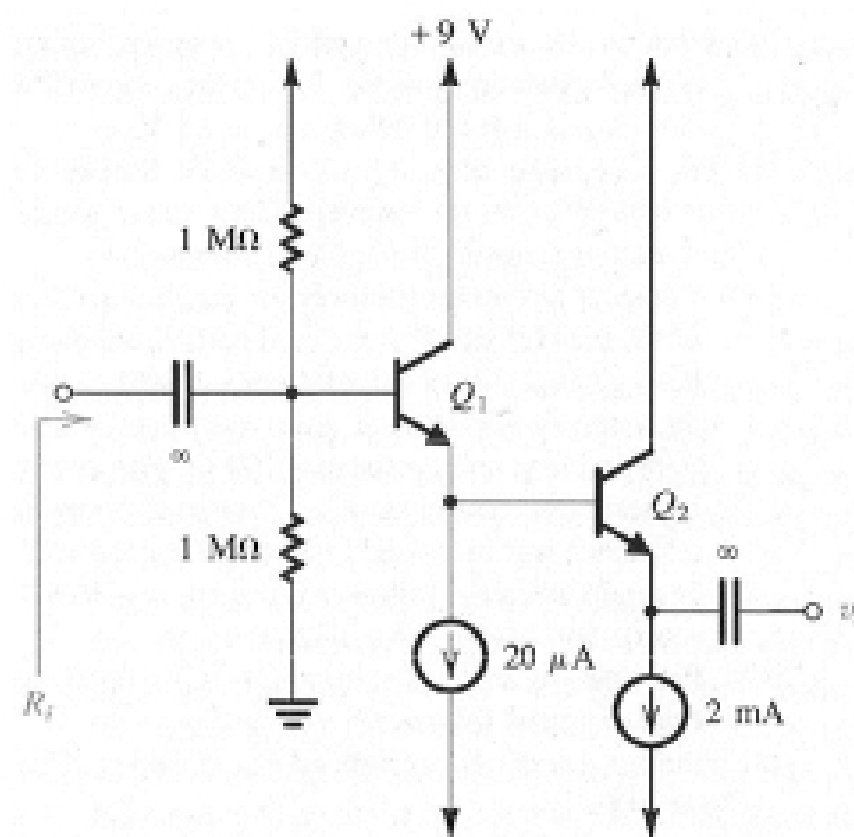


Fig. PS2.4

- Calculate the output resistance  $r_o^c$  of the circuit in Fig. PS2.5 as a function of  $I_{BIAS}$ . Do not neglect  $r_{o1}$  or  $r_{o2}$  in this calculation, but you may neglect  $r_b$  and  $r_u$ . If  $I_{C2} = 1\text{ mA}$ , what is  $r_o^c$  for  $I_{BIAS} = 1\text{ mA}$ ? For  $I_{BIAS} = 0$ ?

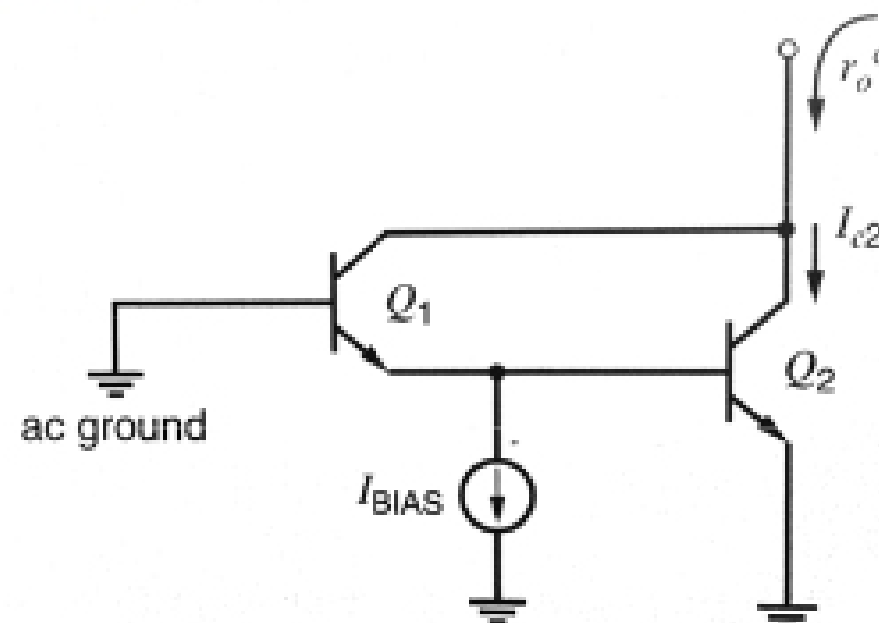


Fig. PS2.5