

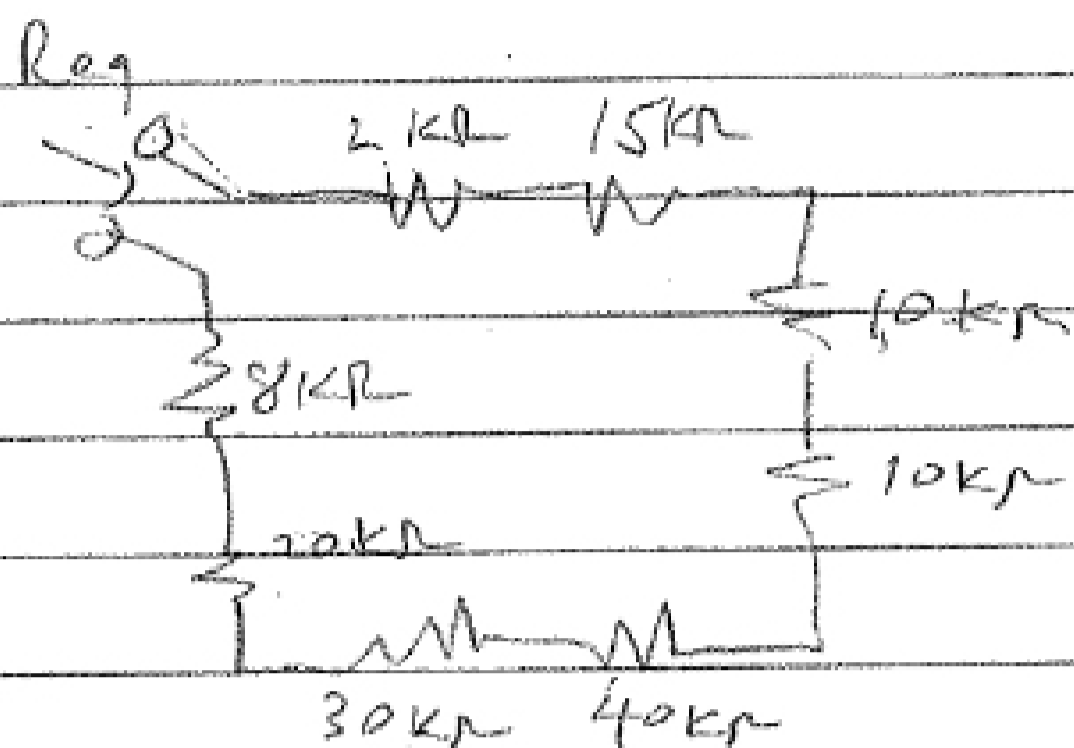




2-46

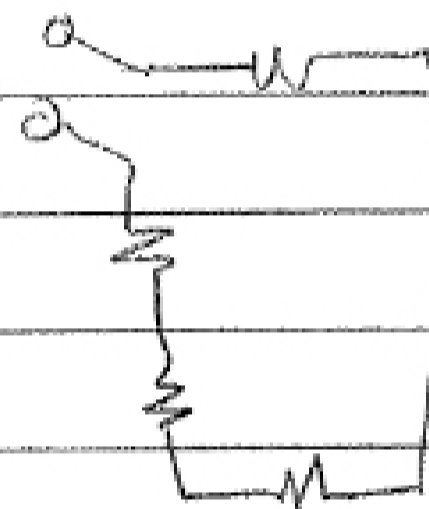

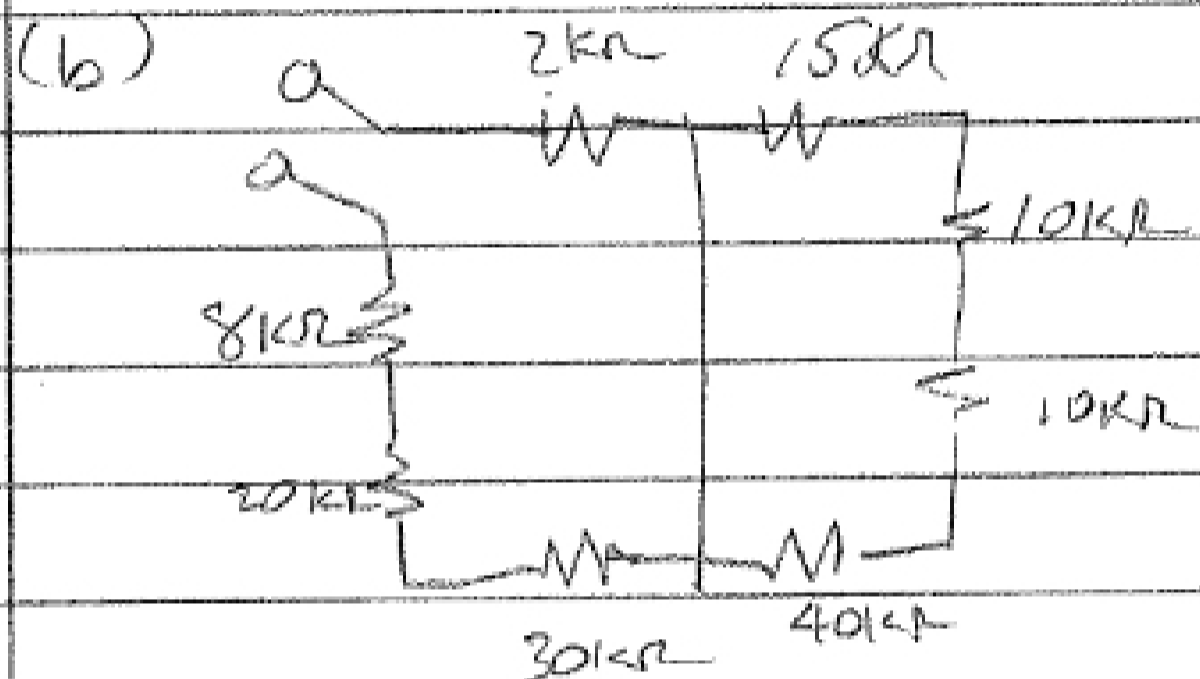$R_{eq} = \sum R$ since all are in series
 $= 135 k\Omega$




$R_{eq} = 60 k\Omega$

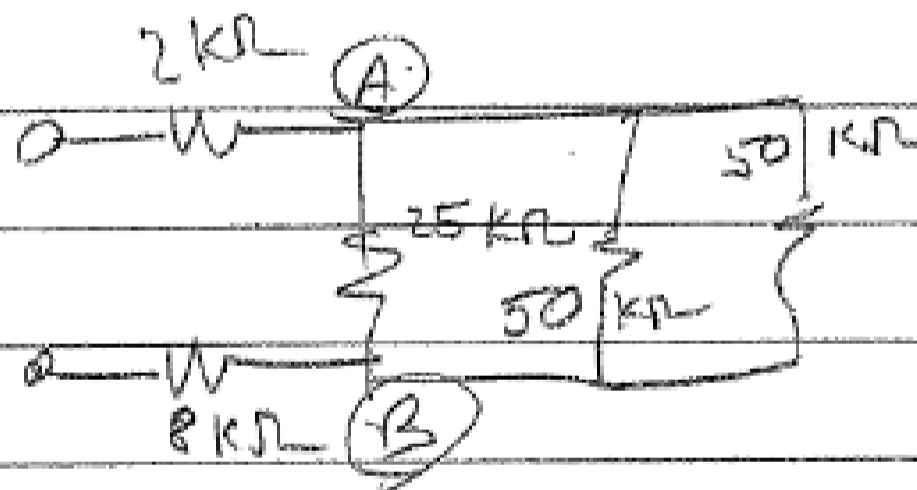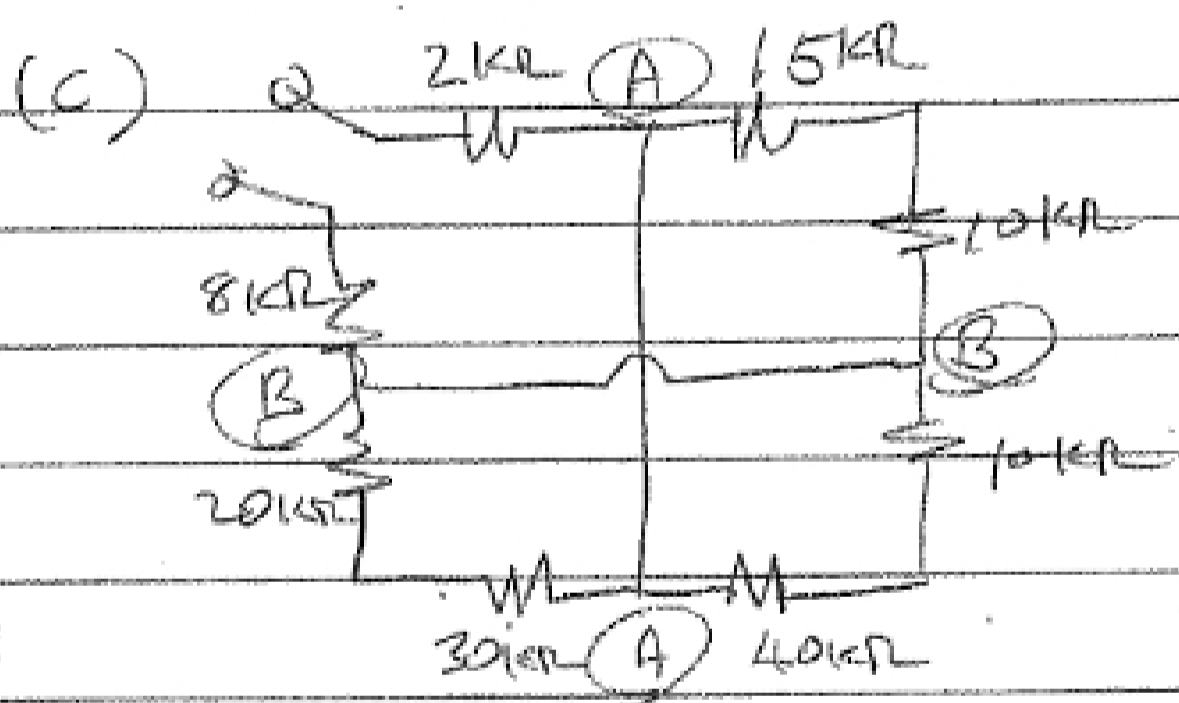

$R_{eq} = 10 k\Omega + 25 \parallel 50 \parallel 50 k\Omega$
 $= 22.5 k\Omega$

(with $P_{5k} = 10 P_{in}$)

2-62

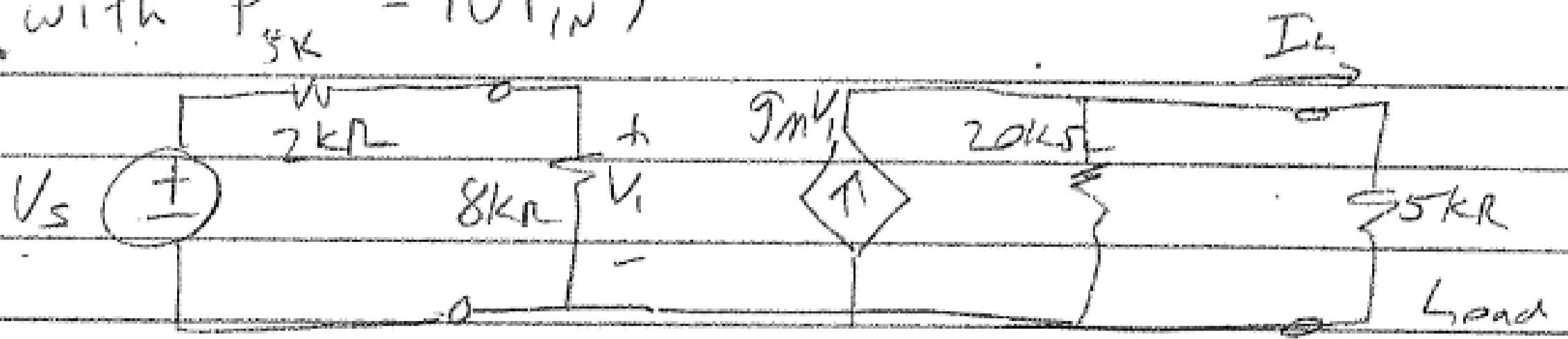

$$P_{5k\Omega} = I_L^2 R_L$$

where $R_L = 5k\Omega$

$$I_L = g_m V_1 \frac{0.2 \text{ mS}}{0.2 \text{ mS} + 0.05 \text{ mS}}$$

$$= 0.8 g_m V_1$$

$$P_{5k\Omega} = (0.8 g_m V_1)^2 R_L$$


$$P_{in} = \frac{V_1^2}{8k\Omega}$$

$$\frac{P_{5k\Omega}}{P_{in}} = \frac{(0.8 g_m V_1)^2 R_L}{V_1^2 / 8k\Omega}$$

$$= 0.64 g_m^2 (5k\Omega) 8k\Omega = 10$$

$$g_m = \sqrt{\frac{10}{(0.64)(5k\Omega)(8k\Omega)}} = 0.625 \text{ mS}$$

2-63

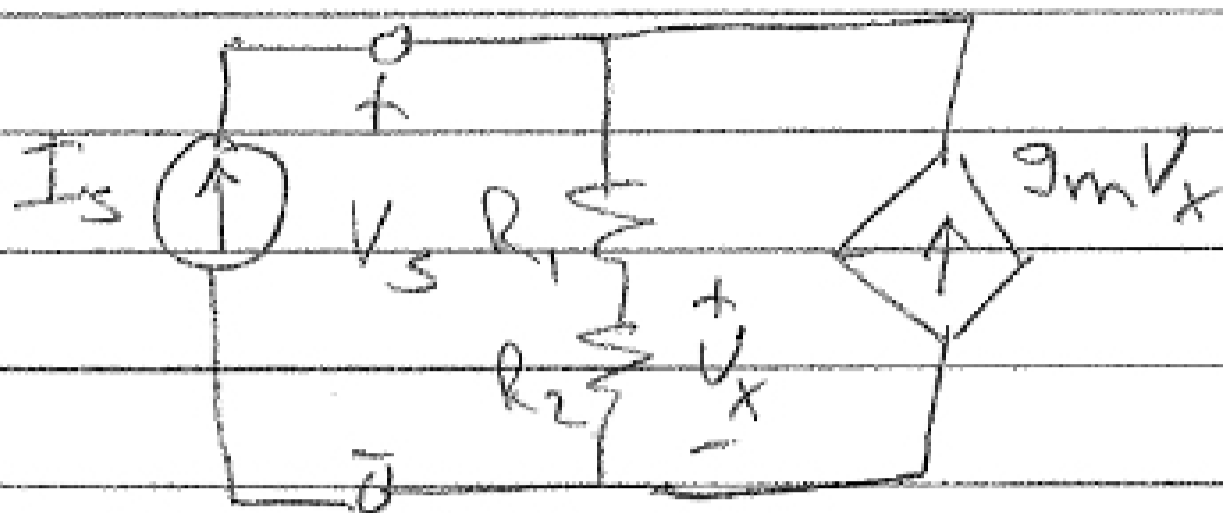

Use KCL at top node:

$$-I_s + \frac{V_s}{R_1 + R_2} - g_m V_x = 0$$

$$V_x = V_s \frac{R_2}{R_1 + R_2} \quad \text{by Voltage Division}$$

$$-I_s + \frac{V_s}{R_1 + R_2} - g_m V_s \frac{R_2}{R_1 + R_2} = 0$$

$$-I_s + V_s \left[\frac{1}{R_1 + R_2} - \frac{g_m R_2}{R_1 + R_2} \right] = 0$$

$$-I_s + V_s \left(\frac{1 - g_m R_2}{R_1 + R_2} \right) = 0$$

$$G_{eq} = \frac{I_s}{V_s} = \boxed{\frac{1 - g_m R_2}{R_1 + R_2} = G_{eq}}$$

$$R_{eq} = G_{eq}^{-1} = \boxed{\frac{R_1 + R_2}{1 - g_m R_2} = R_{eq}}$$

For $R_1 = 1 \text{ k}\Omega$, $R_2 = 3 \text{ k}\Omega$, $g_m = 0.2 \text{ mS}$

$$G_{eq} = \frac{1 - (0.2 \text{ mS})(3 \text{ k}\Omega)}{4 \text{ k}\Omega} = \boxed{0.1 \text{ mS} = G_{eq}}$$

$$R_{eq} = G_{eq}^{-1} = \boxed{10 \text{ k}\Omega = R_{eq}}$$