

CS152  
Computer Architecture and Engineering  
Lecture 5

The Design Process

February 10, 2003

John Kubiatowicz ([www.cs.berkeley.edu/~kubitron](http://www.cs.berkeley.edu/~kubitron))


lecture slides: <http://www-inst.eecs.berkeley.edu/~cs152/>

2/10/03

©UCB Spring 2003

CS152 / Kubiatowicz  
Lect. 5

 Review: recall General C/L Cell Delay Model



Combinational Cell (symbol) is fully specified by:

- functional (input  $\rightarrow$  output) behavior
  - truth-table, logic equation, VHDL
- load factor of each input
- critical propagation delay from each input to each output for each transition
  - $T_{iL}(A, \alpha) = \text{Fixed Internal Delay} + \text{Load-dependent-delay} \times \text{load}$

Linear model composes

2/10/03

©UCB Spring 2003

CS152 / Kubiatowicz  
Lect. 5

Review: Storage Element's Timing Model




- Setup Time: Input must be stable BEFORE trigger clock edge
- Hold Time: Input must REMAIN stable after trigger clock edge
- Clock-to-Q time:
  - Output cannot change instantaneously at the trigger clock edge
  - Similar to delay in logic gates, two components:
    - Internal Clock-to-Q
    - Load dependent Clock-to-Q
- Typical for class: 1ns Setup, 0.5ns Hold

2/10/03

©UCB Spring 2003

CS152 / Kubiatowicz  
Lect. 5

Review: Critical Path & Cycle Time

 

- Critical path: the slowest path between any two storage devices
- Cycle time is a function of the critical path
- must be greater than:
  - $\text{Clock-to-Q} + \text{Longest Path through Combination Logic} + \text{Setup}$


2/10/03

©UCB Spring 2003

CS152 / Kubiatowicz  
Lect. 5

## Review: Tricks to Reduce Cycle Time

### Reduce the number of gate levels

 


### Use ascert/dynamic timing methods

### Pay attention to loading

- One gate driving many gates is a bad idea
- Avoid using a small gate to drive a long wire
 
### Use multiple stages to drive large load



2/10/03

©UCB Spring 2003

CS152 / Rubinfeld  
Lect.5

## Review: Karnaugh Map for easier simplification


$S_0$	$S_1$	$C$	$S_0'$	$S_1'$
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	1	0
1	0	1	1	1
1	1	0	1	1
1	1	1	0	0

$S_0$	00	01	11	10
0	0	1	1	0
1	1	0	0	1

$$S_0 = (\overline{S_0} \cdot C) + (S_0 \cdot \overline{C})$$

$S_1$	00	01	11	10
0	0	0	1	1
1	0	1	0	1
 
$$S_1 = (\overline{S_1} \cdot S_0 \cdot C) + (S_1 \cdot \overline{C}) + (S_1 \cdot \overline{S_0})$$



2/10/03

©UCB Spring 2003

CS152 / Rubinfeld  
Lect.6

## Review: DeMorgan's theorem: Push Bubbles and Morph

### NAND Gate



$$\text{Out} = \overline{A \cdot B} = \overline{A} + \overline{B}$$

### NOR Gate



$$\text{Out} = \overline{A + B} = \overline{A} \cdot \overline{B}$$



2/10/03


©UCB Spring 2003

CS152 / Rubinfeld  
Lect.7
 
## Review: Integrated Circuit Costs

$$\text{Die cost} = \frac{\text{Wafer cost}}{\text{Dies per Wafer} \cdot \text{Die yield}}$$

$$\text{Dies per wafer} = \frac{\pi \cdot (\text{Wafer diam.})^2}{\text{Die Area}} - \frac{\pi \cdot \text{Wafer diam.}}{\sqrt{2} \cdot \text{Die Area}} - \text{test dies} \approx \frac{\text{Wafer Area}}{\text{Die Area}}$$



$$\text{Die Yield} = \frac{\text{Wafer yield}}{\left\{ 1 + \frac{\text{Defects per unit area} \cdot \text{Die Area}}{\alpha} \right\}^2}$$

Die Cost goes roughly with (die area)<sup>3</sup> or (die area)<sup>4</sup>

2/10/03

©UCB Spring 2003

CS152 / Rubinfeld  
Lect.8

## The Design Process

### "To Design is To Represent"

Design activity yields description/representation of an object

- Traditional craftsman does not distinguish between the conceptualization and the artifact
- Separation comes about because of *complexity*
- The concept is captured in one or more representation languages
- This process is design


### Design Begins With Requirements

- **Functional Capabilities:** what it will do
- **Performance Characteristics:** Speed, Power, Area, Cost, ...

## Design Process (cont.)
 
### Design Finishes As Assembly

- Design understood in terms of components and how they have been assembled
- Top Down *decomposition* of complex functions (behaviors) into more primitive functions
- bottom-up *composition* of primitive building blocks into more complex assemblies



*Design is a "creative process," not a simple method*

## Design Refinement

Informal System Requirement

Initial Specification

Intermediate Specification

Final Architectural Description

Intermediate Specification of Implementation


Final Internal Specification

Physical Implementation

refinement  
increasing level of detail



## Design as Search

 

Design Involves educated guesses and verification

- Given the goals, how should these be prioritized?
- Given alternative design pieces, which should be selected?
- Given design space of components & assemblies, which part will yield the best solution?

**Feasible (good) choices vs. Optimal choices**