

# EECS150 - Digital Design

## Lecture 11 - Combinational Logic Circuits


### Part 1 - Adders

October 1, 2002

John Wawrzynek

# Adders

Full-adder cell (FA) revisited:

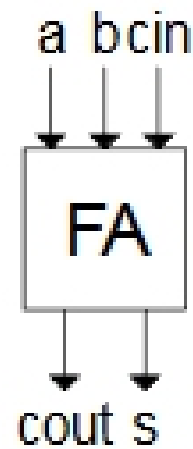

a	b	cin	cout	s
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

cin	ab			
	00	01	11	10
0				
1				

cout

cin	ab			
	00	01	11	10
0				
1				


s

# Carry-ripple Adder


- Each cell:

$$r_i = a_i \text{ XOR } b_i \text{ XOR } c_{in}$$
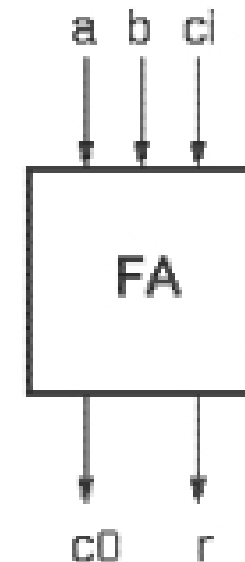
$$c_{out} = a_i c_{in} + a_i b_i + b_i c_{in} = c_{in}(a_i + b_i) + a_i b_i$$



- 4-bit adder:

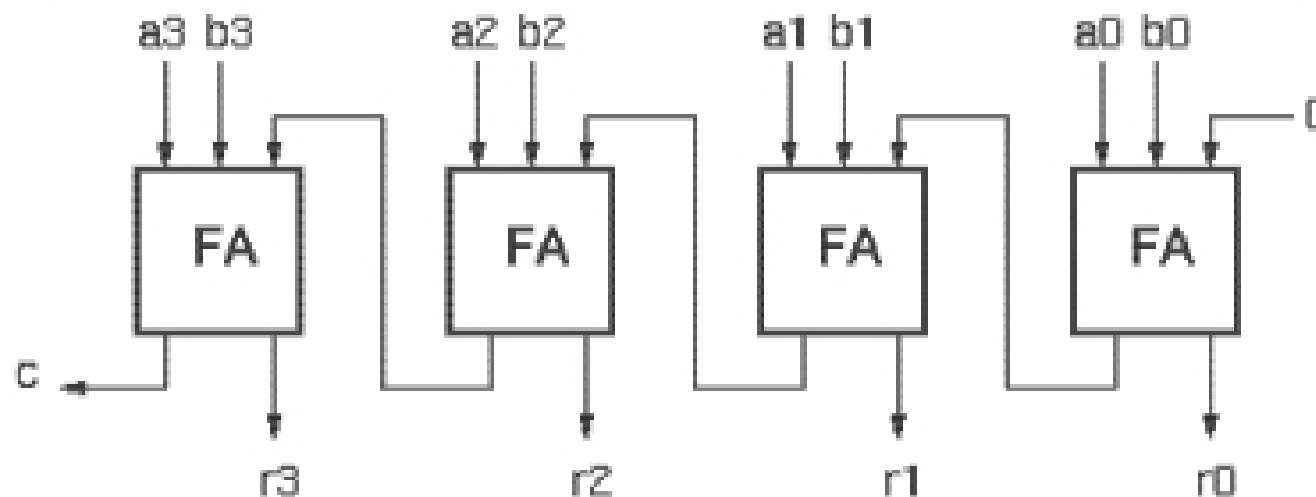

“Full adder cell”

- What about subtraction?