

# Lecture 5


Borja Peleato

- Dependent and real sources
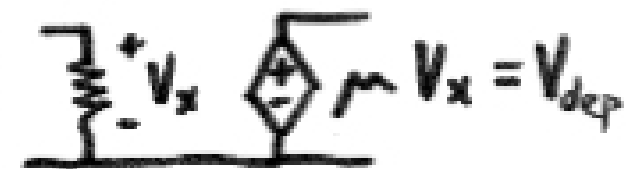
# Dependent sources

- Do not exist as such, just a model for other elements (e.g. amplifiers)
- Their value depends on other quantities in the circuit
- Four types: (see P39 of the book)

– Voltage controlled voltage source (VCVS)



– Current controlled current source (CCCS)



– Voltage controlled current source (VCCS)

- Transconductance parameter (unit S)


$$g_m \text{ units } \frac{A}{V} = \text{Siemens}$$



– Current controlled voltage source (CCVS)

- Transresistance parameter (unit  $\Omega$ )
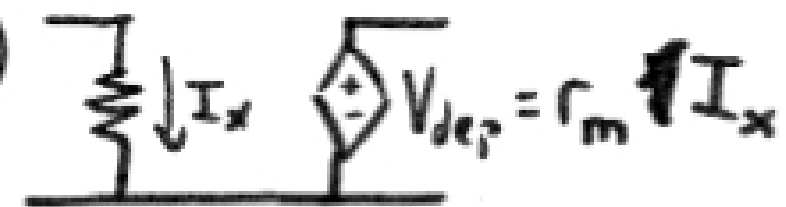
$$r_m \text{ units } \frac{V}{A} = \text{Ohm}$$



- Usually drawn with a shared terminal, but not necessary




# Real sources


- Ideal sources are represented by:

– Voltage  Current 

– Assumed to provide constant V or I, regardless of what is connected to them

– Capable of delivering infinite power

  $10V$   $\oplus$   $\ominus$   $R$  • Deliver  $\frac{100}{R}$  W for  $R$  as small as desired

  $10A$   $\uparrow$   $R$  • Deliver  $100R$  W for  $R$  as large as desired

- Real sources behave like an ideal source with an


internal resistor (No symbol for them)


– Voltage ( $R_s$  very small, ideally 0)

- Is almost ideal for loads  $\gg R_s$


– Current ( $R_s$  very large, ideally  $\infty$ )

- Is almost ideal for loads  $\ll R_s$

*Real source*  
  $V_s$   $R_s$   
 If connected to a large  $R_L$ , it delivers  $V_s$  as promised. If connected to small  $R_L$ , it delivers less (e.g. if  $R_L = R_s$  it delivers  $V_s/2$ ).

*Real source*  
  $I_s$   $R_s$   
 Delivers  $I_s$  if connected to small  $R_L$ , but less for

– Some of the power gets wasted in the internal resistor big load

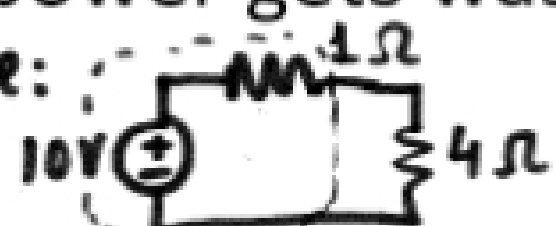For example:   $10V$   $\oplus$   $\ominus$   $1\Omega$   $4\Omega$

Source generates  $10 \cdot 2 = 20W$  but only  $8 \cdot 2 = 16W$  are consumed by  $4\Omega$  resistor.