

**6.012 Microelectronic Devices and Circuits
Spring 2005**

April 20, 2005
Quiz #2

	<u>Problem #points</u>
NAME _____	1 _____
RECITATION TIME _____	2 _____
	3 _____
	Total _____

General guidelines (please read carefully before starting):

- Make sure to write your name on the space provided above.
- Open book: you can use any material you wish. But no computers.
- All answers should be given in the space provided. Please do not turn in any extra material.
- You have 120 minutes to complete the quiz.
- Make reasonable approximations and *state them*, i.e. low-level injection, extrinsic semiconductor, quasi-neutrality, etc.
- Partial credit will be given for setting up problems without calculations. NO credit will be given for answers without reasons.
- Use the symbols utilized in class for the various physical parameters, i.e. N_a , τ , ϵ , etc.
- Pay attention to problems in which *numerical answers* are expected. An algebraic answer will not accrue full points. Every numerical answer must have the proper *units* next to it. Points will be subtracted for answers without units or with wrong units. In situations with a defined axis, the *sign* of the result is also part of the answer.

Unless otherwise stated, use:

$$q = 1.6 \times 10^{-19} \text{ C}$$


$$kT/q = 25 \text{ mV at room temperature}$$

$$n_i = 10^{10} \text{ cm}^{-3} \text{ for silicon at room temperature}$$

$$\epsilon_{\text{Si}} = 10^{-12} \text{ F/cm} \quad \epsilon_{\text{ox}} = 3.45 \times 10^{-13} \text{ F/cm}$$

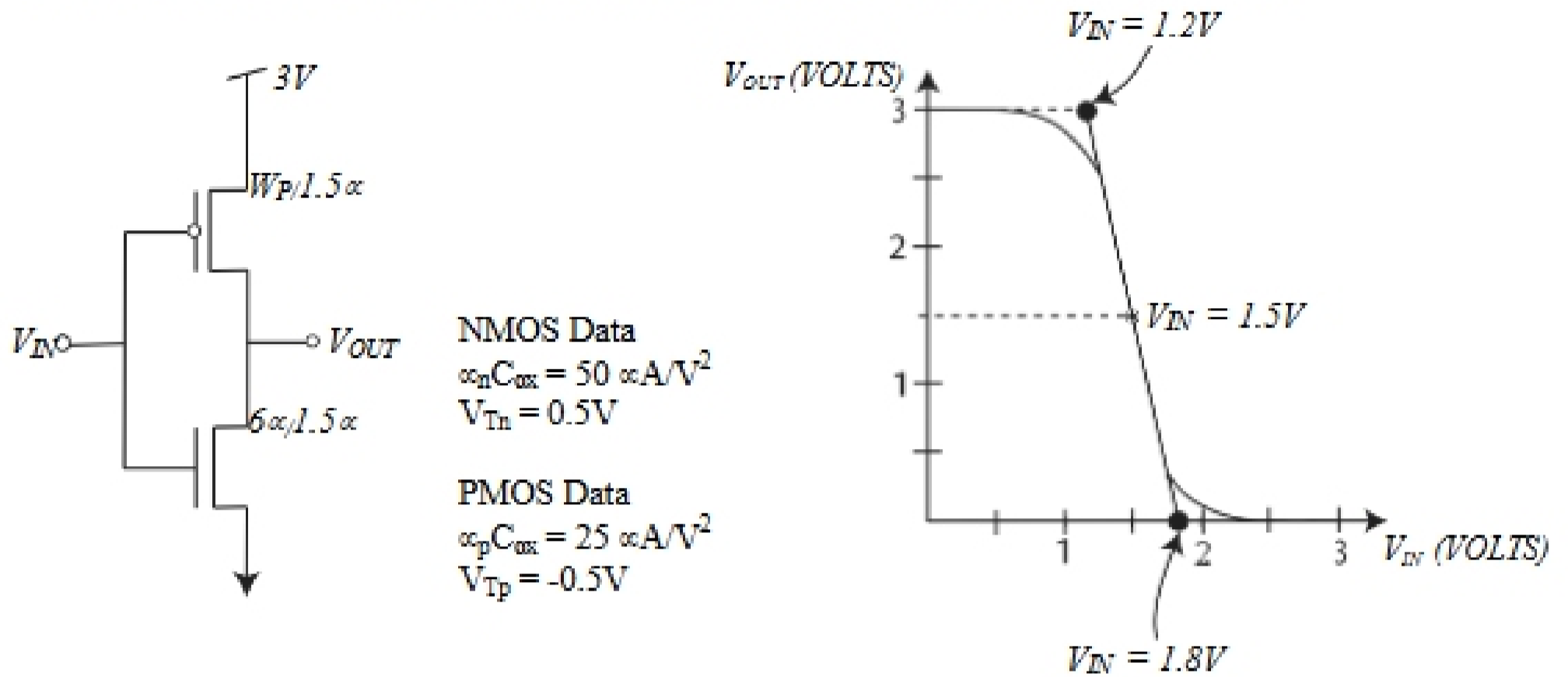1. (30 points)

A CMOS inverter has the following voltage transfer characteristics and transistor data.



a) Calculate W_p such that $-I_{Dp} = I_{Dn} = 100\mu A$ at $V_{IN} = V_M$.

b) Calculate the NMOS transconductance, $g_{m,n}$, at $V_{IN} = V_M$.

c) Calculate $(\lambda_n + \lambda_p)$.