

PROBLEM SET #4

Issued: Tuesday, Feb.15, 2011

Due: Tuesday, Feb.22, 2011, 5:00 p.m. in the EE 140 homework box in 240 Cory

- Write the expressions for the gain of each circuit in Fig. PS4.1 at very low and very high frequencies. Neglect other capacitances and assume $\lambda = 0$ for circuits (a) and (b) and $\gamma = 0$ for all of the circuits. The expressions should be in terms of the given elements and parameters of the small-signal equivalent circuits (i.e., g_m , r_o , etc.) for the transistors used.

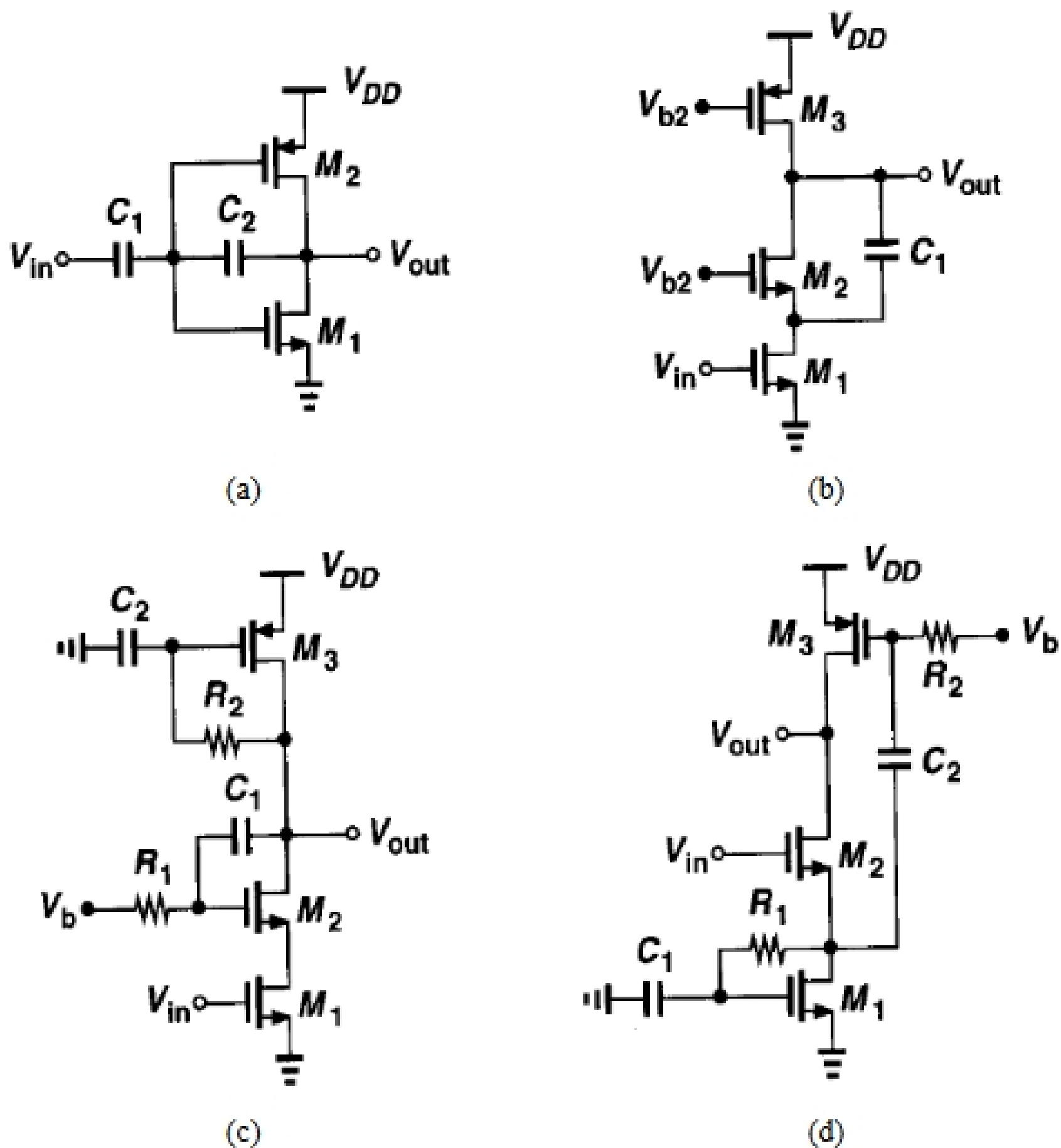


Fig. PS4.1

2. The circuit of Fig. PS4.2 produces a supply insensitive current. Calculate the ratio of small-signal variations in I_{BIAS} to small-signal variations in V_{DD} at low frequencies. Ignore the body effect but include finite transistor r_o in this calculation.

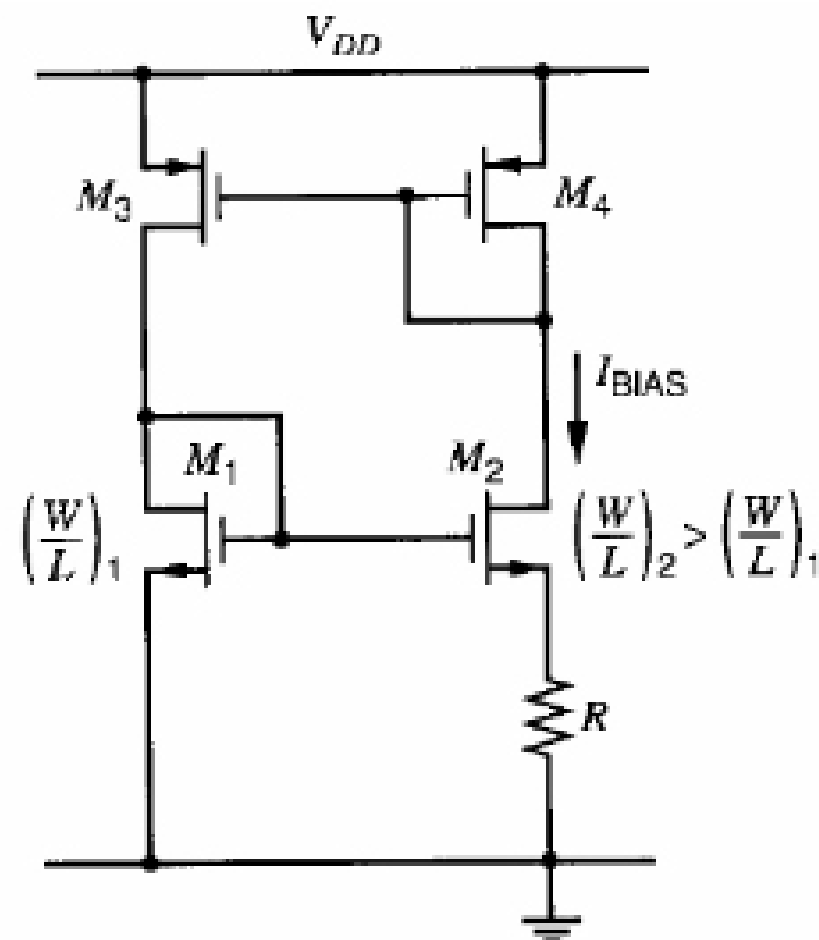


Fig. PS4.2

3. Consider the circuit of Fig. PS4.3, assuming $(W/L)_{1-3} = 40/0.5$, $I_{REF} = 0.3\text{mA}$, and $\gamma = 0$.

Use the following parameters for your calculation if necessary:

$$V_{th0} = 0.7\text{V}, 2\Phi_F = 0.9\text{V}, L_D = 0.08\mu\text{m}, \mu_{n0} = 350\text{cm}^2/\text{Vs}, \lambda = 0.1\text{V}^{-1}, t_{ox} = 9\text{nm}$$

- Determine V_b such that $V_X = V_Y$;
- If V_b deviates from the value calculated in part a by 100mV , what is the mismatch between I_{out} and I_{REF} ?
- If the circuit fed by the cascode current source changes V_P by 1V , how much does V_Y change.

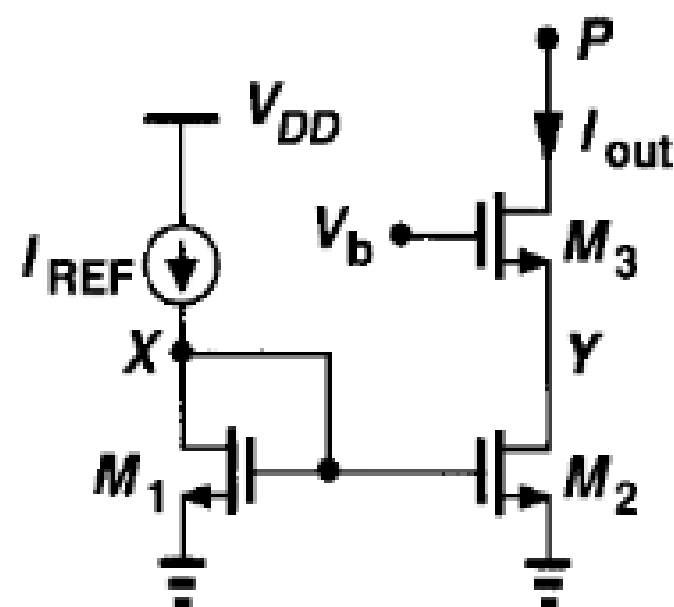


Fig. PS4.3

4. A BICMOS amplifier is shown in Fig. PS4.4. Calculate the small-signal voltage gain v_o/v_i . Assume $I_S = 10^{-16}$ A, $\beta_F = 100$, $r_b = 0$, $V_A \rightarrow \infty$, $\mu_n C_{ox} = 200 \mu\text{A/V}$, $V_t = 0.6\text{V}$, and $\lambda = 0$.

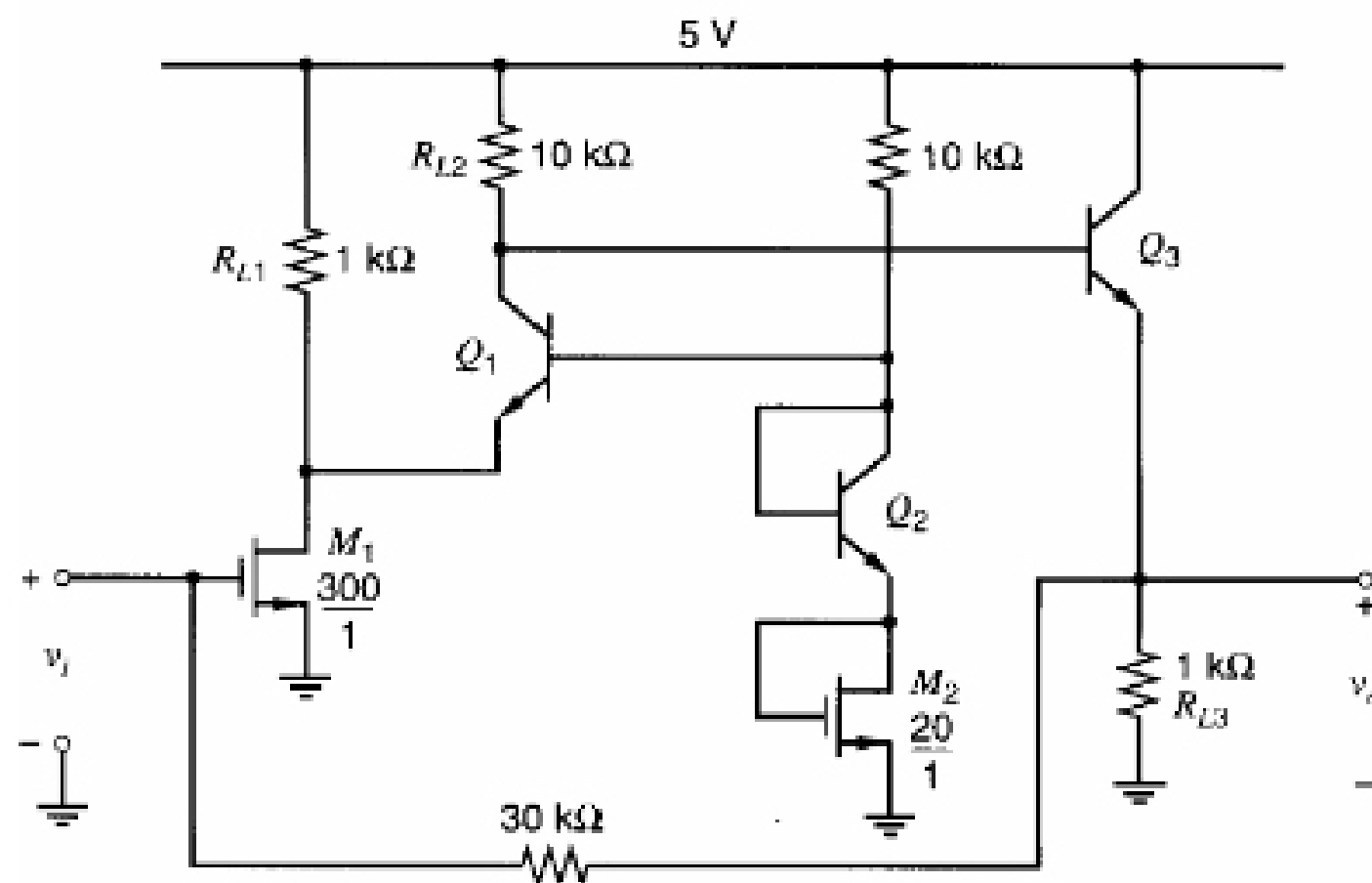


Fig. PS4.4