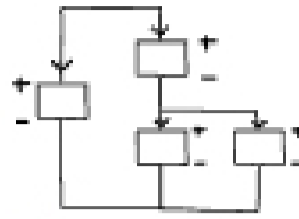


Lecture 7

Last Time: The Circuit Abstraction

- Circuits represent systems as connections of elements
 - through which currents (through variables) flow
 - across which voltages (across variables) develop



Last Time: Analyzing Circuits


- Circuits are analyzed by combining three types of equations
 - KVL: sum of voltages around any closed path is zero
 - KCL: sum of currents out of any closed surface is zero

Element (constitutive) equations

- Resistor: $V = IR$
- Voltage Source: $V = V$
- Current Source: $I = I$

Many KVL and KCL equations are redundant

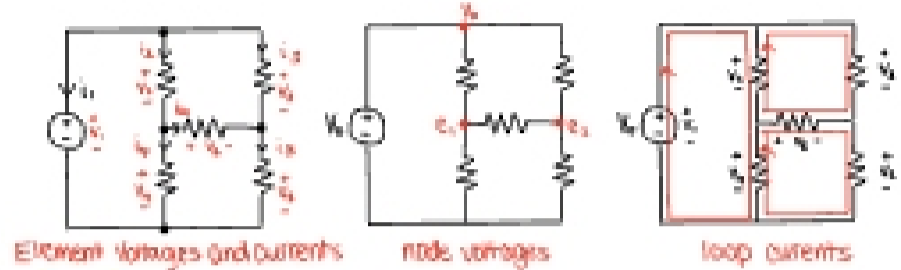We looked at three methods to systematically identify a linearly independent set




Check yourself: Analyzing Circuits

- Correct answer: 2 and 3
- How many of the following are true?
 - $V_3 - 2V_1 = i_3 R_3 = -i_3 R_3$
 - $i_1 + i_2 + i_3 = 0$
 - $v_2 + v_3 + v_4 = v_1 + v_4 + v_1$
 - $i_2 - i_4 = i_2 - i_2$
 - $\frac{5v_1 - v_2}{R_1} + \frac{6v_2 - v_3}{R_2} + \frac{v_3}{R_3} + \frac{v_4}{R_4} = 0$

Interaction of Circuit Elements

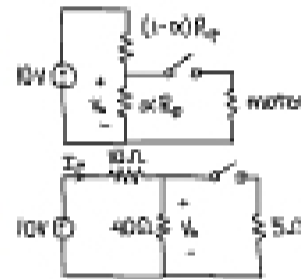- Circuit design is complicated by interactions among the elements
- Adding an element changes voltages and currents throughout the circuit
- Example: closing a switch is equivalent to adding a new element



Concept Question: Closing a switch

- Correct answer: 3
- By closing the switch, V decreased by more than a factor of 1000

Buffering with Op-Amps

- Interactions between elements can be reduced (or eliminated) by using an op-amp as a buffer
- Opening and closing the switch has no effect on I or V
- When the switch is closed, the voltage across the motor is the same as the voltage at the input to the op-amp



Dependent Sources

- To analyze op-amps, we must introduce a new kind of element: a dependent source
- A dependent source generates a voltage or current whose value depends on another voltage or current
- Example: current-controlled current source

Check yourself: Dependent Sources

- Correct answer: 4
- $V_2/V_1 = 1/2$



Dependent sources are two-ports: characterized by two equations

By contrast, one-ports (resistors, voltage sources, current sources) are characterized by a single equation



Op-Amp

An op-amp (operational amplifier) can be represented by a voltage-controlled voltage source

A voltage-controlled voltage source is a two-port


Example: Find V/V_1 for the following circuit

$V_1 = V_i$, $V_2 = \frac{R_2}{R_1 + R_2} V_1$, $V_o = K(V_1 - V_2) \rightarrow V_o = K(V_1 - \frac{R_2}{R_1 + R_2} V_1)$
 $\frac{V_o}{V_1} = \frac{K}{1 + \frac{R_2}{R_1}} = \frac{K(R_1 + R_2)}{R_1 + R_2 + R_2}$, Assuming that K is large, we get $\frac{V_o}{V_1} = \frac{R_1 + R_2}{R_1}$



Non-Inverting Amplifier

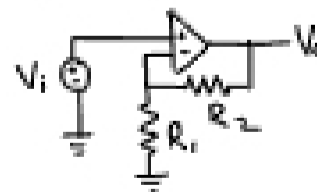- This circuit implements a gain
- For large K , the gain is always greater than or equal to one
- We call this a non-inverting amplifier



Check yourself: Non-Inverting Amplifier

- Correct answer: 4
- $V_o = V_i$ when R_1 is infinity and/or R_2 is zero

The Ideal Op-Amp

The approximation that $V_1 = V_2$ is referred to as the ideal op-amp approximation

