

CS152  
Computer Architecture and Engineering  
Lecture 6  
Multiply, Divide, Shift

February 12, 2003

John Kubiatowicz ([www.cs.berkeley.edu/~kubitron](http://www.cs.berkeley.edu/~kubitron))

lecture slides: <http://www-inst.eecs.berkeley.edu/~cs152/>

2/12/03

©UCB Spring 2003

CS152 / Kubiatowicz  
Lec6.1

Review: Elements of the Design Process

- Divide and Conquer (e.g., ALU)
  - Formulate a solution in terms of simpler components.
  - Design each of the components (subproblems)
- Generate and Test (e.g., ALU)
  - Given a collection of building blocks, look for ways of putting them together that meets requirement
- Successive Refinement (e.g., multiplier, divider)
  - Solve "most" of the problem (i.e., ignore some constraints or special cases), examine and correct shortcomings.
- Formulate High-Level Alternatives (e.g., shifter)
  - Articulate many strategies to "keep in mind" while pursuing any one approach.
- Work on the Things you Know How to Do
  - The unknown will become "obvious" as you make progress.


2/12/03

©UCB Spring 2003

CS152 / Kubiatowicz  
Lec6.2

Review: ALU Design

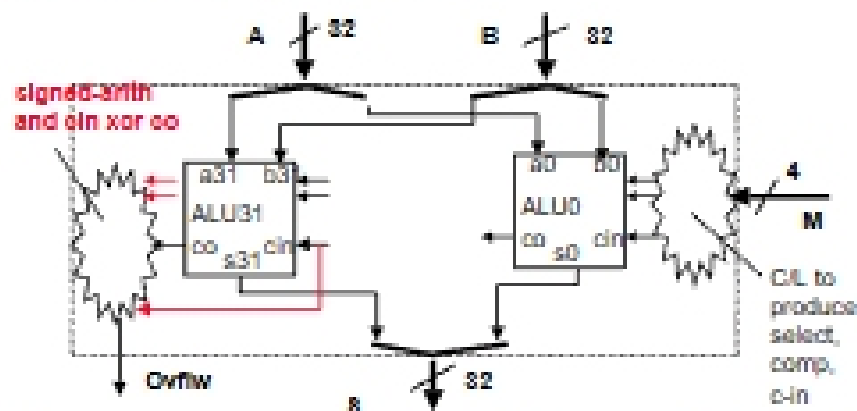- Bit-slice plus extra on the two ends
- Overflow means number too large for the representation
- Carry-look ahead and other adder tricks




2/12/03

©UCB Spring 2003

CS152 / Kubiatowicz  
Lec6.3

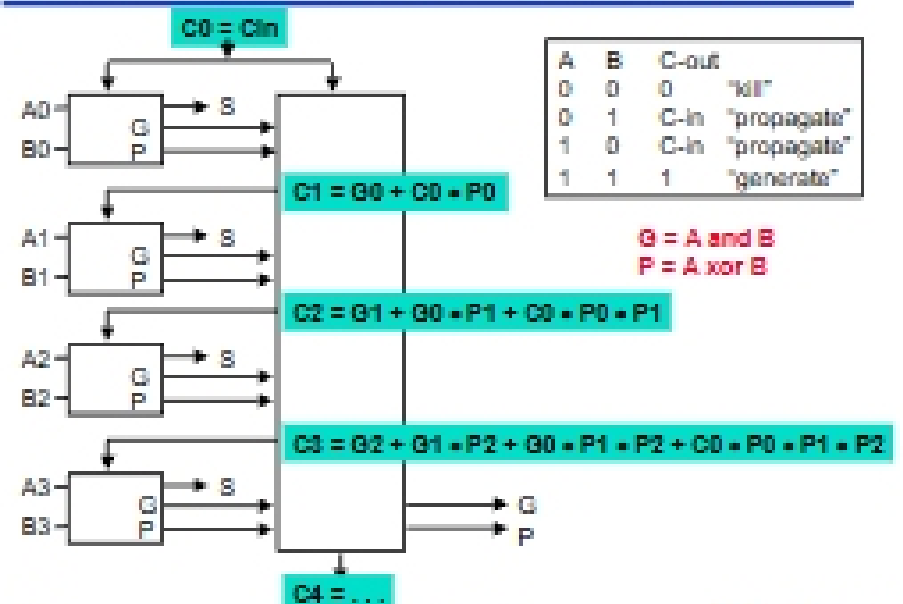Review: Carry Look Ahead (Design trick: peek)




2/12/03

©UCB Spring 2003


CS152 / Kubiatowicz  
Lec6.4

## Review: Design Trick: Guess (or "Precompute")

$$CP(2n) = 2 \cdot CP(n)$$

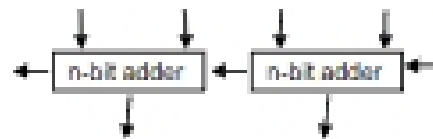

$$CP(2n) = CP(n) + CP(\text{mux})$$

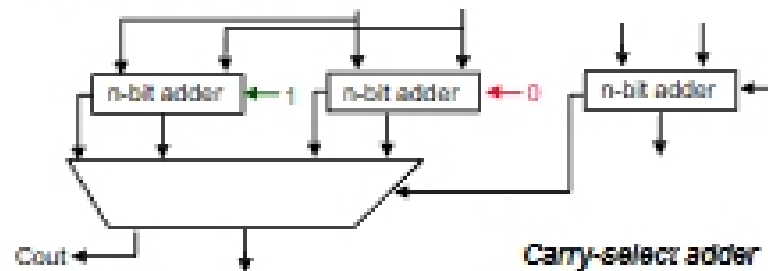


2/12/03

@UCB Spring 2003

CS152 / Rubinfeld  
Lec6.5
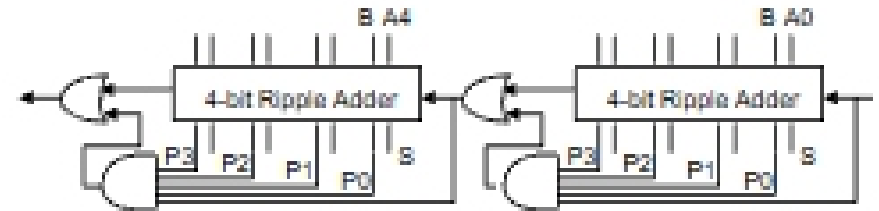
## Review: Carry Skip Adder: reduce worst case delay



Just speed up the slowest case for each block

Exercise: optimal design uses variable block sizes



2/12/03

@UCB Spring 2003

CS152 / Rubinfeld  
Lec6.6

## MIPS arithmetic instructions

| Instruction       | Example           | Meaning                                | Comments                       |
|-------------------|-------------------|--|--------------------------------|
| add               | add \$1,\$2,\$3   | $S1 = S2 + S3$                         | 3 operands; exception possible |
| subtract          | sub \$1,\$2,\$3   | $S1 = S2 - S3$                         | 3 operands; exception possible |
| add immediate     | addi \$1,\$2,100  | $S1 = S2 + 100$                        | + constant; exception possible |
| add unsigned      | addu \$1,\$2,\$3  | $S1 = S2 + S3$                         | 3 operands; no exceptions      |
| subtract unsigned | subu \$1,\$2,\$3  | $S1 = S2 - S3$                         | 3 operands; no exceptions      |
| add imm. unsgn.   | addiu \$1,\$2,100 | $S1 = S2 + 100$                        | + constant; no exceptions      |
| multiply          | mult \$2,\$3      | HI, Lo = $S2 \times S3$                | 64-bit signed product          |
| multiply unsigned | multu \$2,\$3     | HI, Lo = $S2 \times S3$                | 64-bit unsigned product        |
| divide            | div \$2,\$3       | Lo = $S2 / S3$ ,<br>HI = $S2 \bmod S3$ | Lo = quotient, HI = remainder  |
| divide unsigned   | divu \$2,\$3      | Lo = $S2 / S3$ ,<br>HI = $S2 \bmod S3$ | Unsigned quotient & remainder  |
| Move from HI      | mthi \$1          | $S1 = HI$                              | Used to get copy of HI         |
| Move from Lo      | mtlo \$1          | $S1 = Lo$                              | Used to get copy of Lo         |

2/12/03

@UCB Spring 2003

CS152 / Rubinfeld  
Lec6.7

## MULTIPLY (unsigned)

\* Paper and pencil example (unsigned):


Multiplicand

2/12/03

@UCB Spring 2003

CS152 / Rubinfeld  
Lec6.8

## Unsigned Combinational Multiplier

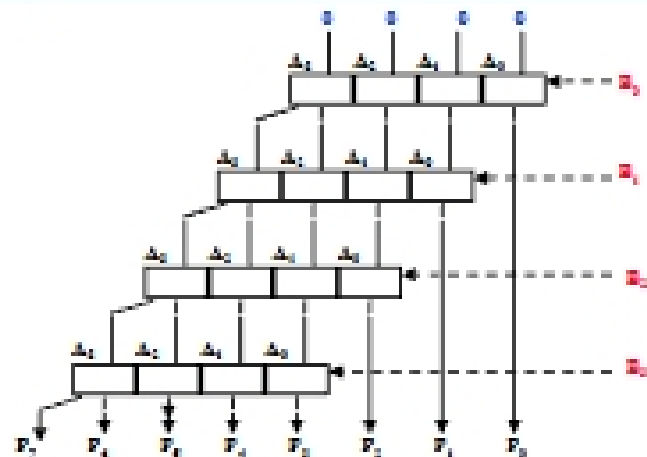


- Stage 1 accumulates  $A * 2^i$  if  $B_i == 1$
- Q: How much hardware for 32 bit multiplier? Critical path?

2/12/03

BUCC Spring 2003

CS152 / Rubinfeld  
Lec0.9

## How does it work?

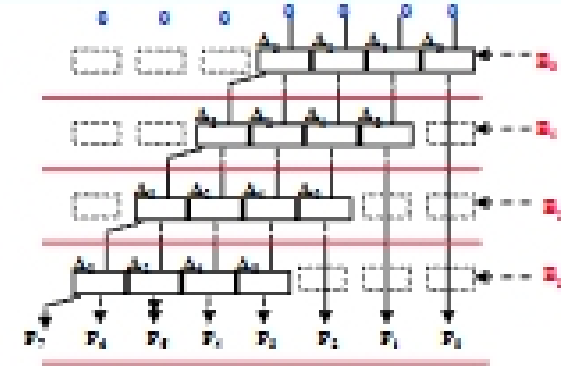

- At each stage shift A left ( $\times 2$ )
- Use next bit of B to determine whether to add in shifted multiplicand
- Accumulate 2n bit partial product at each stage

2/12/03

BUCC Spring 2003


CS152 / Rubinfeld  
Lec0.10

## Carry Save addition of 4 integers

- Adding:
 

|   |   |
|---|---|
| + | A <sub>3</sub> A <sub>2</sub> A <sub>1</sub> A <sub>0</sub> |
| + | B <sub>3</sub> B <sub>2</sub> B <sub>1</sub> B <sub>0</sub> |
| + | C <sub>3</sub> C <sub>2</sub> C <sub>1</sub> C <sub>0</sub> |
| + | D <sub>3</sub> D <sub>2</sub> D <sub>1</sub> D <sub>0</sub> |
|   |   |
|   | S <sub>3</sub> S <sub>2</sub> S <sub>1</sub> S <sub>0</sub> |

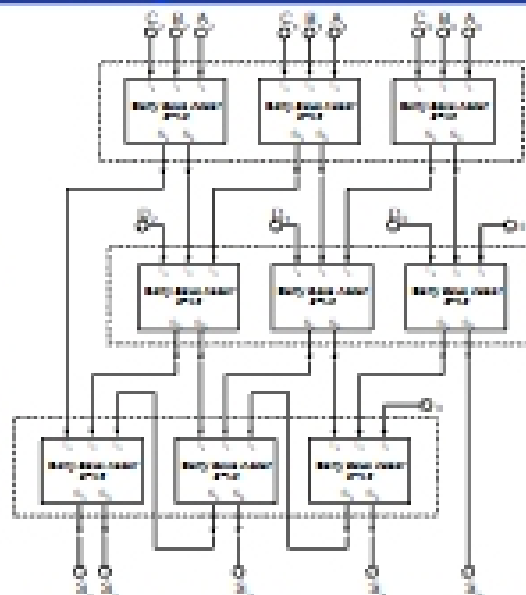- Add Columns first, then rows!
- Full Adder = 3→2 element
- Can be used to reduce critical path of multiply
- Example: 63 bit multiply (for floating point):
  - At least 63 levels with naive technique
  - Only 8 with Carry save addition!




2/12/03

BUCC Spring 2003

CS152 / Rubinfeld  
Lec0.11
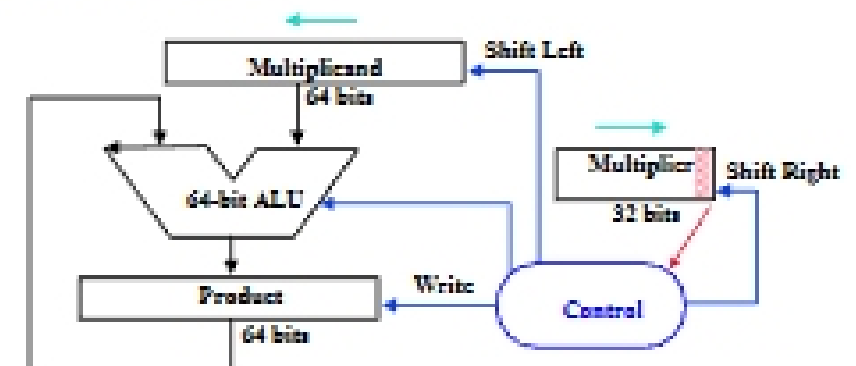
## Unsigned shift-add multiplier (version 1)

- 64-bit Multiplicand reg, 64-bit ALU, 64-bit Product reg, 32-bit multiplier reg



Multiplier = datapath + control

2/12/03

BUCC Spring 2003

CS152 / Rubinfeld  
Lec0.12