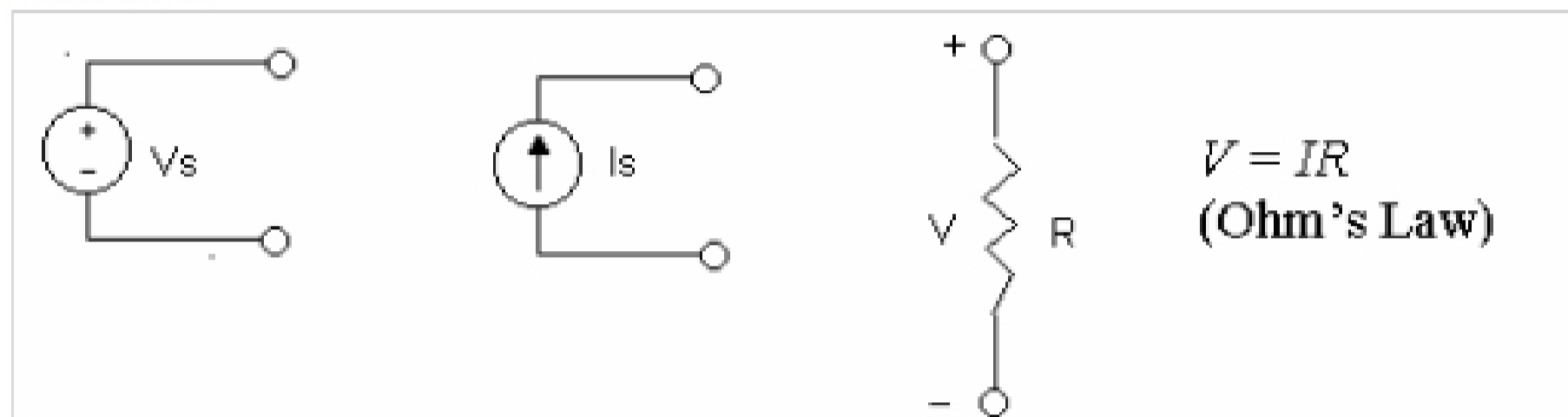


## Applications of the Laplace Transform


### Application in Circuit Analysis

#### 1. Review of Resistive Network


##### 1) Elements




##### 2) Superposition

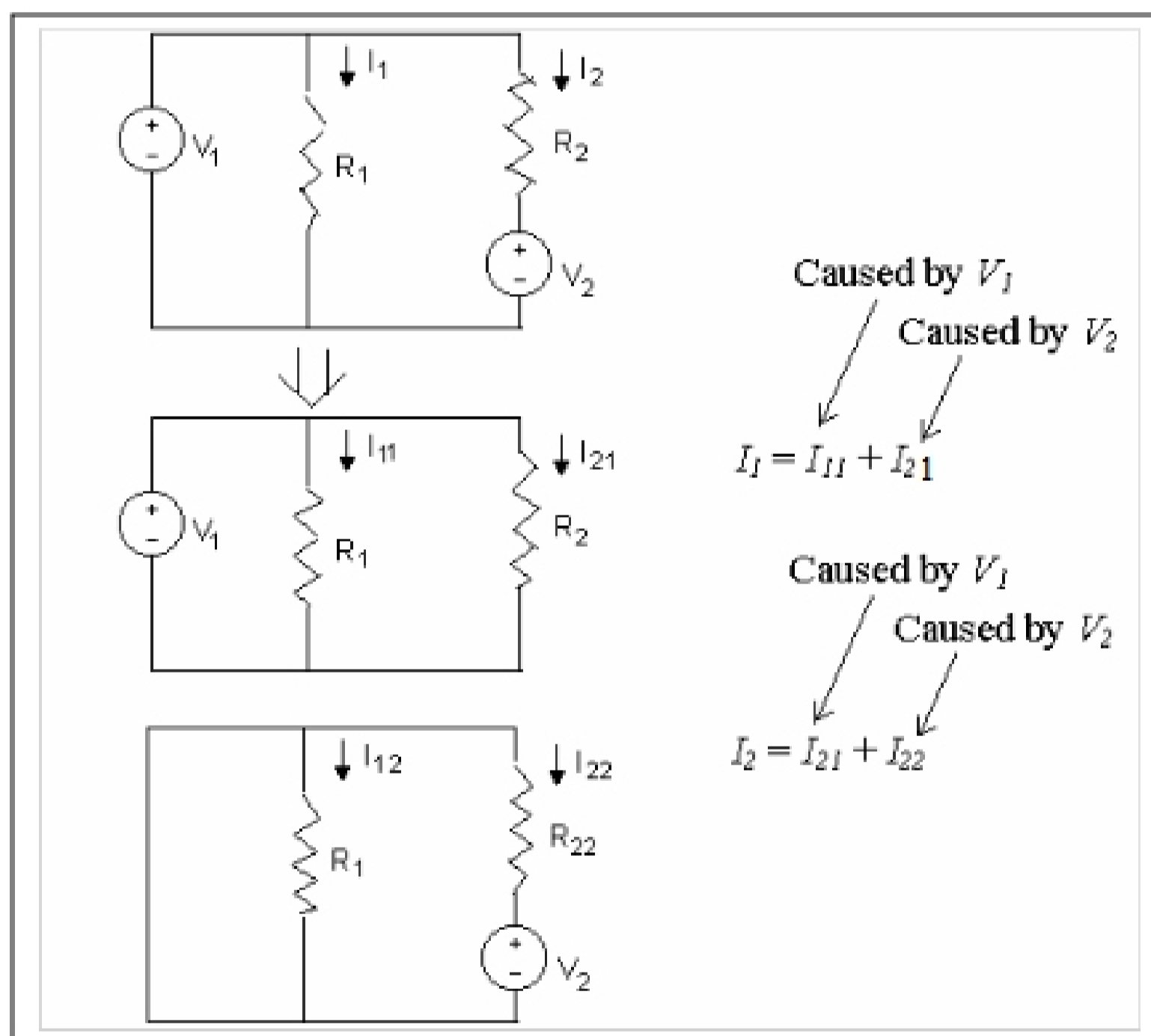

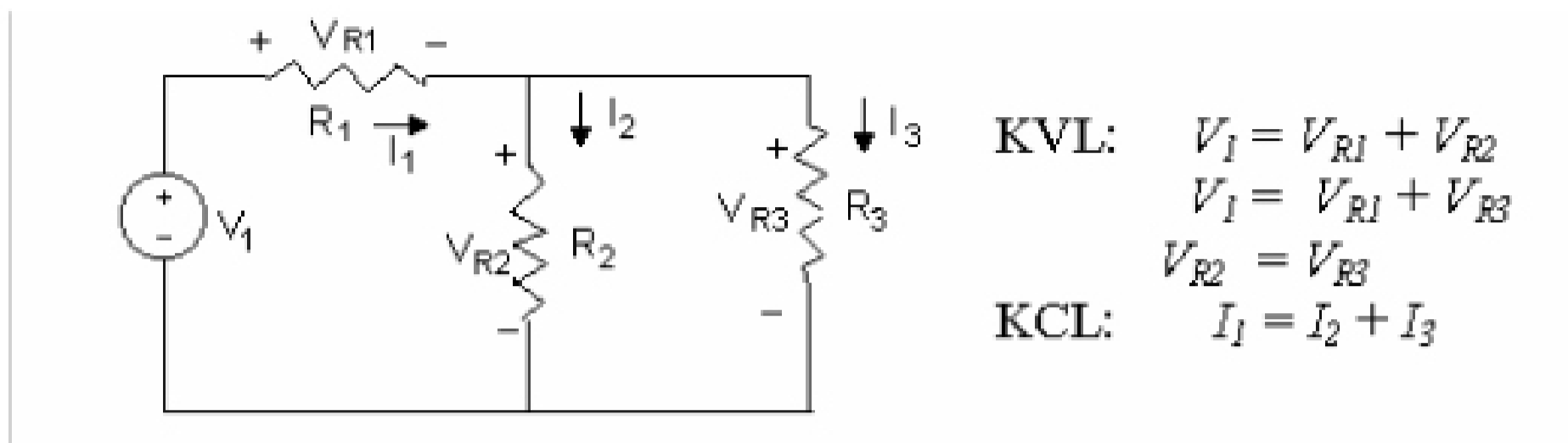3) KVL and KCL – Select a node for ground. Watch out for signs!



4) Equivalent Circuits

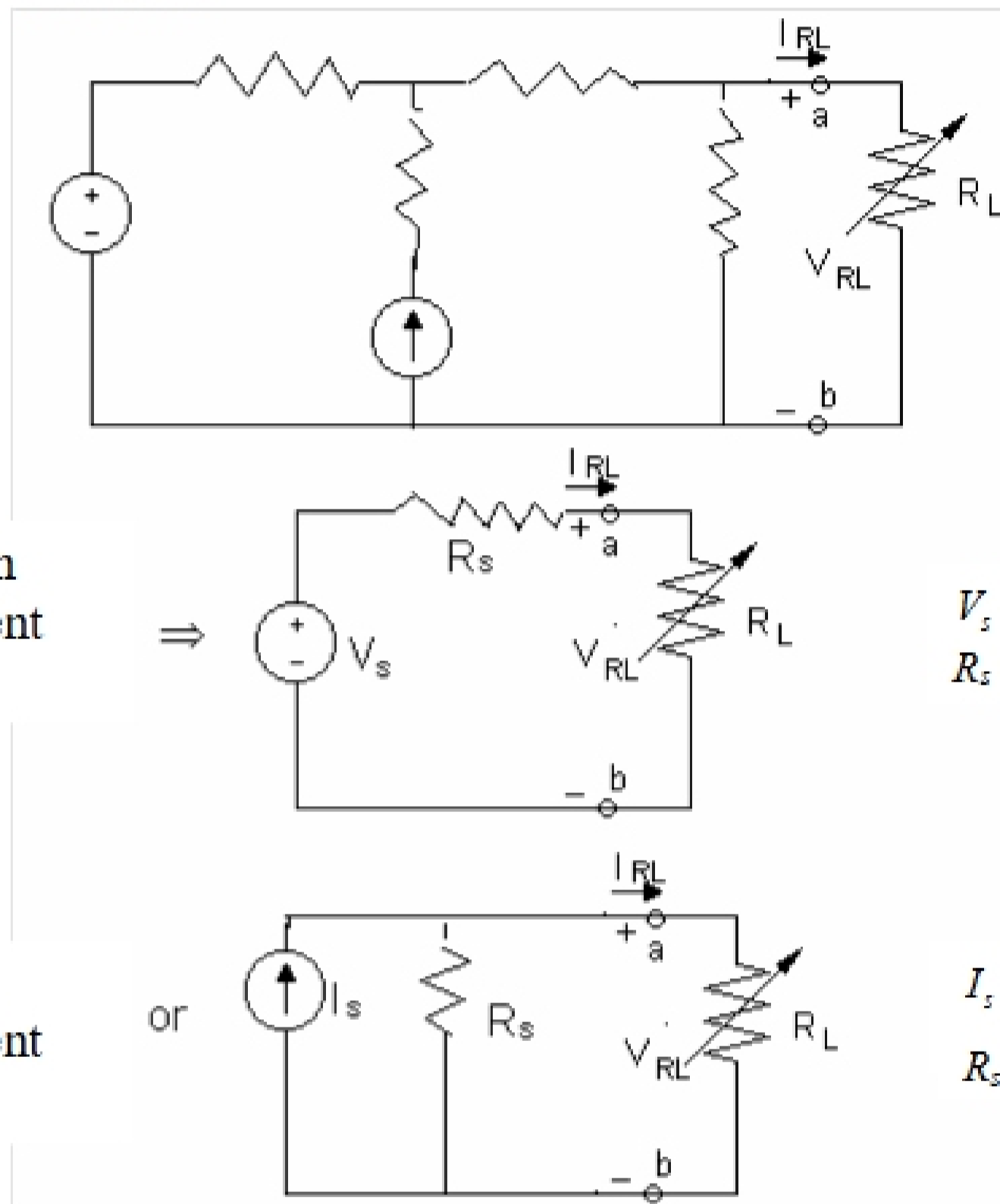

Thevenin Equivalent Circuit

$V_s = V_{OC} =$  Open Circuit Voltage  
 $R_s =$  Equivalent Resistance

Norton Equivalent Circuit

$I_s = I_{SC} =$  Short Circuit Current  
 $R_s =$  Same as before

5) Nodal Analysis and Mesh Analysis

**Nodal Analysis (Use KCL)**

$$\begin{cases} \frac{V_{s1} - V_1}{R_1} + \frac{V_2 - V_1}{R_2} + \frac{V_{s2} - V_1}{R_4} = 0 \\ \frac{V_1 - V_2}{R_2} + \frac{0 - V_2}{R_3} = 0 \end{cases}$$

Solve for  $V_1$  and  $V_2$  and then calculate other currents and voltages.

**Mesh analysis (use KVL)**

$$\begin{cases} V_{s1} = R_1 I_1 + R_2 (I_1 - I_2) + R_3 (I_1 - I_2) \\ V_{s1} = R_1 I_1 + R_4 I_2 + V_{s2} \end{cases}$$

Solve for  $I_1$  and  $I_2$ .

2. Characteristics of Dynamic Networks

1) Inductor

$$v_L(t) = L \frac{d}{dt} i_L(t)$$

$$\text{or } i_L(t) = \frac{1}{L} \int_{-\infty}^t v_L(\tau) d\tau$$

2) Capacitor

$$i_C(t) = C \frac{d}{dt} v_C(t)$$

$$\text{or } v_C(t) = \frac{1}{C} \int_{-\infty}^t i_C(\tau) d\tau$$