

**6.003: Signals and Systems**

**CT Feedback and Control**

October 27, 2009

**Mid-term Examination #2**

Tomorrow, October 28, 7:30-9:30pm, Walker Memorial.

No recitations tomorrow.

Coverage: cumulative with more emphasis on recent material  
lectures 1-12  
homeworks 1-7

Homework 7 includes practice problems for mid-term 2.  
It will not be collected or graded. Solutions are posted.

Closed book: 2 pages of notes (8½ x 11 inches; front and back).


Designed as 1-hour exam; two hours to complete.

**Feedback and Control**

Feedback is pervasive in natural and artificial systems.

We have previously investigated feedback in DT systems.

Example: robotic steering

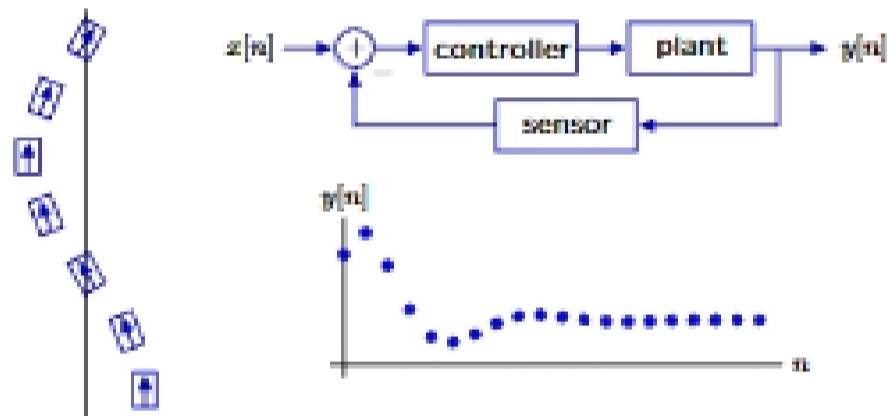

**Feedback and Control**

Today: investigate continuous-time feedback and control.


Examples:

- improve performance of an op amp circuit.
- control position of a motor.
- reduce sensitivity to unwanted parameter variation.
- reduce distortions.
- stabilize unstable systems
  - magnetic levitation
  - inverted pendulum

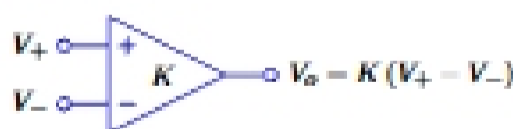**Op-Amp**


Much of the utility of op-amps depends on their having high gain.

Ideal op-amp:  $\lim K \rightarrow \infty$



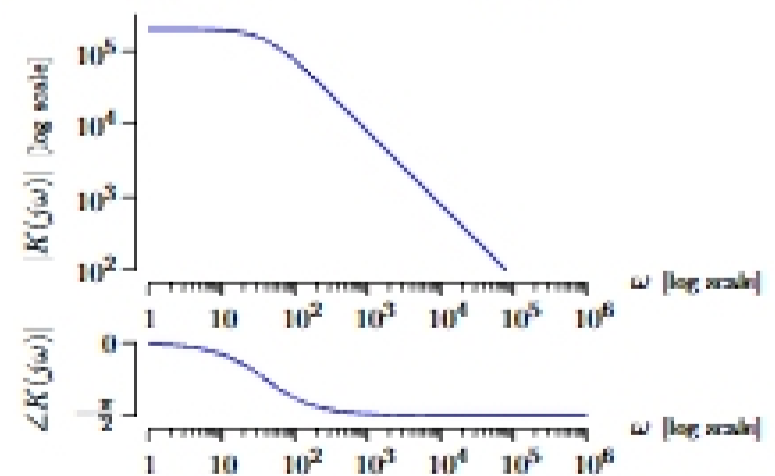**Op-Amp**


The gain of an op-amp depends on frequency.



Frequency dependence of LM741 op-amp.

Check Yourself

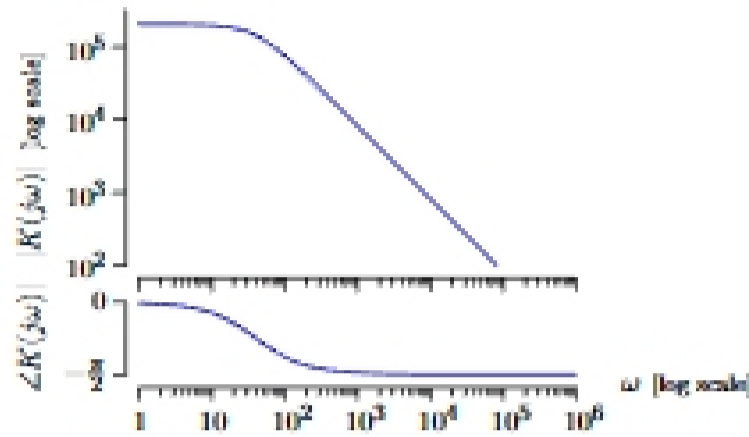
What system function has this frequency response?



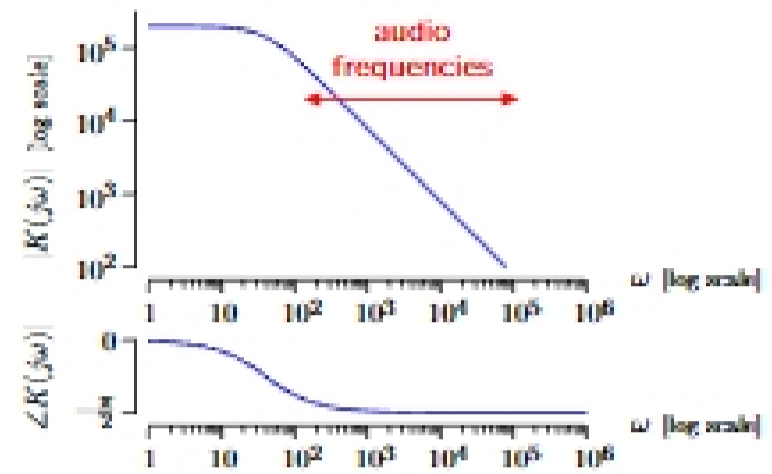1.  $\frac{\alpha K_0}{s + \alpha}$
2.  $\frac{K_0 s}{s + \alpha}$
3.  $\frac{K_0(s + \alpha)}{s}$
4.  $\frac{K_0(s + \alpha)}{\alpha}$
5. none

Op-Amp


Low-gain at high frequencies limits applications.




Unacceptable frequency response for an audio amplifier.

Op-Amp

An ideal op-amp has fast time response.

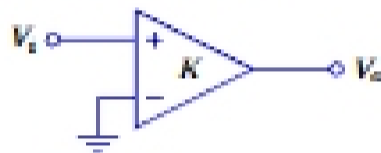


Step response:

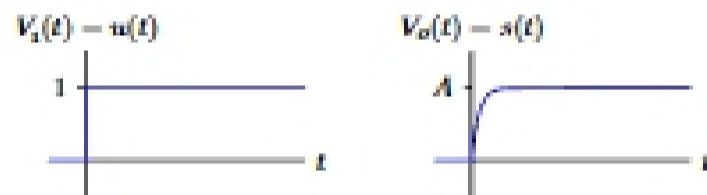

Check Yourself


Determine the step response of an LM741.

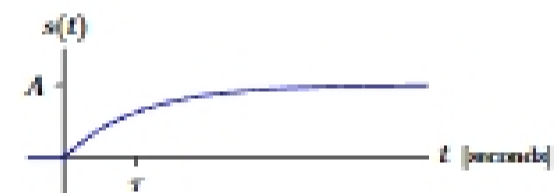

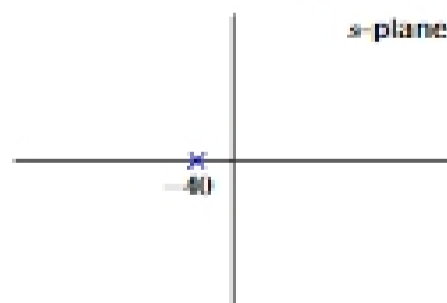1.  $A = 2 \times 10^5$ ;  $\tau = 40 \mu s$
2.  $A = 2 \times 10^5$ ;  $\tau = \frac{1}{30} \mu s$
3.  $A = 80 \times 10^5$ ;  $\tau = 40 \mu s$
4.  $A = 80 \times 10^5$ ;  $\tau = \frac{1}{40} \mu s$
5. none of the above

Op-Amp

The op-amp's poor performance parameters result from a dominant pole at a relatively low frequency.




$$\alpha = 40 \text{ rad/s} = \frac{40 \text{ rad/s}}{2\pi \text{ rad/cycle}} \approx 6.4 \text{ Hz}$$

Op-amps are designed to have a dominant pole:  
 → easy to customize their behavior using feedback!

Improving Performance

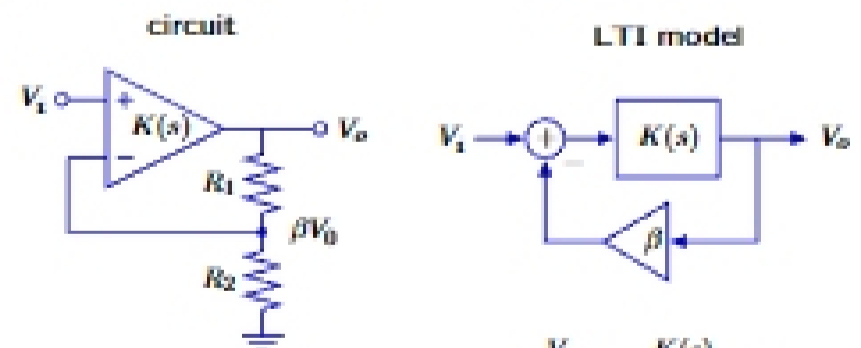Using feedback to improve performance parameters.




$$V_- = \beta V_o = \left( \frac{R_2}{R_1 + R_2} \right) V_o$$

$$\begin{aligned} \frac{V_o}{V_i} &= \frac{K(s)}{1 + \beta K(s)} \\ &= \frac{\frac{\alpha K_0}{s + \alpha}}{1 + \beta \frac{\alpha K_0}{s + \alpha}} \\ &= \frac{\alpha K_0}{s + \alpha + \alpha \beta K_0} \end{aligned}$$

Check Yourself

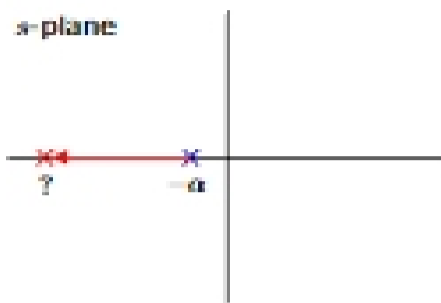
What is the most negative value of the closed-loop pole that can be achieved with feedback?



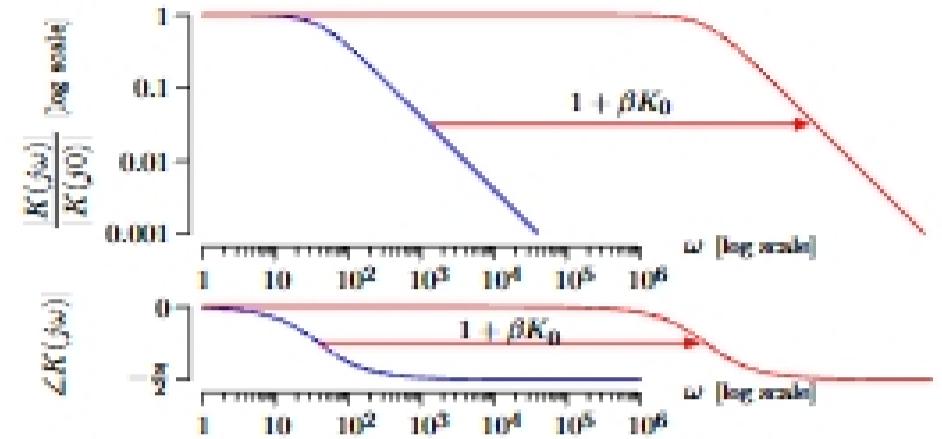1.  $-\alpha(1 + \beta)$
2.  $-\alpha(1 + \beta K_0)$
3.  $-\alpha(1 + K_0)$
4.  $-\infty$
5. none of the above


Improving Performance

Feedback extends frequency response by a factor of  $1 + \beta K_0$  ( $K_0 = 2 \times 10^5$ ).



Improving Performance

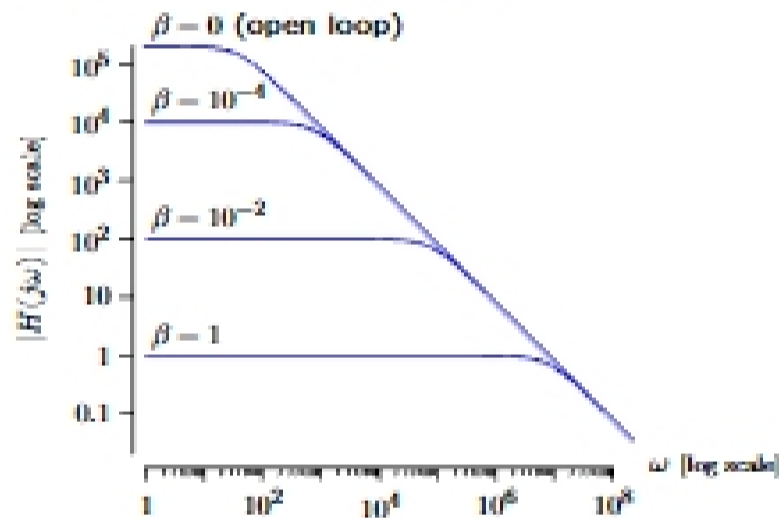Feedback produces higher bandwidths by reducing the gain at low frequencies. It trades gain for bandwidth.




Improving Performance

Feedback makes the time response faster by a factor of  $1 + \beta K_0$  ( $K_0 = 2 \times 10^5$ ).

Step response
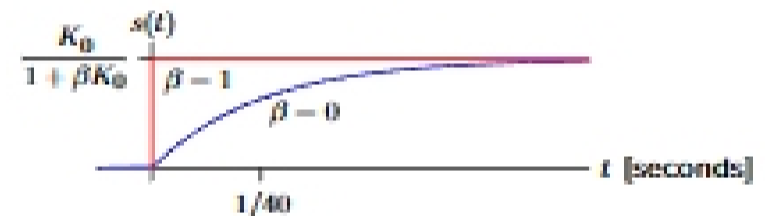
$$s(t) = \frac{K_0}{1 + \beta K_0} (1 - e^{-\alpha(1 + \beta K_0)t}) u(t)$$




Improving Performance

Feedback produces faster responses by reducing the final value of the step response. It trades gain for speed.

Step response
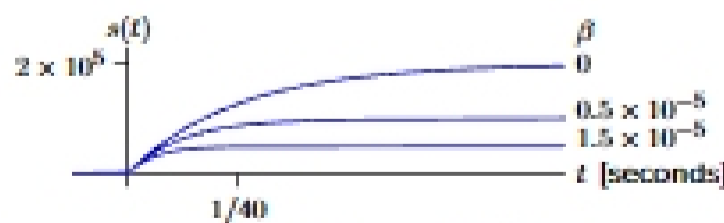
$$s(t) = \frac{K_0}{1 + \beta K_0} (1 - e^{-\alpha(1 + \beta K_0)t}) u(t)$$



The maximum rate of voltage change  $\left. \frac{ds(t)}{dt} \right|_{t=0+}$  is not increased.

Improving Performance

Feedback improves performance parameters of op-amp circuits.

- can extend frequency response
- can increase speed

Performance enhancements are achieved through a reduction of gain.