


Phasor domain:

Resistor




$$I_x = i_x \angle \phi_i$$

$$V_x = R i_x \angle \phi_i$$

$$Z_x = \frac{R i_x \angle \phi_i}{i_x \angle \phi_i} = R$$

Capacitor




$$V_c = v_c \angle \phi_v$$

$$I_c = \omega C v_c \angle \phi_v + 90^\circ$$

$$Z_c = \frac{v_c \angle \phi_v}{\omega C v_c \angle \phi_v + 90^\circ} \quad Z_c = \frac{1}{\omega C} \angle -90^\circ$$

$$Z_c = \frac{-j}{\omega C} = \frac{1}{j\omega C}$$

Inductor




$$V_L = \omega L i_L \angle \phi_i + 90^\circ$$

$$I_L = i_L \angle \phi_i$$

$$Z_L = \frac{\omega L i_L \angle \phi_i + 90^\circ}{i_L \angle \phi_i} \quad Z_L = \omega L \angle 90^\circ$$


$$Z_L = j\omega L$$

Combining impedances:

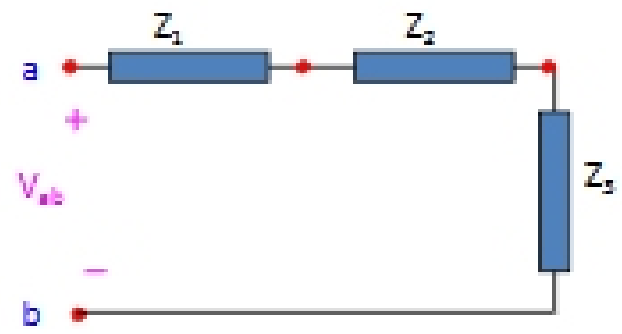

$$V_{ab} = I[Z_1] + I[Z_2] + I[Z_3]$$

$$V_{ab} = I\{[Z_1] + [Z_2] + [Z_3]\}$$
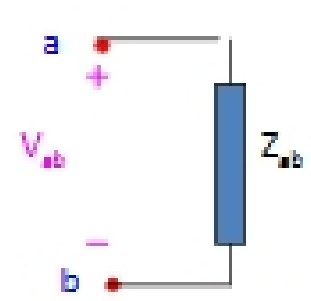
$$V_{ab} = I[Z_{ab}]$$


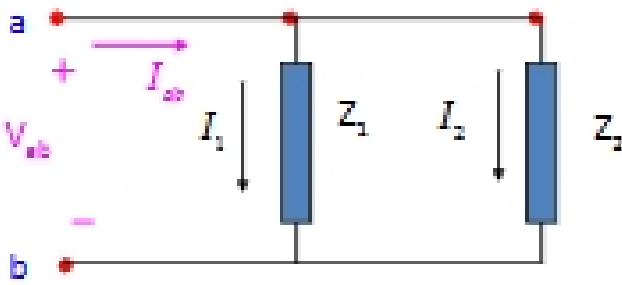
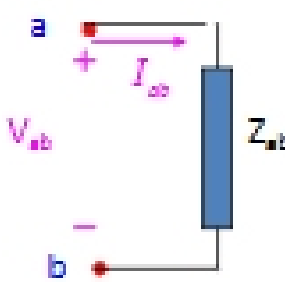
$$I_{ab} = I_1 + I_2$$

$$I_{ab} = \frac{V_{ab}}{Z_1} + \frac{V_{ab}}{Z_2}$$







$$I_{ab} = V_{ab} \left[\frac{1}{Z_1} + \frac{1}{Z_2} \right]$$

$$I_{ab} = V_{ab} \left[\frac{Z_1 + Z_2}{Z_1 Z_2} \right]$$


$$V_{ab} = I_{ab} \left[\frac{Z_1 Z_2}{Z_1 + Z_2} \right]$$

$$V_{ab} = I_{ab} \{ Z_{ab} \}$$

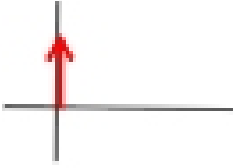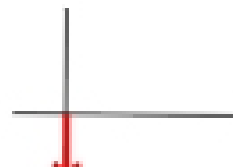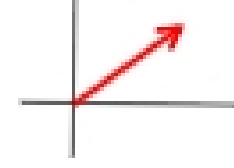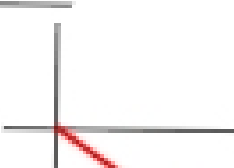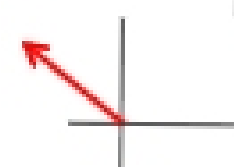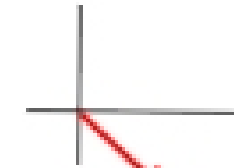

Complex Numbers:

$A = 5j$	\longleftrightarrow	$A = 5 \angle 90^\circ$	
$A = -5j$	\longleftrightarrow	$A = 5 \angle -90^\circ$	
$A = 5 + j5$	\longleftrightarrow	$A = 5\sqrt{2} \angle 45^\circ$	
$A = 5 - j5$	\longleftrightarrow	$A = 5\sqrt{2} \angle -45^\circ$	
$A = -5 + j5$	\longleftrightarrow	$A = 5\sqrt{2} \angle 135^\circ$	
$A = -5 - j5$	\longleftrightarrow	$A = 5\sqrt{2} \angle -135^\circ$	

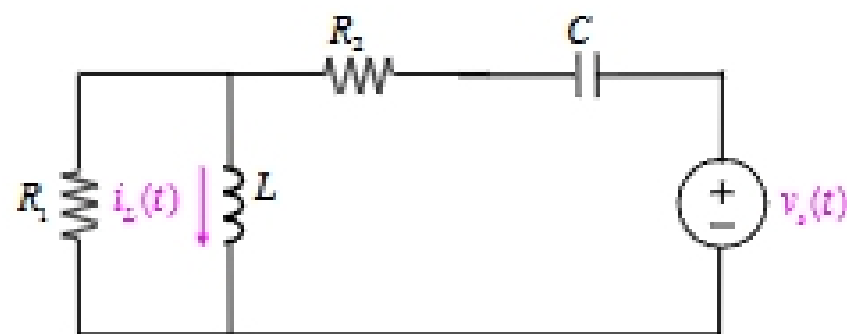Example (1):



Given: $v_s(t) = 300 \cos(2000t)$
 $R_1 = 100\Omega$ $R_2 = 10\Omega$
 $L = 50\text{mH}$ $C = 10\mu\text{F}$

Find:
 $i_L(t) = ?$

Hint: $\omega = 2000 \text{ rad/sec}$ $\Rightarrow i_L(t) = i_m \cos(2000t + \theta)$

Find: $i_m = ?$ $\theta = ?$

Solution:

1. Transform the circuit from time domain to phasor domain

$\omega = 2000 \text{ rad/sec}$

$v_s(t) = 300 \cos(2000t)$

Element impedance:

$$Z_L = j\omega L = j(2000)(0.05) = j100$$

$$Z_C = -\frac{j}{\omega C} = -j \frac{1}{2 \times 10^3 \times 10 \times 10^{-6}} = -j50$$

Source:

$$V_s = 300 \angle 0^\circ \text{ volt}$$

