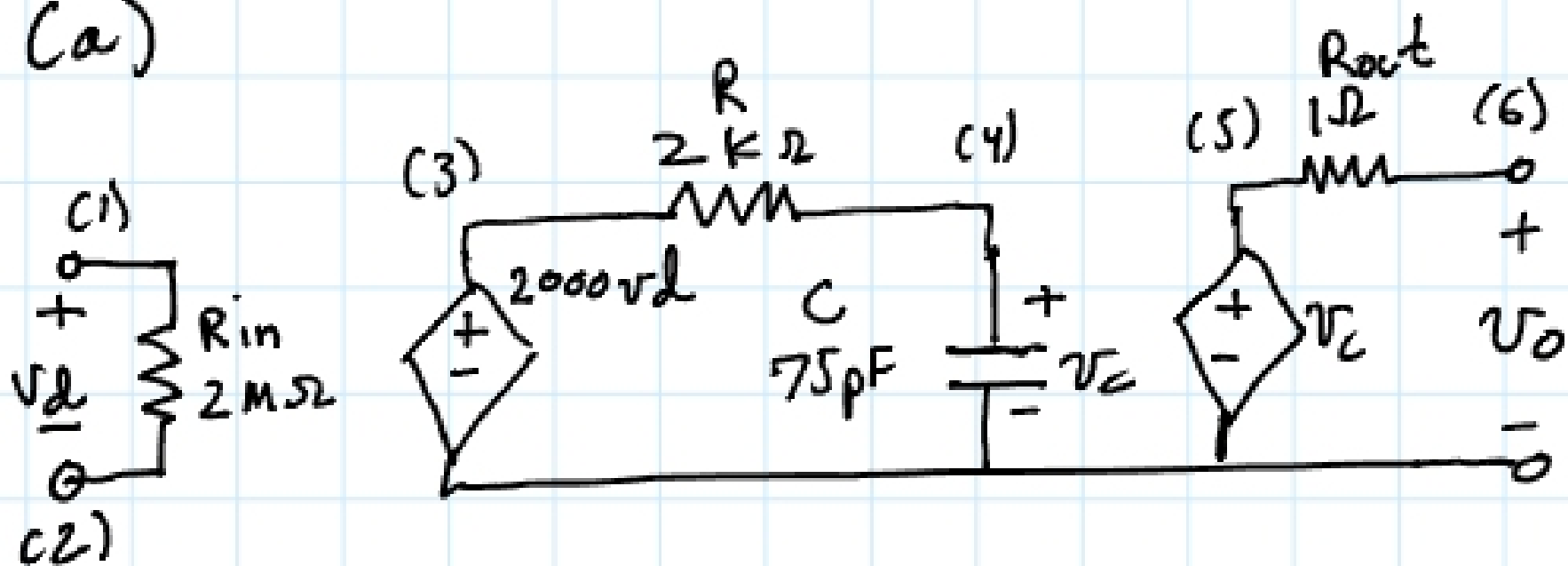


Problem 13 : See attached file ps4-p13-soln.ms12.

Problem 14 : See attached file ps4-p14-soln.ms12.

Problem 15 :

1. (a)




SPICE model:

```
.SUBCKT OPAMP 1 2 6
r Rin 1 2 2MEG
e vd 3 0 1 2 2K
r R 3 4 2K
c C 4 0 75p
e vc 5 0 4 0 1
r Rout 5 6 1
.ENDS OPAMP
```

Problem 15

1. (b) Phasor Domain Circuit Model

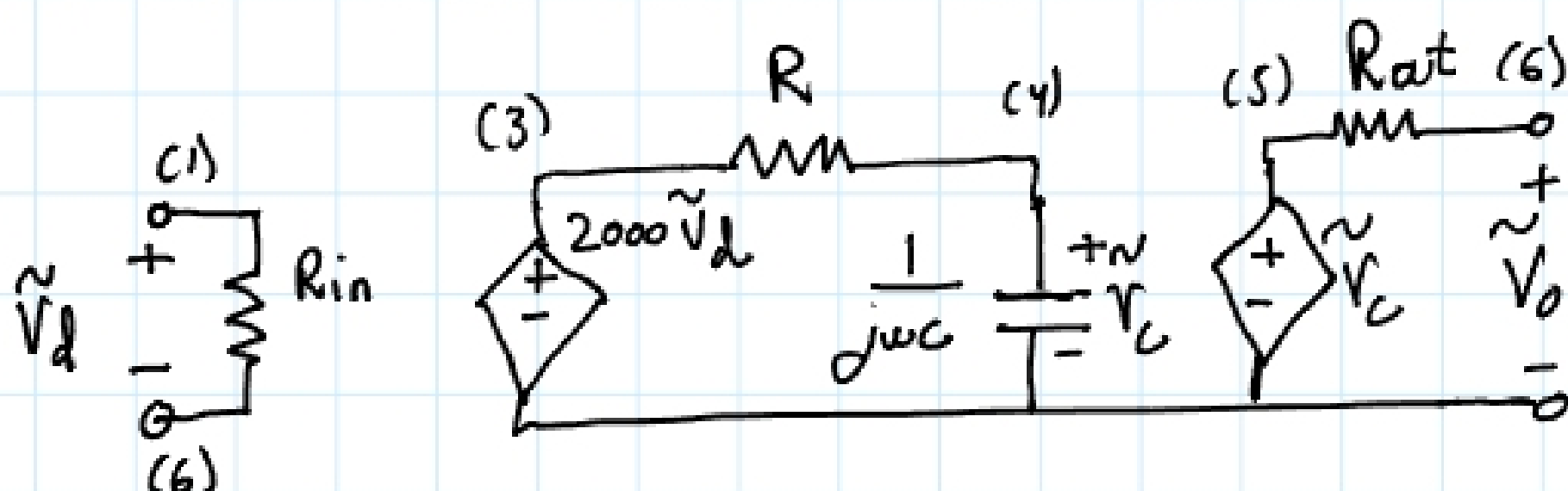

- Because the Op Amp output sees an open circuit, $\tilde{V}_o = \tilde{V}_c$
- Using voltage division

$$\tilde{V}_o = \tilde{V}_c = \frac{1/j\omega C}{1/j\omega C + R} 2000 \tilde{V}_d$$

$$H(j\omega) = \frac{\tilde{V}_o}{\tilde{V}_d} = 2000 \frac{1}{j\omega RC + 1}$$

$$H(j\omega) = K \frac{1}{j\omega/\omega_c + 1}$$

$$K = 2000$$

$$\omega_c = \frac{1}{RC}$$

$$(i) \text{ DC gain [V/V]} = H(j0) = K = 2000$$

$$\text{DC gain [dB]} = 20 \log_{10} |K| = 66 \text{ dB}$$

Problem 15


1 (b) (ii)

$$\omega_c = \frac{1}{RC} = \frac{1}{(2000 \Omega)(75 \times 10^{-12} \text{F})}$$

$$\omega_c = 6.67 \times 10^6 \text{ rad/sec}$$

$$f_c = \frac{\omega_c}{2\pi} = 10.5 \text{ MHz}$$

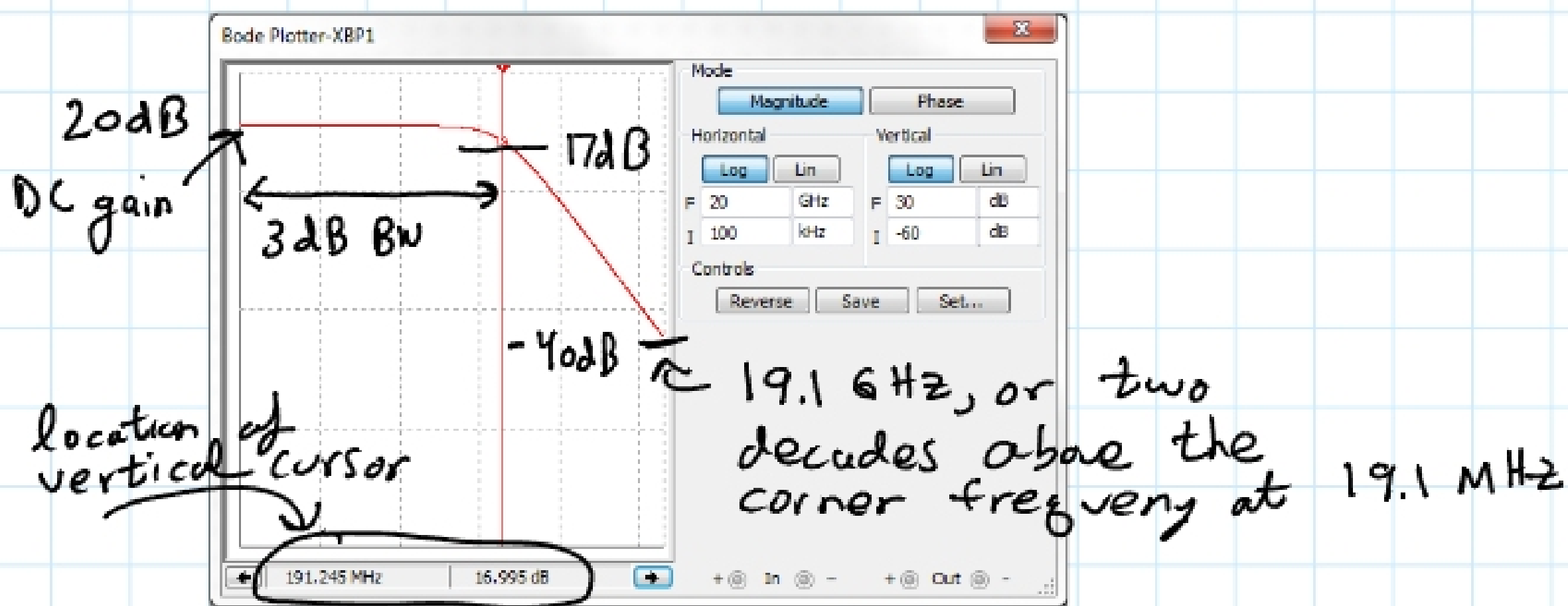2. The magnitude response generated by Multisim is



$$(a) \quad 3\text{dB BW} = 191.2 \text{ MHz} = 1.20 \times 10^9 \frac{\text{rad}}{\text{sec}}$$

In comparison, the 3dB BW of the Op Amp without negative feedback is 10.5 MHz.