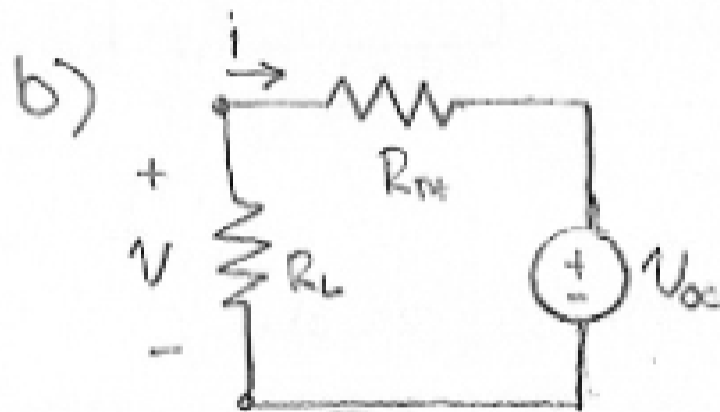


ECE 201 HW14 Solutions

1) a) $i = \frac{V}{R_L}$

1) $i = \frac{8V}{32\Omega} = \frac{1}{4} A$

2) $i = \frac{7V}{-21\Omega} = -\frac{1}{3} A$



$$V = i R_{TH} + U_{oc}$$


① $8 = (\frac{1}{4}) R_{TH} + U_{oc}$

② $7 = (-\frac{1}{3}) R_{TH} + U_{oc}$


$$\begin{bmatrix} 1/4 & 1 \\ -1/3 & 1 \end{bmatrix} \begin{bmatrix} R_{TH} \\ U_{oc} \end{bmatrix} = \begin{bmatrix} 8 \\ 7 \end{bmatrix}$$

$$U_{oc} = \frac{53}{7} \quad R_{TH} = \frac{12}{7}$$

$$= 7.57V \quad = 1.71\Omega$$

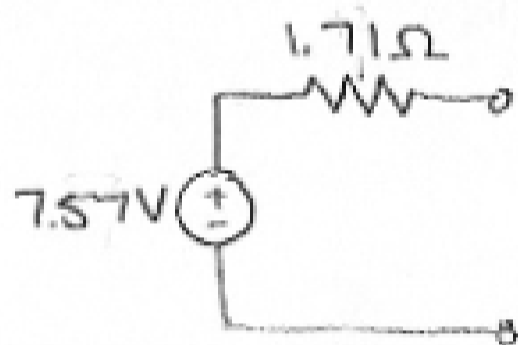

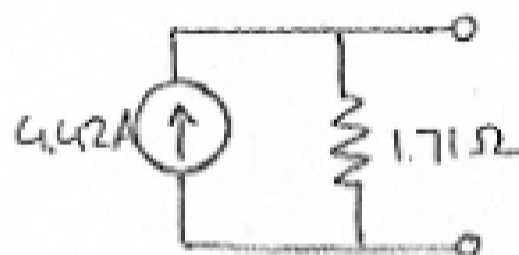
c) $i_{sc} = \frac{U_{oc}}{R_{TH}} = \frac{53}{\frac{12}{7}} = \frac{53}{12} = 4.42 A$




d) $R_L = R_{TH} = 1.71\Omega$

e) $P = \frac{U_{oc}^2}{4R_{TH}} = \frac{(7.57V)^2}{4(1.71\Omega)} = 8.38W$

2) a) Rearrange circuit into:

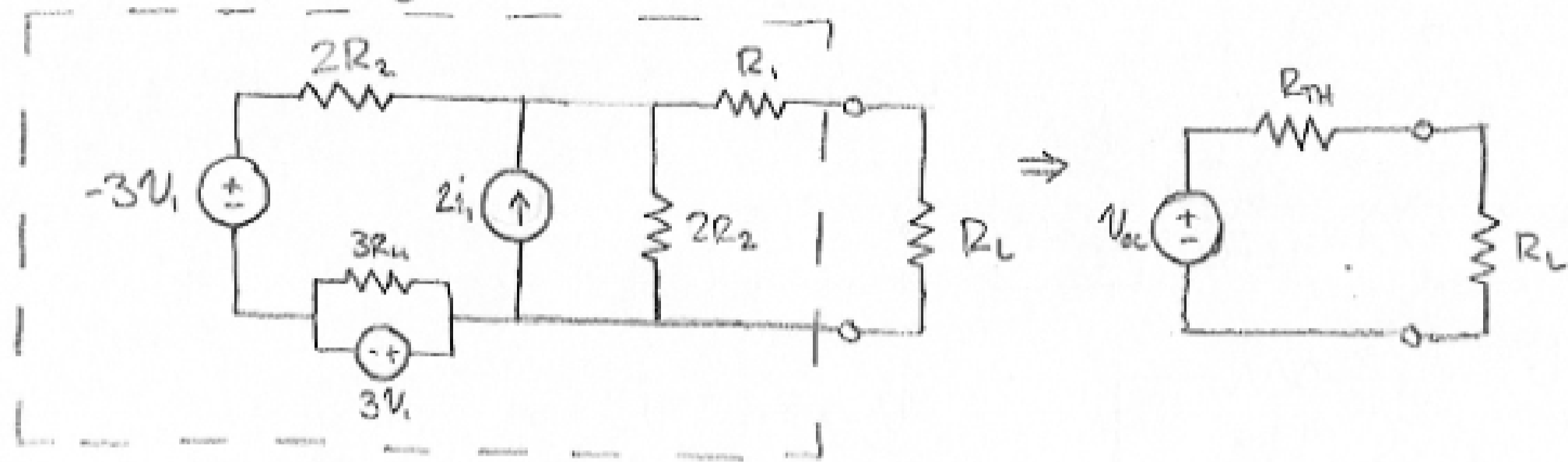

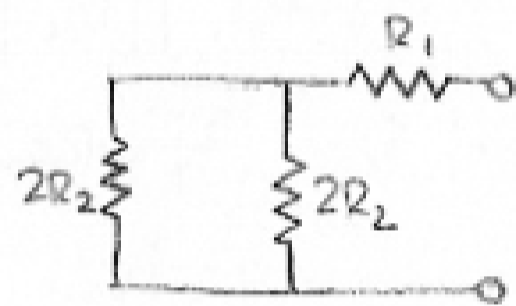$R_{TH} = R_{eq}$ of boxed circuit with independent sources off




$$R_{TH} = R_{eq} = R_1 + ((2R_2)^{-1} + (2R_2)^{-1})^{-1} \\ = R_1 + R_2$$

$R_L = R_{TH}$ For maximum power

$$= \boxed{R_1 + R_2}$$

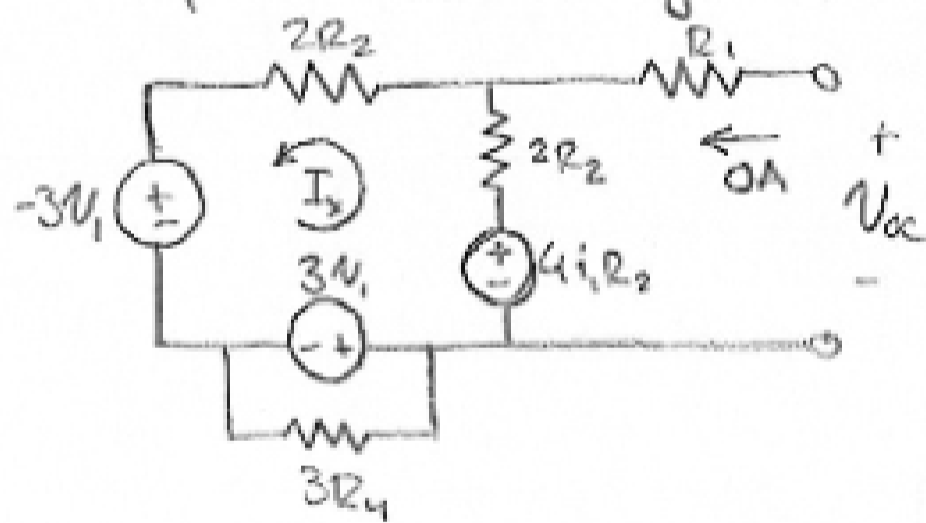b) After current to voltage source transformation, we find the open circuit voltage



$$3V_1 + 3V_1 + 4i_1 R_2 - 2R_2 I_x - 2R_2 I_y = 0$$

$$4R_2 I_x = 6V_1 + 4i_1 R_2$$

$$I_x = \frac{3V_1 + 2i_1 R_2}{2R_2}$$

$$V_{oc} = 4i_1 R_2 - 2R_2 I_x$$

$$= 4i_1 R_2 - 3V_1 - 2i_1 R_2$$

$$= 2i_1 R_2 - 3V_1$$

$$P_{L, Max} = \frac{V_{oc}^2}{4R_{TH}} = \boxed{\frac{(2i_1 R_2 - 3V_1)^2}{4(R_1 + R_2)}}$$

$$3) a) V_{AB} = i_s R_{TH} + V_{oc}$$

$$V_{AB} = i_s g + (V_1 + V_2)$$

$$\boxed{R_{TH} = g}$$

$$b) \boxed{V_{oc} = V_1 + V_2}$$

$$c) i_{sc} = \frac{V_{oc}}{R_{TH}} \\ = \boxed{\frac{V_1 + V_2}{R_{TH}}}$$

$$d) R_L = R_{TH} \\ = \boxed{g}$$

$$e) P_{L,Max} = \frac{V_{oc}^2}{4 R_{TH}} \\ = \boxed{\frac{(V_1 + V_2)^2}{4g}}$$