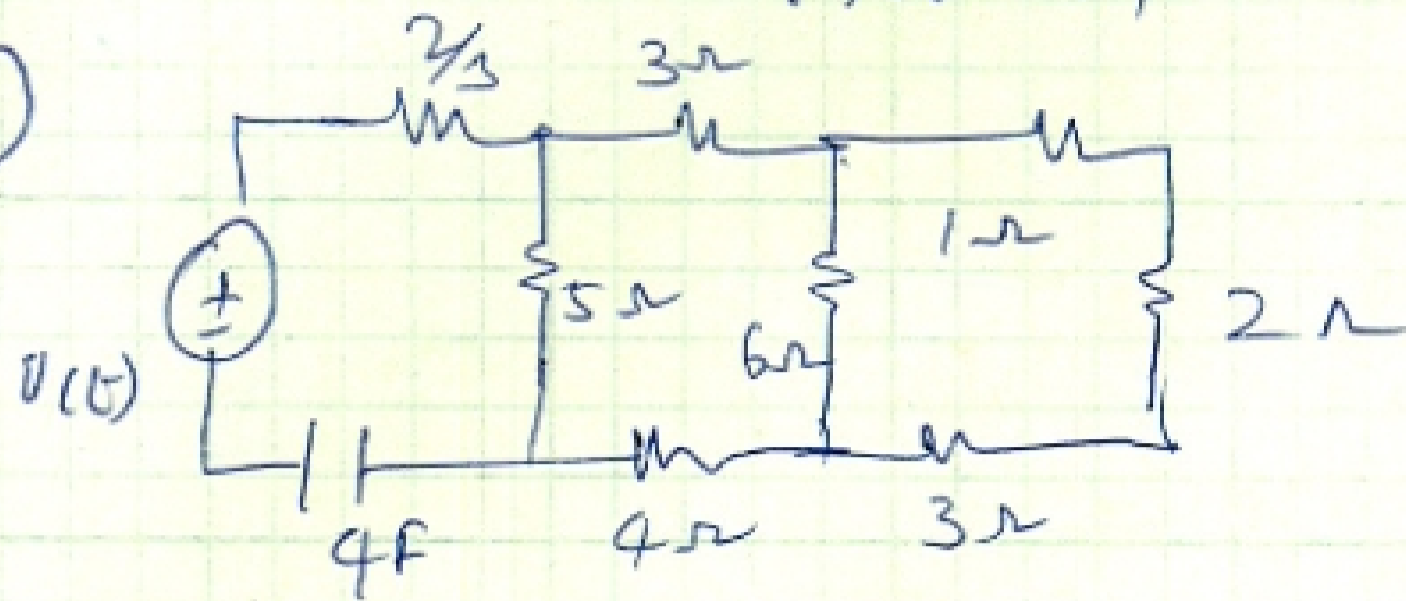


HW-19

①



(a) R_{eff} seen by capacitor = $\frac{2}{3} + \left(5 \parallel \left[3 + 4 + \left[6 \parallel (1 + 2 + 3) \right] \right] \right)$

$$= \frac{2}{3} + 5 \parallel (3 + 4 + 3)$$

$$= \frac{2}{3} + 5 \parallel 10 = 4 \Omega$$

(b) Time constant $\tau = RC = 4 \times 4 = 16 \text{ sec}$

(c) $V_c(0) = 0$ $V_c(\infty) = 10 \text{ V}$ (as cap becomes open)

$$\Rightarrow V_c(t) = (\text{final value}) + \left(\frac{\text{initial value} - \text{final value}}{\text{value}} \right) e^{-t/\tau}$$

$$\Rightarrow V_c(t) = 10 - 10e^{-t/16} = \boxed{10(1 - e^{-t/16}) = V_c(t)}$$

(d) $V_c(0) = 4 \text{ V}$ $V_c(\infty) = 10 \text{ V}$ $\therefore V_c(t) = 10 - e^{-t/16}(4 - 10)$

$$\Rightarrow \boxed{V_c(t) = 10 - 6e^{-t/16}}$$


(e) $V_c(0) = -2 \text{ V}$ $V_c(\infty) = 10 \text{ V}$

$$\Rightarrow V_c(t) = 10 - 12e^{-t/16}$$

$$\therefore i_c(t) = C \frac{dV_c}{dt} \Rightarrow \boxed{i_c(t) = 3e^{-t/16}}$$


①

(c)

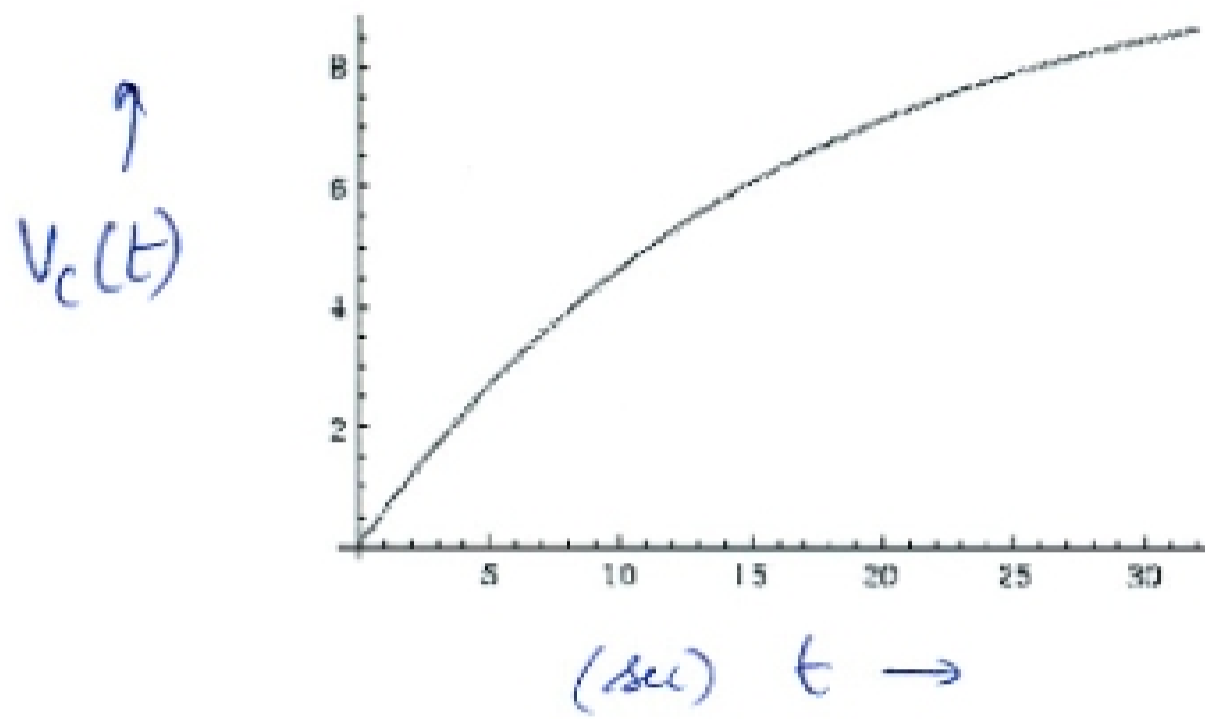


$$V_c(t) = 10(1 - e^{-t/16})$$

(d)

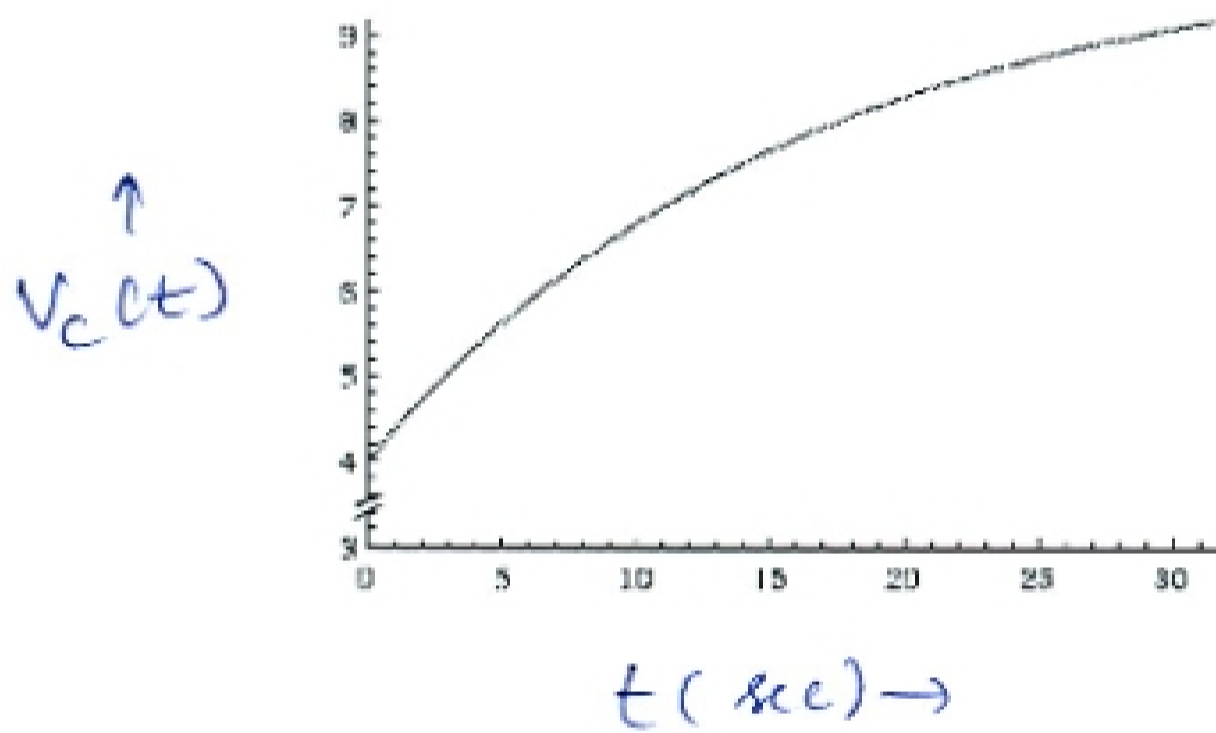


$$V_c(t) = 10 - 6e^{-t/16}$$

(e)

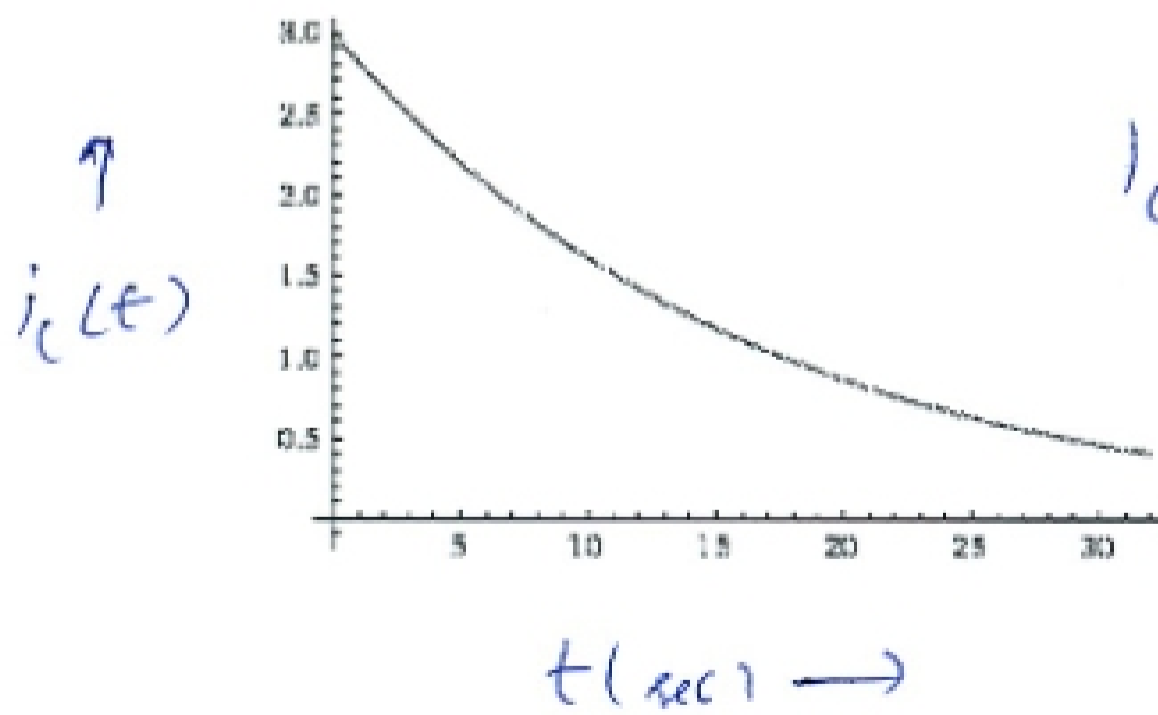


$$i_c(t) = 3e^{-t/16}$$

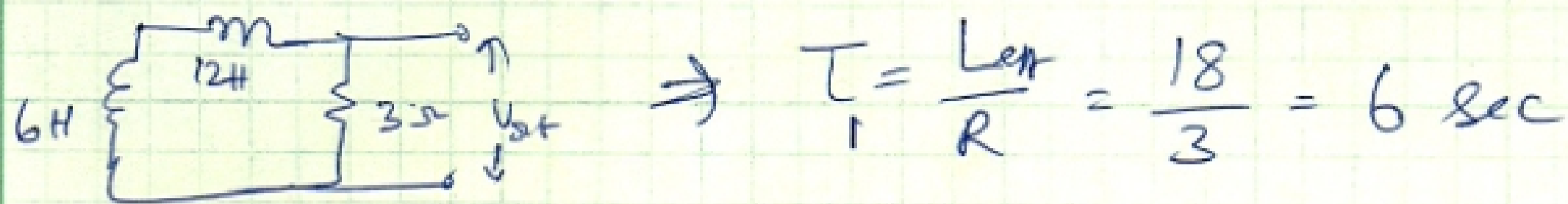② (a) When the switch is open, the circuit is



(b) When switch is closed

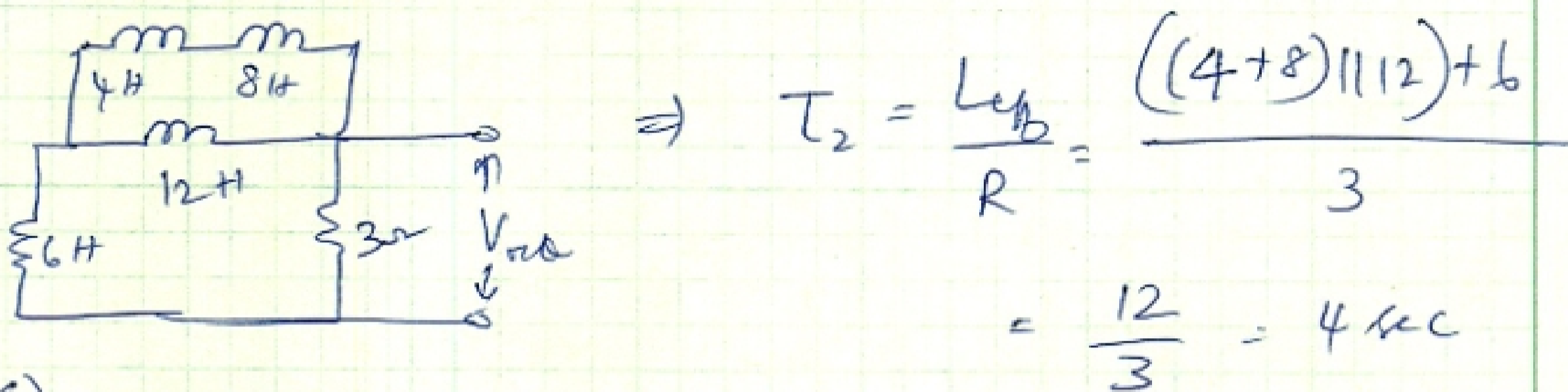

(c) $i(0) = 2 \text{ A}$ & circuit is not driven so the current decays to 0 A $i(\infty) = 0 \text{ A}$

$$\therefore i(t) = \left(\text{final value} \right) + \left(\text{initial value} - \text{final value} \right) e^{-t/\tau}$$

$$i_L(t) = 2e^{-t/6} \quad \boxed{V_{out} = i_L R = 6e^{-t/6} \quad 0 < t < 6}$$

(d) @ $t = 6$ $i_L(6) = 2e^{-1}$ @ $t = \infty$ $i_L(\infty) = 0$

$$i_L(t) = \frac{2}{e} e^{-\frac{(t-6)}{4}} \quad \text{for } 6 < t < 10$$

$$\& i_L(t) = 2e^{-t/6} \quad \text{for } 0 < t < 6$$

$$\Rightarrow V_{out} = \begin{cases} 6e^{-t/6} & 0 \leq t \leq 6 \\ \frac{6}{e} e^{-\frac{(t-6)}{4}} & 6 < t \leq 10 \end{cases}$$