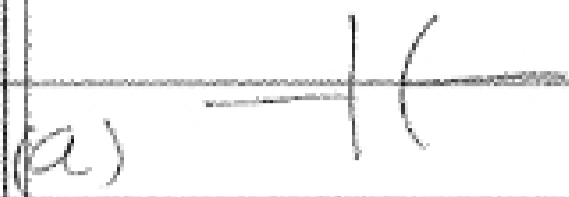


7-11




$$\begin{aligned} (a) \quad q &= CV \\ &= (20 \mu\text{F}) 100 \text{ V} = 2.0 \text{ mC} \end{aligned}$$

$$(b) \quad V = \frac{q}{C} = \frac{2.0 \text{ mC}}{5 \mu\text{F}} = 0.4 \text{ kV} = 400 \text{ V}$$

$$(c) \quad V = \frac{q}{C} = \frac{50 \mu\text{C}}{2 \mu\text{F}} = 25 \text{ V}$$

$$\begin{aligned} (d) \quad W_C &= \frac{1}{2} CV^2 = \frac{1}{2} (20 \mu\text{F}) (100 \text{ V})^2 \\ &= 0.1 \text{ J} \end{aligned}$$

7-17

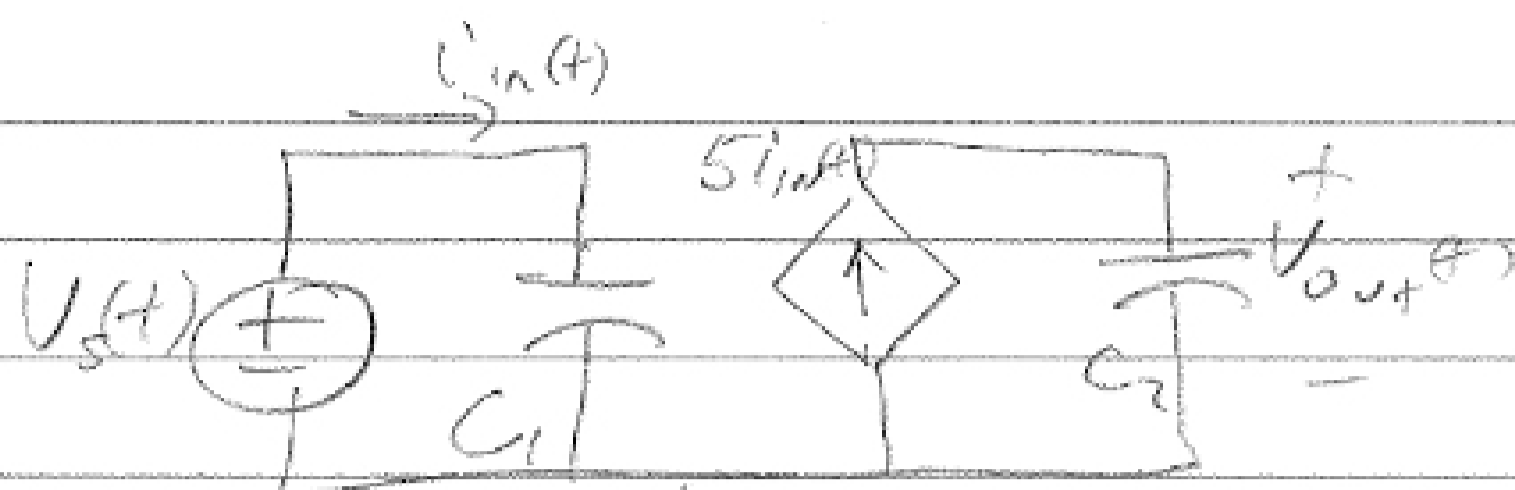

$$C_1 = 20 \mu\text{F}$$

$$C_2 = 0.1 \text{ mF}$$

$$V_s(t) = 5 \sin(2000t) \text{ V}$$

$$V_{out}(0) = 10 \text{ V}$$

$$(a) \quad i_{in}(t) = C \frac{dV_s(t)}{dt} = 20 \mu\text{F} \cdot 5 (2000/s) \cos 2000t \text{ V}$$

$$= 0.2 \cos 2000t \text{ A}$$

$$5i_{in}(t) = 1.0 \cos 2000t \text{ A}$$

$$V_{out} = \frac{1}{C_2} \int_0^t 5i_{in}(t') dt' + V_{out}(0)$$

$$= \frac{1}{0.1 \text{ mF}} \frac{1.0}{2000/s} \sin 2000t \Big|_0^t + 10 \text{ V}$$

$$\boxed{V_{out} = (5 \sin 2000t + 10) \text{ V}}$$

Since  $i_{in}(t)$  depends on  $\frac{dV_s}{dt}$ , any initial voltage on  $C_1$  does not affect  $i_{in}(t)$  or  $V_{out}$ .

$$(b) \quad P_{DS} = 5 i_{in}(t) V_{out}(t)$$

$$= (1.0 \cos 2000t \text{ A})(5 \sin 2000t + 10) \text{ V}$$

$$= (2.5 \sin 4000t + 10 \cos 2000t) \text{ W}$$

$$(c) W_C(t) = \frac{1}{2} C_2 V_{out}^2(t)$$

$$= \frac{1}{2} (0.1 \text{ mF}) (5 \sin 2000t + 10)^2 V^2$$

