

## Lecture 19 - Differential Amplifier Stages - Outline

### Announcements

**Design Problem** - coming out tomorrow; PS #10 looks at pieces;  
neglect the Early effect in large signal analyses

### Review - Single-transistor building block stages

**Common source:** general purpose gain stage, workhorse

**Common gate:** small  $R_{in}$ , large  $R_{out}$ , unity  $A_v$ , same  $A_v$  as CS

**Source follower:** large  $R_{in}$ , small  $R_{out}$ , unity  $A_v$ , same  $A_v$  as CS

**Series and Shunt feedback:** we'll see in special situations

### Differential Amplifier Stages - Large signal behavior

**General features:** symmetry, inputs, outputs, biasing (Symmetry is the key!)

**Large signal transfer characteristic**

### Difference- and common-mode signals

**Decomposing and reconstructing general signals**

### Half-circuit incremental analysis techniques

**Linear equivalent half-circuits**


**Difference- and common-mode analysis**

**Example:** analysis of source-coupled pair
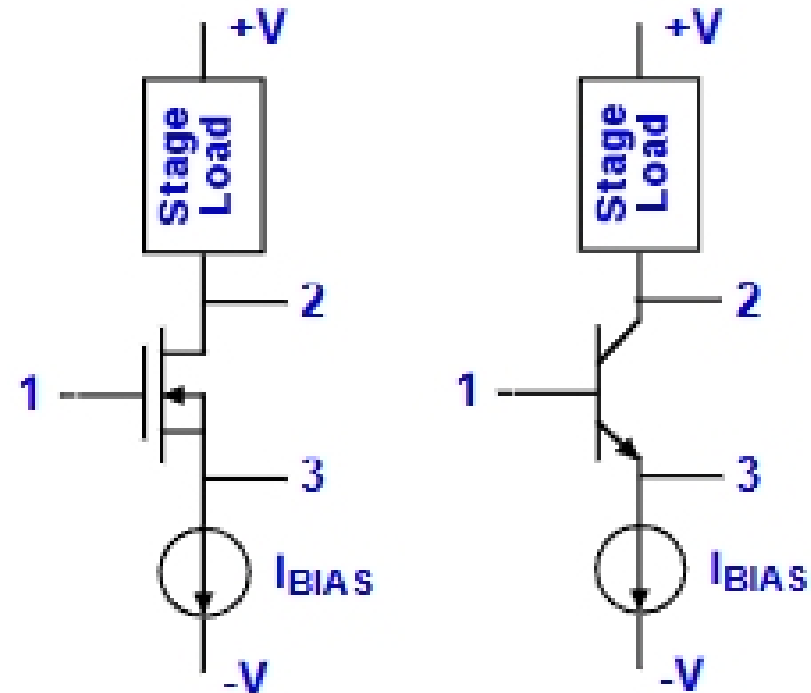
## Linear amplifier layouts: The practical ways of putting inputs to, and taking outputs from, transistors to form linear amplifiers


There are 12 choices: three possible nodes to connect to the input, and for each one, two nodes from which to take an output, and two choices of what to do with the remaining node (ground it or connect it to something).

Not all these choices work well, however. In fact only three do:





Name	Input	Output	Grounded
Common source/emitter	1	2	3
Common gate/base	3	2	1
Common drain/collector (Source/emitter follower)	1	3	2
Source/emitter degeneration	1	2	none

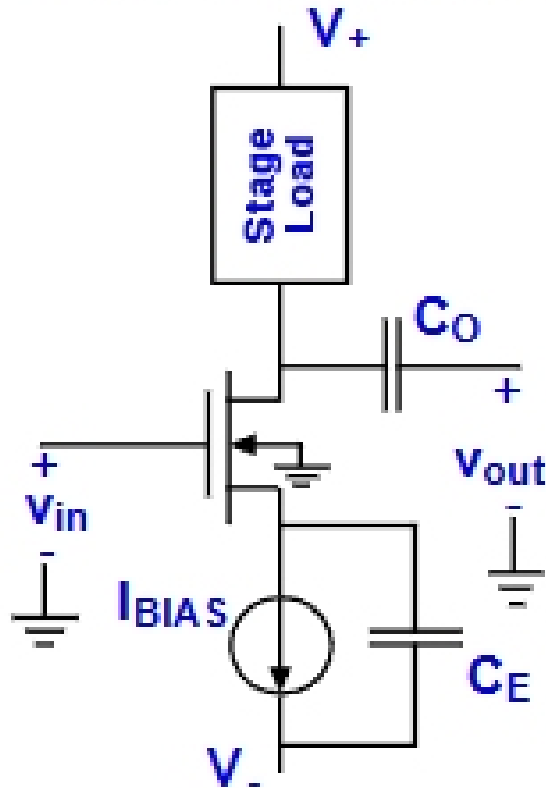- Three MOSFET single-transistor amplifiers



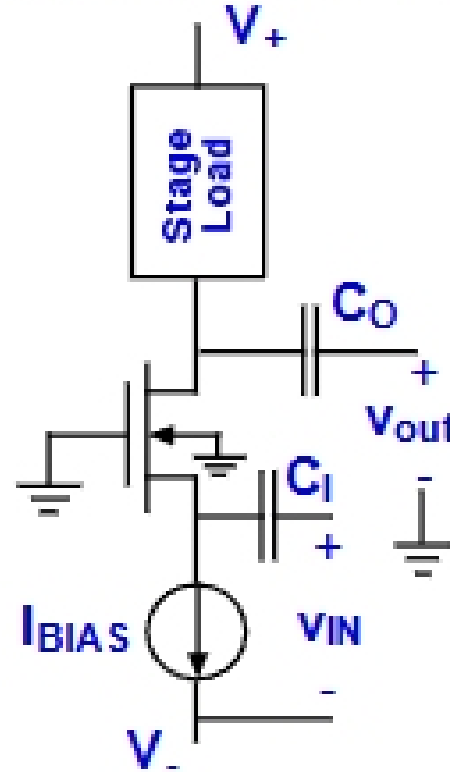
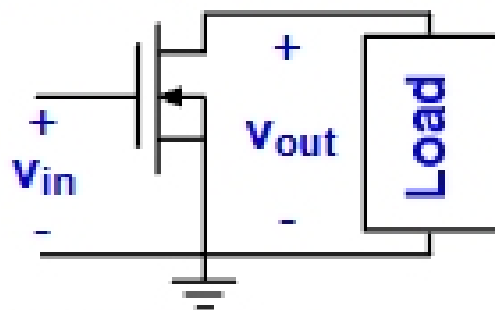
**COMMON SOURCE**

Input: gate  
Output: drain  
Common: source  
Substrate: to source



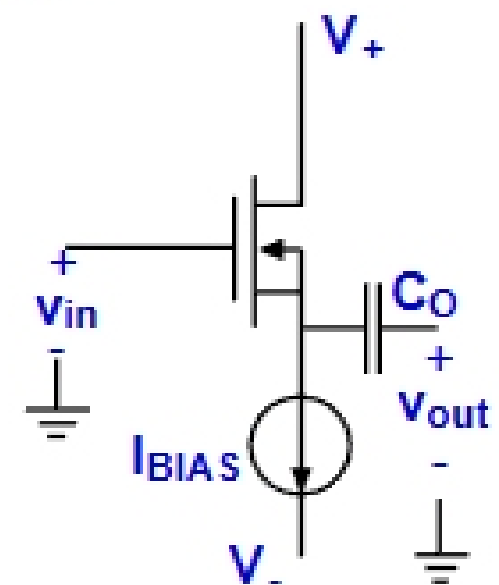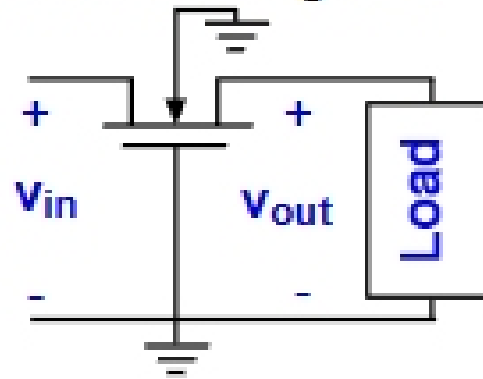**COMMON GATE**

Input: source; Output: drain  
Common: gate  
Substrate: to ground



**SOURCE FOLLOWER**

Input: gate  
Output: source  
Common: drain  
Substrate: to source

