

## 7.2 - The T-Junction Power Divider

**Reading Assignment:** *pp. 315-318*

Three-port couplers are also known as **T-Junction Couplers**, or **T-Junction Dividers**.



**HO: THE T-JUNCTION COUPLER**

We will study **three** standard T-Junction couplers:

**HO: THE RESISTIVE DIVIDER**

**HO: THE LOSSLESS DIVIDER**

**HO: CIRCULATORS**

Now let's consider a 3dB power divider from another viewpoint; let's consider the **scattering matrix** of a (nearly) **ideal** 3dB power divider.

**HO: THE (NEARLY) IDEAL POWER DIVIDER**

This ideal 3dB power divider **can** be constructed! It is the **Wilkinson Power Divider**—the subject of the next section.

# The T-Junction Coupler

Say we desire a **matched** and **lossless** 3-port coupler.



*Wait a minute! I already told you that a matched, lossless, reciprocal **3-port** device of any kind is a physical impossibility!*


Absolutely true! Our desire in this case will be **unfulfilled**. There are, however, a few designs that come **close**.

- 1. The Lossless Divider** - As the name states, this coupler is lossless. It is likewise reciprocal, and thus is **not matched**.
- 2. The Resistive Divider** - As the name implies, this coupler is **lossy**. However, it is both matched and reciprocal.
- 3. The Circulator** - This three-port coupler is both matched and (ideally) lossy. This of course means that it is **not reciprocal!**
- 4. The Wilkinson Divider** - Like the resistive divider, it is matched and reciprocal, and thus is **lossy**. However, it is lossy in a way that is not apparent when power is **divided** (i.e., power can be divided **without loss**).

As a result, the Wilkinson Power Divider is in most ways as **ideal** a T-junction as there is. Accordingly, it has its very **own section** in your textbook!

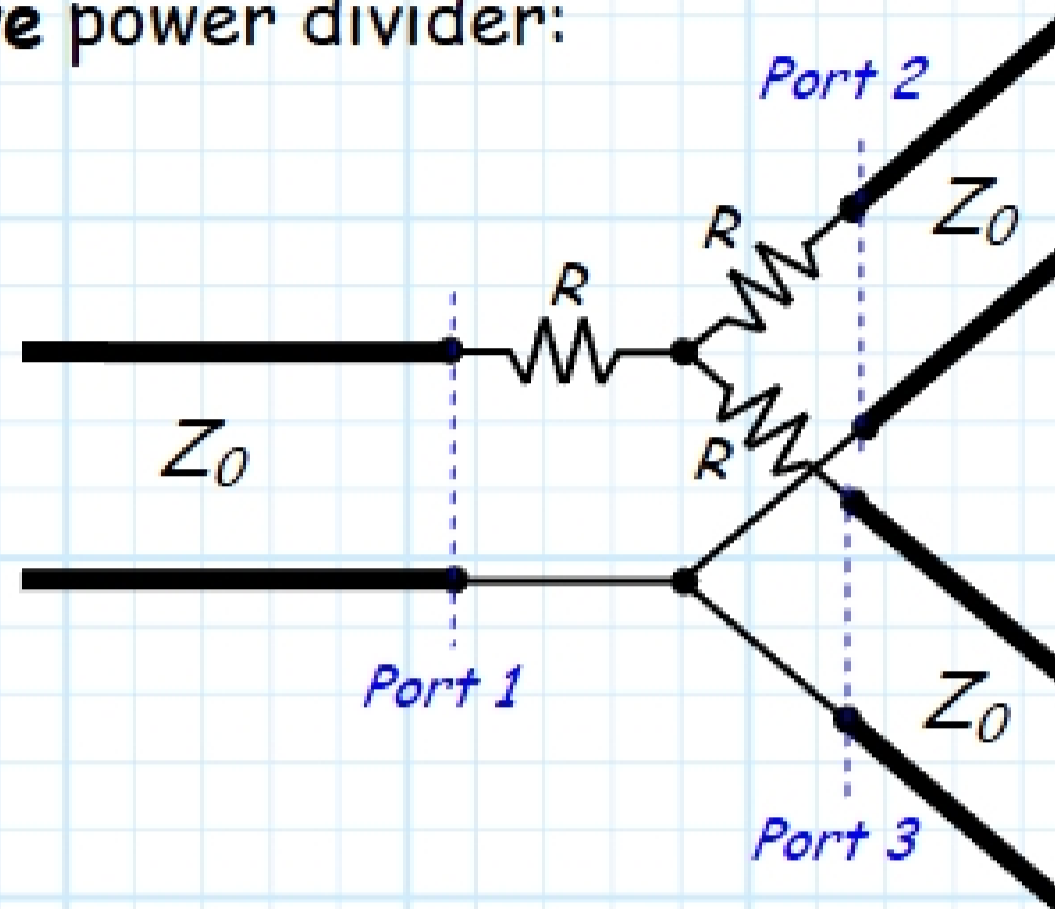
# The Resistive Divider

Consider the **resistive power divider**:



This symmetric power divider will be matched at port 1 if  $R$  is selected as:
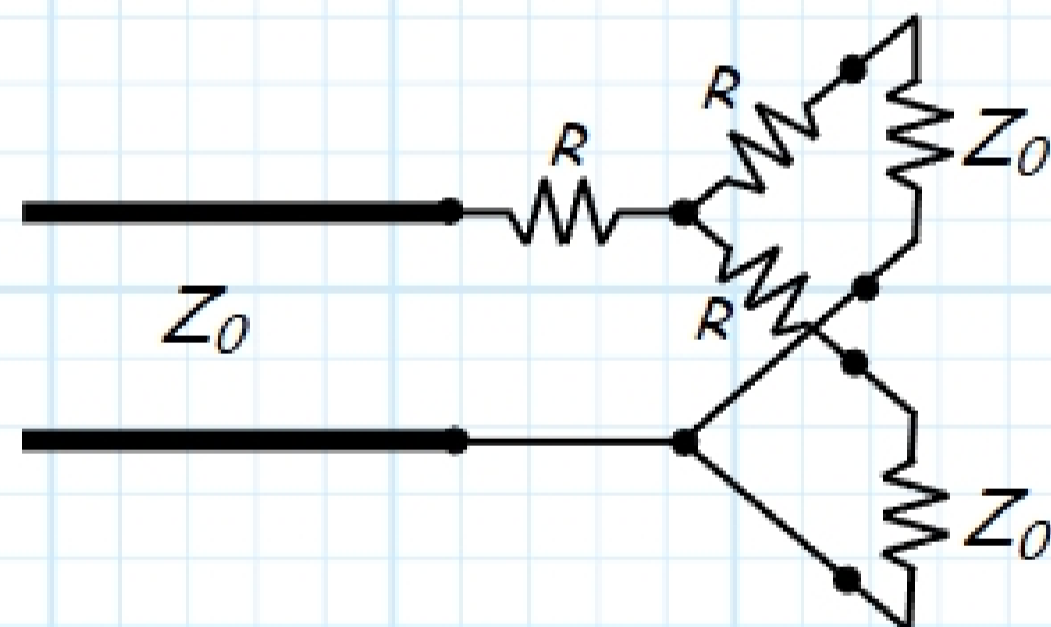
$$\begin{aligned} Z_0 &= R + (R + Z_0) \parallel (R + Z_0) \\ &= R + \frac{R + Z_0}{2} \\ &= 1.5R + \frac{Z_0}{2} \end{aligned}$$



Solving this equation, we find that port 1 is matched if:

$$R = \frac{Z_0}{3}$$