

## Project 1 Test Bench

### **Circuit**

Put your circuit in a file name `

5. Operating point and differential mode gain for  $V_{DD} = 1.2 \cdot 0.9$  V and  $V_{IC} = \text{midpoint}$ .

- Purpose: check gain variation with supply variation
- $A_{dm}$  must meet specs.

6. Common mode gain for  $V_{IC} = \text{midpoint}$ .

- Purpose: check  $A_{cm}$ .

7. AC analysis (differential mode gain) at 1 Hz for  $V_{out} = 0$  V.

8. AC analysis (differential mode gain) at 1 Hz for  $V_{out} = +0.4$  V.

- Purpose: check output range
- $A_{dm}$  must meet specs

9. AC analysis (differential mode gain) at 1 Hz for  $V_{out} = -0.4$  V.

- Purpose: check output range
- $A_{dm}$  must meet specs

Tests 7-9 use a simple feedback network to set the output voltage. An AC analysis at low frequency is used instead of a TF analysis, because the feedback network is active for DC analyses (include OP, TF), but not for AC analyses.

## Test benches

- testbench1.sp: runs tests 1-6
- testbench2.sp: runs tests 7-9

Usage: put