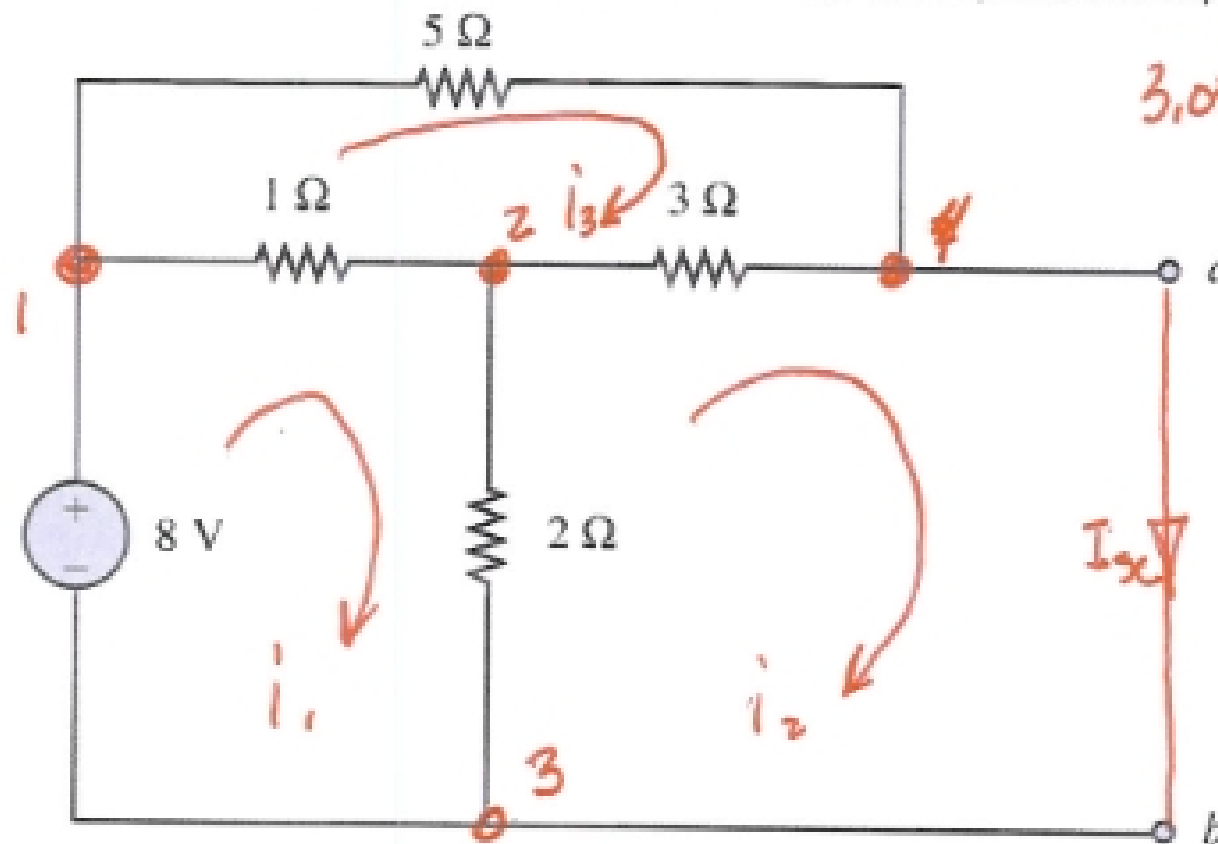



3.54 Norton Equivalent

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



Norton

$3.054A = I_N$

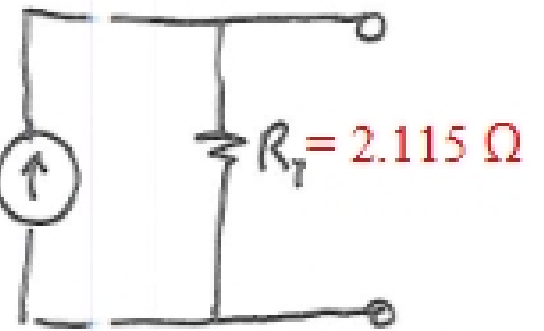


Thevenin

$R_T = 2.115 \Omega$

source transform:

$V_T = 2.115 (3.054) V = 6.46 V$

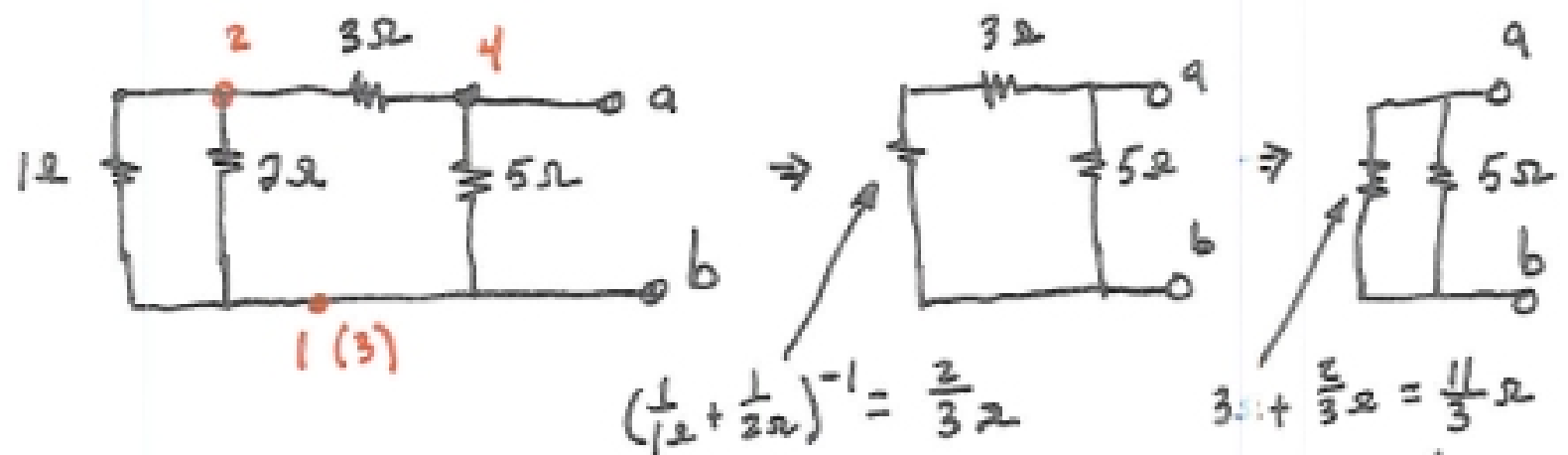- A. Remove sources & find resistance
 → replace 8V source with a short circuit
 - this means node 1 and node 3 become one node



$\left[\left(\frac{11}{3} \Omega \right)^{-1} + \frac{1}{5 \Omega} \right]^{-1} = \frac{55}{26} \Omega = 2.115 \Omega$

- B. Short a to b & find current
 Can use Node Voltage or Mesh Current

Using Mesh Current

1. Label meshes $n = 3$

$M1: \sum V_n = -8V + 1\Omega(i_1 - i_3) + 2\Omega(i_1 - i_2) = 0$

$M2: \sum V_n = 2\Omega(i_2 - i_1) + 3\Omega(i_2 - i_3) = 0$

$M3: \sum V_n = 5\Omega i_3 + 3\Omega(i_3 - i_2) + 1\Omega(i_3 - i_1) = 0$

3.54 (cont)

$$\begin{bmatrix} 3\Omega & -2\Omega & -1\Omega \\ -2\Omega & 5\Omega & -3\Omega \\ -1\Omega & -3\Omega & 9\Omega \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 8V \\ 0 \\ 0 \end{bmatrix}$$

$$\begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 5.236 \\ 3.054 \\ 1.6 \end{bmatrix} \text{ A}$$

$$I_{sc} = i_2 = 3.054 \text{ A}$$

