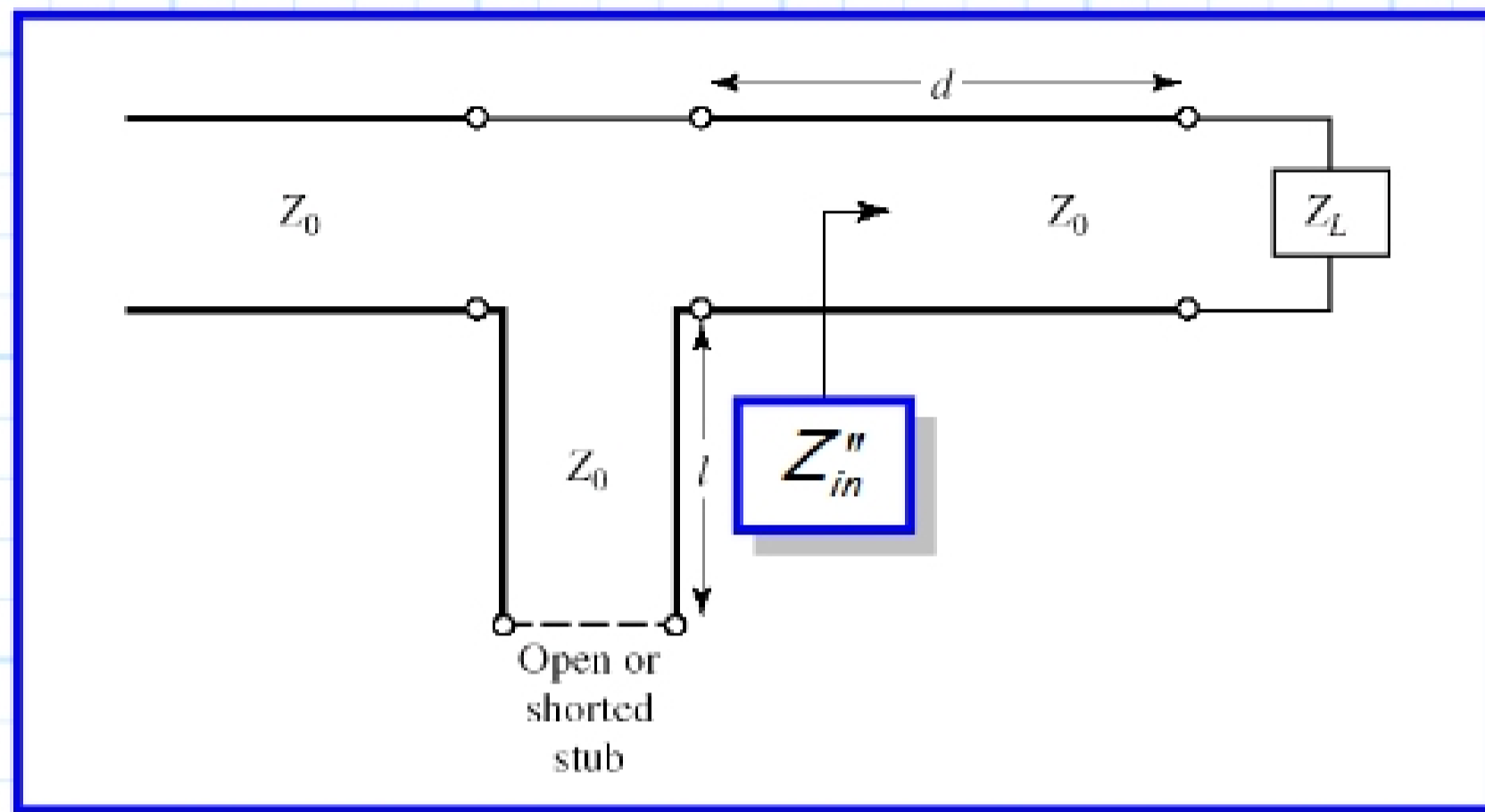
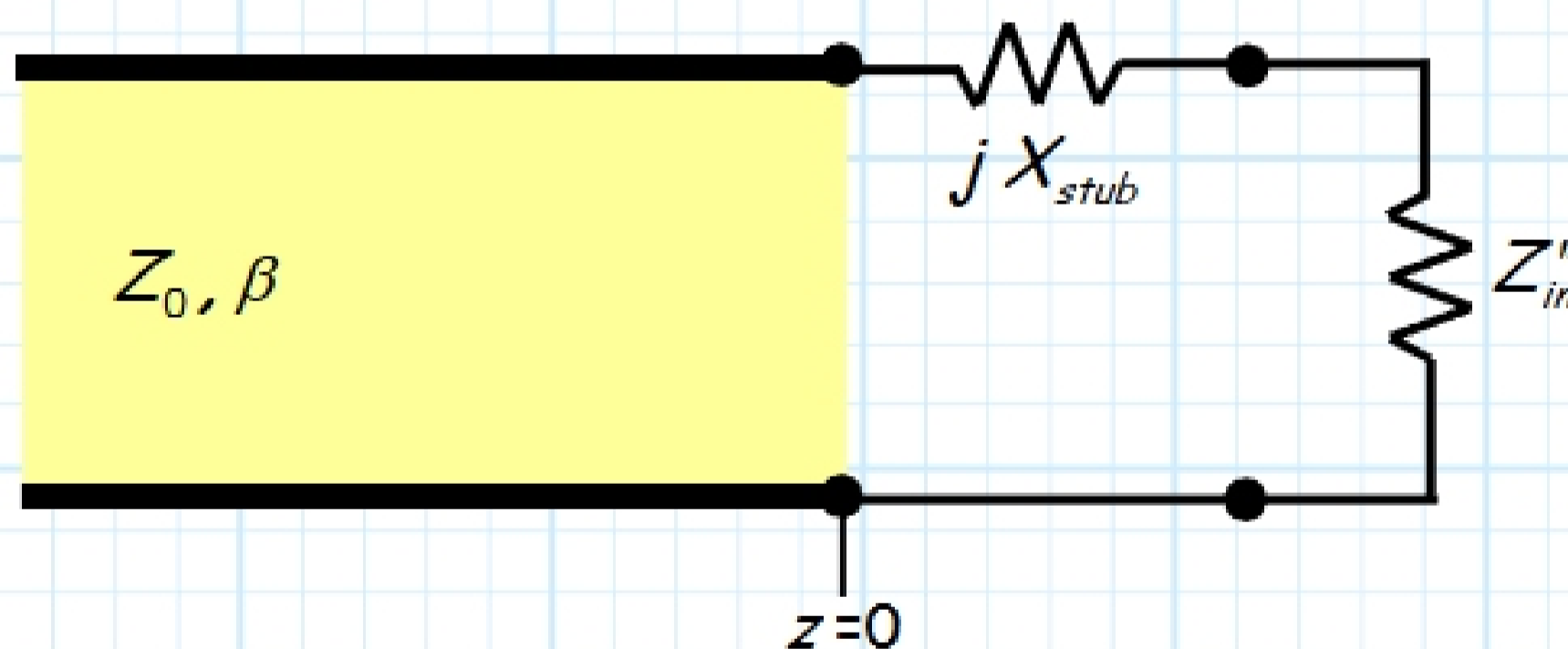


# Series Stub Tuning

Consider the following transmission line structure, with a **series stub**:



Therefore an **equivalent** circuit is:



where of course:

$$Z''_{in} = Z_0 \left( \frac{Z_L + j Z_0 \tan \beta d}{Z_0 + j Z_L \tan \beta d} \right)$$

and the reactance  $jX_{stub}$  is either:

$$jX_{stub} = \begin{cases} -jZ_0 \cot \beta l & \text{for an open-circuit stub} \\ jZ_0 \tan \beta l & \text{for an short-circuit stub} \end{cases}$$

Therefore, for a **matched** circuit, we **require**:

$$jX_{stub} + Z_{in}'' = Z_0$$

i.e.,

$$\text{Re}\{Z_{in}''\} = Z_0$$

and

$$\text{Im}\{jX_{stub} + Z_{in}''\} = 0 \Rightarrow X_{stub} = -X_{in}''$$

where

$$X_{in}'' = \text{Im}\{Z_{in}''\}$$

Note the **design parameters** for this stub tuner are transmission line **lengths**  $d$  and  $\ell$ . More specifically we:

- 1) Set  $d$  such that  $\text{Re}\{Z_{in}''\} = Z_0$ .
- 2) Then set  $\ell$  such that  $X_{stub} = -X_{in}''$ .

We have **two** choices for determining the lengths  $d$  and  $\ell$ . We can use the design equations (5.14, 5.15, 5.16) on pp. 235.

OR

we can use the **Smith Chart** to determine the lengths!

- 1) Rotate clockwise around the Smith Chart from  $z_L$  until you intersect the  $r = 1$  circle. The "length" of this rotation determines the value  $d$ . Recall there are **two** possible solutions!
- 2) Rotate clockwise from the short/open circuit point around the  $r = 0$  circle until  $x_{stub}$  equals  $-x_{in}''$ . The "length" of this rotation determines the stub length  $\ell$ .

For example, your **book** describes the case where we want to match a load of  $Z_L = 100 + j80$  (at 2 GHz) to a transmission line of  $Z_0 = 50\Omega$ .

Using **open stubs**, we find **two** solutions to this problem:

