

Exam 4 – v1
Physics 2760
FS 2013

Lab Section

Last Name _____

First Name _____

ID # _____


Solutions

This is a closed book exam. I understand, pursuant to University Regulations on academic honesty, that I am not to use any notes or information other than what is in the official, non-annotated formula sheet.

Signature _____

- For multiple choice questions, please make sure that you **circle the letter for the answer which you believe to be correct and only that answer**. If more than one answer is circled for the same problem, you will not receive credit for it.
- For full credit show your work for solutions to questions that require calculations. Write the equation from where you start to solve the problem and show your math flowing from it for full credit. **No shown work, no credit!**
- Surround your final answer with a box and **make sure you include units for your final answer**, otherwise you will be penalized!
- Don't get hung up on questions. If you find yourself spending too much time on a question, skip it and come back to it later. **Relax, read carefully, think – and then read everything again.**
- During the exam, if you have questions please **raise your hand** and the instructor will come to you and provide help.
- **The last page is the formula sheet.** Feel free to tear it off. You may keep the formula sheet after the exam.

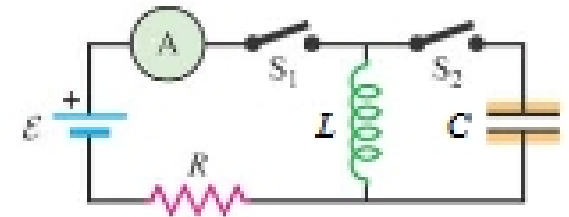1. In the circuit shown the emf is 40 V, $R = 10 \Omega$, $L = 2 \text{ mH}$ and $C = 6 \mu\text{F}$. While switch S_2 is open, switch S_1 is closed.



- a) What is the voltage across the inductor at the instant switch S_2 is closed? (1 point)

$$V_L = \mathcal{E} = 40\text{V}$$

- b) What is the current in the circuit after a long time? (1 point)

$$I = \frac{\mathcal{E}}{R} = \frac{40}{10} \Rightarrow \boxed{I = 4 \text{ A}}$$

- c) At what time is the current in the circuit half of its maximum value? (3 points)

$$i = I_{\text{max}} (1 - e^{-t/\tau}) \Rightarrow \frac{1}{2} = 1 - e^{-t/\tau} \quad e^{-t/\tau} = \frac{1}{2}$$

$$= \frac{1}{2} I_{\text{max}}$$

$$-\frac{t}{\tau} = \ln \frac{1}{2} \Rightarrow t = \tau \cdot \ln 2 = \frac{L}{R} \ln 2 \Rightarrow \boxed{t = 0.138 \text{ ms}}$$

- d) S_1 is opened and S_2 is closed. Find the maximum charge on the capacitor in the LC circuit. (4 points)

$$\frac{1}{2} LI^2 = \frac{1}{2} \frac{Q^2}{C} \Rightarrow Q^2 = LI^2 \cdot C \quad Q = I \sqrt{LC}$$

$$Q = 4 \sqrt{(2 \times 10^{-3})(6 \times 10^{-6})} \Rightarrow \boxed{Q = 4.38 \times 10^{-4} \text{ C}}$$

- e) What is the current in the inductor when the capacitor has maximum charge? (1 point)

$$I_L = 0 \text{ when } Q = Q_{\text{max}}$$

- f) At what time is the energy stored in the inductor equal to the energy stored in the capacitor? (4 points)

$$\frac{1}{2} Li^2 = \frac{1}{2} \frac{q^2}{C} \quad \text{where } \begin{cases} i = I \sin \omega t = \omega Q \cdot \sin \omega t \\ q = Q \cos \omega t \end{cases} \quad \omega = \frac{1}{\sqrt{LC}}$$

$$L (\omega Q)^2 \sin^2 \omega t = \frac{Q^2}{C} \cos^2 \omega t \Rightarrow \frac{\sin^2 \omega t}{\cos^2 \omega t} = \frac{Q^2}{\omega^2 Q^2 C L} = 1$$

$$\Rightarrow \tan^2 \omega t = 1 \Rightarrow \omega t = \frac{\sqrt{1}}{1} \Rightarrow t = \frac{\pi}{4\omega} \Rightarrow \boxed{t = 0.085 \text{ ms}}$$

2. An L-R-C series circuit has $R = 290 \Omega$. At the frequency of the source, the inductor has reactance $X_L = 900 \Omega$ and the capacitor has reactance $X_C = 500 \Omega$. The maximum voltage across the inductor is 440 V.
- a) What is the maximum current in the circuit? (2 points)

$$V_L = I \cdot X_L \Rightarrow I = \frac{V_L}{X_L} = \frac{440}{900} \Rightarrow \boxed{I = 0.48 \text{ A}}$$

- b) What is the maximum voltage across the resistor? (2 points)

$$V_R = I \cdot R \Rightarrow V_R = (0.48)(290) \Rightarrow \boxed{V_R = 139.2 \text{ V}}$$

- c) What is the phase angle? (2 points)

$$\tan \varphi = \frac{X_L - X_C}{R} = \frac{900 - 500}{290} = 1.38 \Rightarrow \boxed{\varphi = 54^\circ}$$

- d) What is the maximum voltage of the source? (2 points)

$$V = I \cdot Z \quad \text{where} \quad Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$Z = \sqrt{(290)^2 + (900 - 500)^2} \approx 494 \Omega$$

$$V = (0.48)(494) \Rightarrow \boxed{V = 237.12 \text{ V}}$$

- e) What is the average power delivered by the source? (3 points)

$$P_{\text{avg}} = \frac{1}{2} I V \cos \varphi = \frac{1}{2} (0.48)(237.12) \cos 54^\circ \Rightarrow \boxed{P_{\text{avg}} = 33.45 \text{ W}}$$

- f) Draw a phasor diagram of the voltages and current in this circuit and make sure you indicate all angles in your drawing. (3 points)

