

Soln :

General approach is

$$\underline{V}_s = 250 \angle 0^\circ + \underline{I}_s (0.05 + j0.5)$$

where  $\underline{I}_s = \underline{I}_1 + \underline{I}_2 + \underline{I}_3$

i) For  $\underline{I}_1$ ,

$(\theta_v - \theta_i) = \cos^{-1}(0.8)$   
 $(\theta_v - \theta_i) = 36.8^\circ$

$$S = \underline{V} \underline{I}_1^* = 8000 + j6000$$

$$\therefore \underline{I}_1^* = \frac{8000 + j6000}{250 \angle 0^\circ} = 32 + j24 \text{ A}_{rms}$$

$$\therefore \underline{I}_1 = 32 - j24 \text{ A}_{rms}$$

ii) For  $\underline{I}_2$  :

$$(\theta_v - \theta_i) = \cos^{-1}(0.6) = 53.1^\circ$$

$$\therefore P = (20000)(0.6) = 12,000$$

$$Q = (20000)(0.8) = 16,000$$

Since Pf is leading - capacitive load  $\rightarrow -Q$

$$\therefore S = 12000 - j16000 \text{ KVA}$$

$$\therefore \underline{I}_2^* = \frac{12000 - j16000}{250 \angle 0^\circ} = 48 - j64 \text{ A}_{rms}$$

$$\therefore \underline{I}_2 = 48 + j64 \text{ A}_{rms}$$

43-389 50 SHEETS 3 SQUARE  
43-389 100 SHEETS 3 SQUARE  
43-389 200 SHEETS 3 SQUARE  
NATIONAL

For  $\underline{I}_3$ :

$$\underline{I}_3 = \frac{250 \angle 0^\circ}{Z_3} = \frac{250 \angle 0^\circ}{2.5 + j5} = 20 - j40 \text{ Arms}$$

$$\therefore \underline{I}_s = 100 + j0 \text{ Arms}$$

$$\begin{aligned} \therefore \underline{V}_s &= 250 \angle 0^\circ + (100)(0.05 + j0.5) \\ &= 255 + j50 \\ &= 260 \angle 11^\circ \text{ rms} \end{aligned}$$

$$\therefore v_s(t) = \sqrt{2} 260 \cos(377t + 11^\circ) \text{ V}$$

Howe  $\sqrt{2}/\sqrt{2}$   $\sqrt{2}/\sqrt{2}$  10.20

10.24 (Power factor correction)